



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

I B.Tech I Sem Supply End Examination, April 2022

Basic Electrical Engineering (EEE, CSE, IT)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part – A, answer all questions which carries 20 marks.

3. In Part – B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

PART- A

(10*2 Marks = 20 Marks)

- | | | | | |
|-------|--|----|-----|-----|
| 1. a) | Write the formulae for energy store across the inductor and capacitor. | 2M | C01 | BL1 |
| b) | State Kirchhoff's of voltage law. | 2M | C01 | BL1 |
| c) | Define power factor. What is the formula for RL series circuit with AC excitation? | 2M | C02 | BL1 |
| d) | Define resonance. What is the condition for series resonance? | 2M | C02 | BL1 |
| e) | Why transformer rating in KVA but not in KW? Discuss | 2M | C03 | BL1 |
| f) | Define voltage regulation in transformer. | 2M | C03 | BL1 |
| g) | Why single-phase induction motor is not self-starting? | 2M | C04 | BL1 |
| h) | What are the applications of single phase induction motor? | 2M | C04 | BL1 |
| i) | What is the purpose of fuse? | 2M | C05 | BL1 |
| j) | What is earthing? Give the importance of earthing? | 2M | C05 | BL1 |


PART- B

(10*5 Marks = 50 Marks)

- | | | | | |
|---|---|-----|-----|-----|
| 2 | Define Superposition Theorem and verify it on a suitable example. | 10M | C01 | BL3 |
|---|---|-----|-----|-----|

OR

- | | | | | |
|---|---|-----|-----|-----|
| 3 | For the circuit show below $R_1 = 6k\Omega$, $R_2 = 80k\Omega$, $R_3 = 4k\Omega$, $R_4 = 25k\Omega$, $R_5 = 4k\Omega$, $R_6 = 45k\Omega$ and $V_s = 40v$ find the values for Thevenin's equivalent circuit respect to the terminals a and b. | 10M | C01 | BL3 |
|---|---|-----|-----|-----|

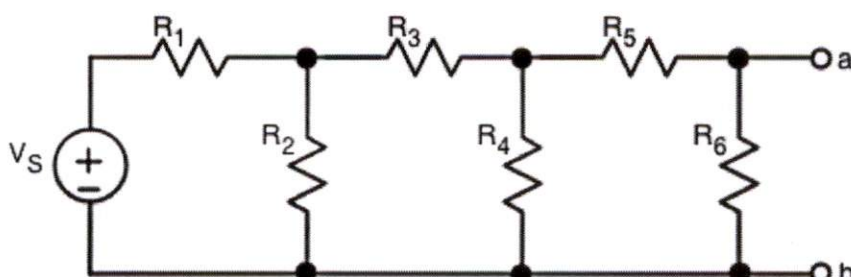

- 4 Define the terms Real Power, Reactive Power, Apparent Power and Power Factor of a A.C circuit with suitable examples. 10M C02 BL1
- OR**
- 5 Explain the series RLC resonance. Define the terms related to resonance. 10M C02 BL4
- 6 Mention various types of losses in a Transformer. Explain the factors influencing these losses. 10M C03 BL4
- OR**
- 7 Write short notes on star-delta connection in three phase transformer. 10M C03 BL1
- 8 Explain the constructional details and principle of operation of a 3-phase Induction motor. 10M C04 BL4
- OR**
- 9 Explain the speed control methods of separately excited dc motor 10M C04 BL4
- 10 Write short notes on i) ELCB and ii) MCCB 10M C05 BL1
- OR**
- 11 What are the types of Batteries? Discuss Important Characteristics for Batteries. 10M C05 BL2

---oo0oo---