



MARRI LAXMAN REDDY
INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

I B.Tech I Sem Supply Examination, December 2021

BASIC ELECTRICAL ENGINEERING

(EEE, CSE & IT)

Time: 3 Hours.

Max. Marks: 70

Note: 1. This question paper contains two parts A and B.

2. Part- A is Compulsory. Answer all Questions which carries 20 marks.

3. Part – B consists 5 units. Answer any one question from each unit. Each question carries 10 marks and may have a, b as sub questions.

PART- A

(10*2 Marks=20Marks)

- | | | | |
|--|----|-----|-----|
| 1. a) Define Active element and give example. | 2M | CO1 | BL1 |
| b) State Kirchhoff's of current law . | 2M | CO1 | BL1 |
| c) What is the phase angle between voltage and current in pure inductor? | 2M | CO2 | BL3 |
| d) Define resonance. What is the condition for series resonance? | 2M | CO2 | BL1 |
| e) What are the losses in transformer? | 2M | CO3 | BL1 |
| f) Write different connections of three phase transformers. | 2M | CO3 | BL2 |
| g) Draw torque slip characteristic of three phase induction motor. | 2M | CO4 | BL1 |
| h) What are the applications of single phase induction motor? | 2M | CO4 | BL2 |
| i) Define Earthing. | 2M | CO5 | BL1 |
| j) What are the types of cables? | 2M | CO5 | BL2 |


PART - B

(5*10 Marks=50Marks)

UNIT-I

Find the power loss in 1Ω resistor shown in figure


2 a)

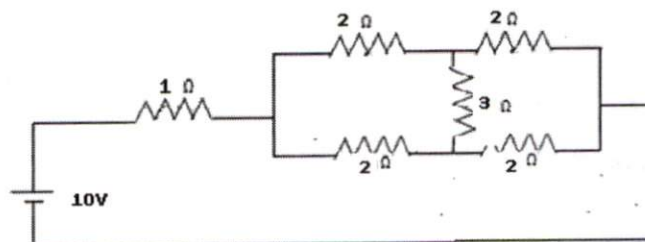

5M CO1 BL3

Using Thevenin theorem find I_0 for circuit shown below


b)

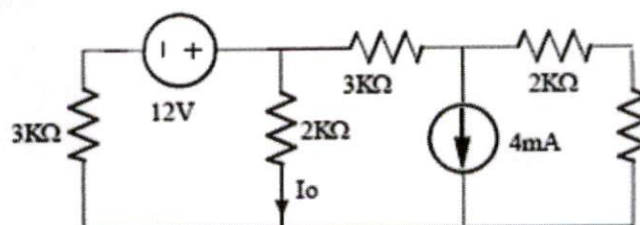

5M CO1 BL3

OR

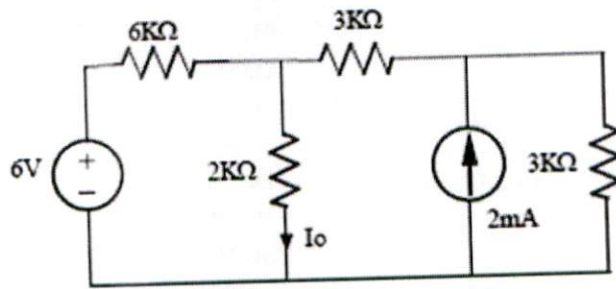- 3 a) Derive the expression for current flowing through first order RL circuit for DC excitation. 5M CO2 BL3
Using Norton theorem find I_0 for circuit shown below




b)

5M CO2 BL3

UNIT-II

Find the Average value of the periodic waveform shown in below figure

4 a)

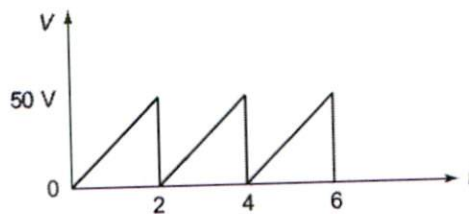


5M CO2 BL3

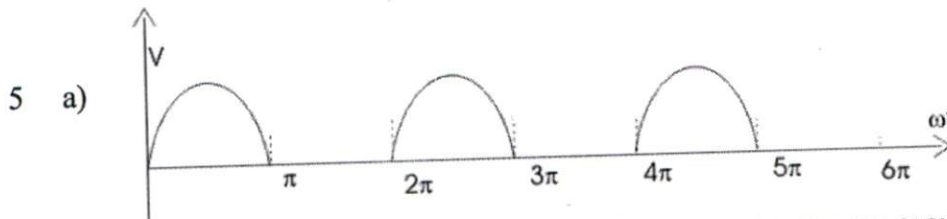- b) A series circuit consisting of a 10Ω resistor, $100\mu\text{F}$ capacitor and a 10mH inductor is driven by 50Hz a.c voltage source of maximum value 100 volts . Calculate the equivalent impedance, current in the circuit, power factor and power dissipated in the circuit. 5M CO2 BL3

OR

Determine RMS value of the wave form shown in below figure



5 a)

5M CO2 BL3

- b) The impedances of parallel circuit are $Z_1=(8+j10)$ & $Z_2=(10-j12)$. If the applied voltage is 120V , find
- Current & power of each branch.
 - Overall current & power factor of the combination

5M CO2 BL3

UNIT-III

- 6 a) Explain operation of single phase ideal transformer. 10M CO2 BL2

OR

- 7 a) Describe working of Auto transformer. 5M CO2 BL1

- b) Draw the equivalent circuit of transformer and explain the significance of each term in it. 5M CO2 BL1

UNIT-IV

- 8 a) Explain Construction and working of synchronous generators. 10M CO3 BL2

OR

- 9 a) Describe star delta method of starting of a squirrel cage three phase induction motor. 5M CO3 BL1

- b) Discuss how to control the speed of separately excited dc motor below the rated speed. 5M CO3 BL1

UNIT-V

- 10 a) Explain working principle of MCB. 5M CO4 BL2
b) What are the types of Batteries? Discuss Important Characteristics for Batteries. 5M CO4 BL2

OR

- 11 a) Explain working principle of ELCB. 5M CO4 BL2
b) Describe Elementary calculations for energy consumption. 5M CO4 BL2

---oo0oo---

