



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

I B.Tech I Sem Supply End Examination, November 2020

BASIC ELECTRICAL ENGINEERING

(EEE, CSE, IT)


Time: 2 Hours.

Max. Marks: 70


Note: 1. Answer any FIVE questions.

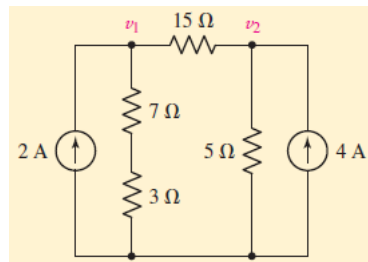2. Each question carries 14 marks and may have a, b as sub questions.


- 1 a) Define Superposition Theorem and verify it on a suitable example. 7M
- b) Determine the current flowing left to right through the 15 Ω resistor in the figure shown below. 7M



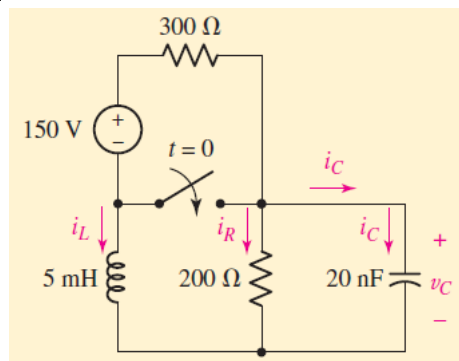- 2 Find an expression for $v_C(t)$ valid for $t > 0$ in the circuit shown in below figure. 14M



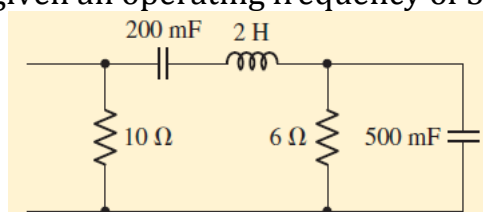- 3 a) Define the terms Real Power, Reactive Power, Apparent Power and Power Factor of a A.C circuit. 7M
- b) Determine the equivalent impedance of the network shown in Below figure, given an operating frequency of 5 rad/s. 7M



- | | | |
|---|---|-----|
| 4 | Define efficiency and regulation of a single-phase Transformer. Give the expressions for each and discuss about the effects of load power-factor on them. | 14M |
| 5 | a) Explain the series RLC resonance. Define the terms related to resonance. | 7M |
| | b) Mention various types of losses in a Transformer. Explain the factors influencing these losses. | 7M |
| 6 | List out different speed control methods employed for Induction motor. Explain rotor resistance control method with suitable Torque-Slip characteristics. | 14M |
| 7 | a) Explain the constructional details and principle of operation of a 3-phase Induction motor. | 7M |
| | b) Explain the constructional details and electrical properties of various types of Cables. | 7M |
| 8 | Write short notes on i) ELCB and ii) MCCB | 14M |

---oo0oo---