



## I B.TECH I Sem Supplementary Examination, October 2022

**Basic Electrical Engineering**

(CSE, IT)

**Time: 3 Hours.****Max. Marks: 70**

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.


**PART- A****(10\*2 Marks = 20 Marks)**

- |       |   |    |     |     |
|-------|---|----|-----|-----|
| 1. a) | State Thevenin's theorem.   | 2M | C01 | BL1 |
| b)    | List any three types of circuit elements.                           | 2M | C01 | BL1 |
| c)    | Define the RMS value of an alternating quantity.                    | 2M | C02 | BL1 |
| d)    | What is the significance of 'j' notation in alternating quantities? | 2M | C02 | BL2 |
| e)    | Draw the no-load phasor diagram of a transformer.                   | 2M | C03 | BL2 |
| f)    | What is the condition for maximum efficiency of a transformer?      | 2M | C03 | BL1 |
| g)    | List out the various speed control methods of an induction motor.   | 2M | C04 | BL1 |
| h)    | What are the main components of a synchronous motor?                | 2M | C04 | BL1 |
| i)    | What is the necessity of battery backup?                            | 2M | C05 | BL1 |
| j)    | What is the full form of ELCB?                                      | 2M | C05 | BL1 |

**PART- B****(10\*5 Marks = 50 Marks)**

- |       |  |    |     |     |
|-------|--|----|-----|-----|
| 2. a) | State Kirchhoff's current and voltage laws with neat a figure. | 5M | C01 | BL1 |
| b)    | State and explain the Superposition theorem.                   | 5M | C01 | BL1 |

**OR**

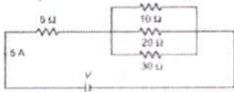- |       |   |    |     |     |
|-------|---|----|-----|-----|
| 3. a) | Derive the expression for current $i(t)$ in series R-C circuit without source       | 5M | C01 | BL3 |
| b)    |  | 5M | C01 | BL2 |

Calculate the equivalent resistance of the circuit.

- |       |  |    |     |     |
|-------|--|----|-----|-----|
| 4. a) | Derive the condition for the series RLC resonance circuit. | 5M | C02 | BL3 |
| b)    | Define power factor, active power, and reactive power.     | 5M | C02 | BL1 |

**OR**

|           |    |   |    |     |     |
|-----------|----|---|----|-----|-----|
| 5         | a) | Derive the relation between phase and line voltages in a 3-phase star-connected system.   | 5M | C02 | BL3 |
|           | b) | A coil having a resistance of 10 k $\Omega$ and inductance of 50 mH is connected to a 10 volts, 10 kHz power supply. Calculate the impedance. | 5M | C02 | BL2 |
| 6         | a) | Draw the equivalent circuit of a single-phase transformer.  | 5M | C03 | BL2 |
|           | b) | Discuss the autotransformer with a neat sketch.   | 5M | C03 | BL2 |
| <b>OR</b> |    |   |    |     |     |
| 7         | a) | With a neat fig., explain the constructional details of a transformer.  | 5M | C03 | BL2 |
|           | b) | Define the efficiency and regulation of a transformer.  | 5M | C03 | BL1 |
| 8         | a) | Discuss various starting methods of an induction motor.   | 5M | C04 | BL3 |
|           | b) | What are the various losses present in an induction motor?  | 5M | C04 | BL2 |
| <b>OR</b> |    |   |    |     |     |
| 9         | a) | How does the rotor of an induction motor will rotate?   | 5M | C04 | BL1 |
|           | b) | Draw the torque-slip characteristic of an induction motor.  | 5M | C04 | BL2 |
| 10        | a) | Explain any three components of an LT switch gear.  | 5M | C05 | BL1 |
|           | b) | Define earthing and discuss the necessity of earthing.  | 5M | C05 | BL1 |
| <b>OR</b> |    |   |    |     |     |
| 11        | a) | List the different types of batteries and explain any one type.   | 5M | C05 | BL1 |
|           | b) | Discuss power factor improvement methods.   | 5M | C05 | BL2 |

---oo0oo---

**CO: Course Outcome**

**BL - Blooms Taxonomy Levels**