

Final — 23.10.2021

Course Code: 1930405

Roll No:

MLRS- R19



# MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

## II B.Tech I Sem Supply End Examination, October 2021 ANALOG AND DIGITAL ELECTRONICS (CSE & IT)

Time: 3 Hours.


Max. Marks: 70

Note: 1. Answer any FIVE questions.

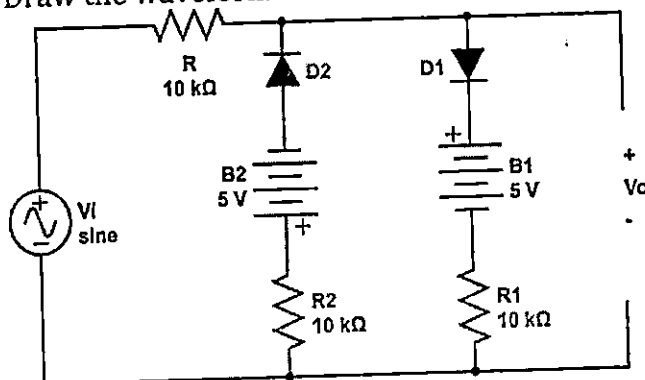2. Each question carries 14 marks and may have a, b as sub questions.

- 1 a) Explain how a diode used for rectification? Draw the full wave rectifier circuit diagram and derive the expression for ripple factor. 7M CO1 BL4
- b) How a tunneling phenomenon is used as a diode and draw its band diagrams. 7M CO1 BL2

- 2 a) Draw the waveform obtained at  $V_0$  and indicate all the voltages. 7M CO1 BL5



- b) Draw the circuit model and V-I characteristics of photo diode and explain its conducting process. 7M CO1 BL2

- 3 a) Draw and explain the circuit diagram, input and output characteristics of transistor in Common Collector configuration. 9M CO2 BL4
- b) Find the collector and emitter currents for a transistor when both emitter and collector junctions are reverse biased. Assume  $I_{CO}=5\mu A$ ,  $I_{EO}=3.57\mu A$  and  $\alpha_N=0.98$ . 5M CO2 BL5

- 4 Derive the voltage gain of Common source MOSFET amplifier with a neat circuit diagram and draw its equivalent circuit diagrams and compare it with Common Drain amplifier. 14M CO3 BL4

- 5 a) Explain the effect of coupling capacitor on the performance parameters of RC coupled amplifier. 7M CO2 BL4
- b) Draw and explain the working of NOR gate in DTL using truth table 7M CO3 BL4

- 6 Find all min terms and design logic circuit using NAND gates only by k-map method for the following function 14M CO4 BL5

$$f(x, y, z, w) = \sum 0,1,2,4,7,8,9,10,12,14$$

- 7 a) Design a 4-bit binary adder and draw its logic diagram. 7M CO5 BL4  
 b) Reduce the states for the following state table: 7M CO4 BL5

Present state	Next State		Output	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	C	D	0	0
C	A	D	0	0
D	E	F	0	1
E	A	F	0	1
F	G	F	0	1
G	A	F	0	1

- 8 Design a ripple counter using D flip-flop and write its state table and explain why it is called Asynchronous counter? 14M CO5 BL4

---0000---