



II B.Tech I Sem Supplementary Examination, July-2022

Electronic Devices and Circuits

(ECE)

Time: 3 Hours.**Max. Marks: 70**

Note: 1. Answer any FIVE questions.

2. Each question carries 14 marks and may have a, b as sub questions.

- | | | | | | |
|---|----|---|----|-----|-----|
| 1 | a) | Explain the following terms (i) Static resistance (ii) Dynamic resistance (iii) Junction resistance (iv) Reverse resistance of a Diode with suitable figures. | 7M | C01 | BL4 |
| | b) | Draw the circuit diagram of Full-wave rectifier and derive the expressions for average value, R.M.S value and voltage drop across diode. | 7M | C01 | BL6 |
| 2 | a) | A half wave rectifier has a load of 5.5 K Ω . If the diode resistance and the secondary coil resistance together have a resistance of 500 Ω and the input voltage has a signal voltage of 240 V, calculate i) Peak, average and rms value of current flowing. ii) dc power output. iii) ac power input iv) Efficiency of the rectifier. | 7M | C01 | BL3 |
| | b) | Define diffusion and transition capacitance of p-n junction diode. Prove that diffusion capacitance is proportional to current I. | 7M | C01 | BL3 |
| 3 | a) | Sketch a family of CB input and output characteristics of for a transistor? Indicate the cutoff, active and saturation regions? | 7M | C02 | BL3 |
| | b) | A transistor with $\beta = 100$ is to be used in Common Emitter Configuration with collector to base bias. The collector circuit resistance is $R_C = 1k\Omega$ and $V_{CC} = 10V$. Assume $V_{BE} = 0$. i) Choose R_B so that the quiescent collector to emitter voltage is 4V. ii) Find the stability factor. | 7M | C02 | BL3 |
| 4 | a) | List out different types of biasing methods. Derive the equation for stability factor for fixed bias. | 7M | C02 | BL6 |
| | b) | Determine the quiescent currents and the collector to emitter voltage for a Ge transistor with $\beta = 50$ in the self biasing arrangements. The circuit component values are $V_{CC} = 20V$, $R_C = 2k\Omega$, $R_e = 0.1 k\Omega$, $R_1 = 100 k\Omega$ and $R_2 = 5 k\Omega$. Find the stability factor S. | 7M | C02 | BL3 |
| 5 | a) | Explain the working of Zener diode as voltage regulator. | 7M | C03 | BL4 |
| | b) | Discuss the characteristics and applications of UJT. | 7M | C03 | BL2 |

- | | | | | | |
|---|----|--|-----|-----|-----|
| 6 | a) | Explain the construction and operation of JFET and draw its characteristics. | 7M | C03 | BL4 |
| | b) | Explain how a FET is used as a voltage variable resistor. | 7M | C03 | BL4 |
| 7 | | Draw the circuit diagram of CC amplifier using hybrid parameters and derive the expression for A_i , A_v , R_i and R_o . | 14M | C04 | BL |
| 8 | | Explain the working of a n-channel depletion MOSFET. Discuss its characteristics. | 14M | C05 | BL |

---oo0oo---