



**II B.Tech I Sem Regular End Examination, March 2021**  
**NETWORK ANALYSIS AND TRANSMISSION LINES**  
 (ECE)


**Time: 3 Hours.**

**Max. Marks: 70**


**Note: 1. Answer any FIVE questions.**

**2. Each question carries 14 marks and may have a, b as sub questions.**

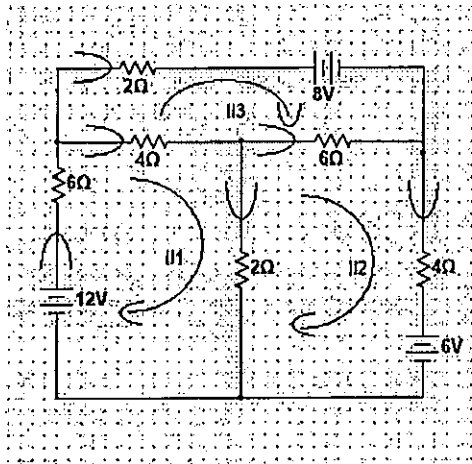
1. a) Evaluate the mutual inductance for different types of magnetic coupling schemes using dot convention with neat sketches? 7M CO BL
- b) Calculate the value of 'K' for the series circuit, if  $L_1 = 15 \text{ mH}$ ,  $L_2 = 30 \text{ mH}$  and  $M = 12 \text{ mH}$ . 7M CO BL
  
2. a) Design the Oriented Graph and Frame the incident, tie-set & Cut-set Matrix? 7M CO BL



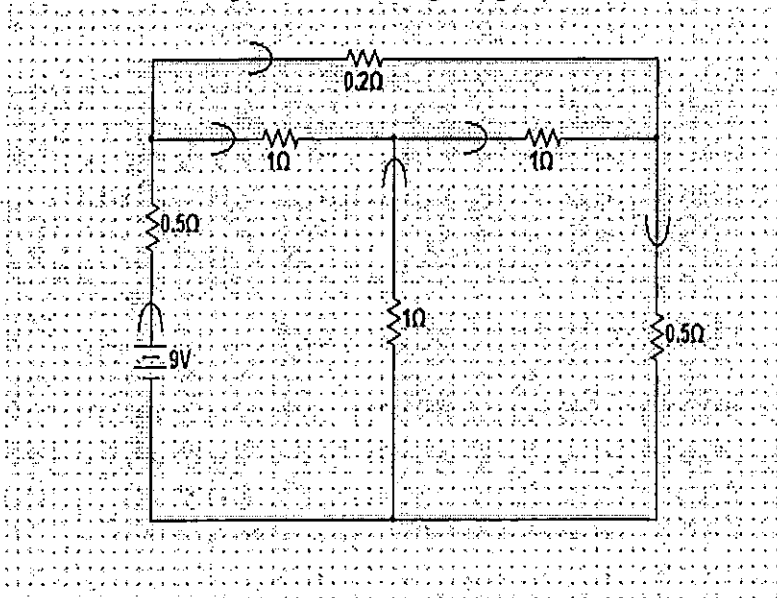
- b) Calculate the loop currents for giving oriented Graph using tie-set. 7M CO BL



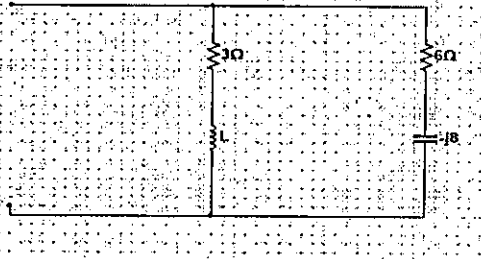
- 3 a) Derive the expressions for transient parameters in the series RLC Circuit? 7M CO BL
- b) Calculate the L for which the circuit is resonant at frequency  $\omega = 10,000$  rad/sec. 7M CO BL



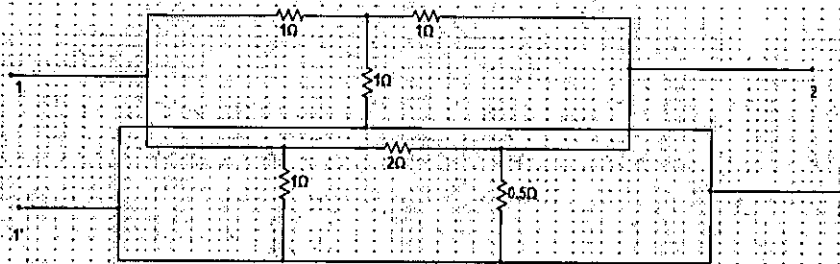- 4 a) Determine the Y-parameters for the network shown in figure. 7M CO BL



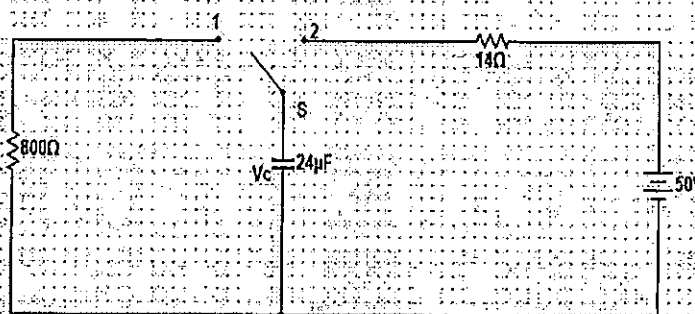- b) For the given n/w Switch is position 1 for long time and it is moved to position 2 at  $t=0$ . Determine the  $V_c(0+)$ ,  $I_c(0+)$ ? 7M CO BL



- 5 a) A dc voltage of 40 V is applied for a series RLC circuit, when the switch is closed at  $t = 0$ . Find the current transient for  $R = 20$  ohm,  $L = 2$  H,  $C = 0.2$  F 7M CO BL
- b) Design T-Pad attenuator to given attenuation of 60 db and to work in line of impedance ( $R_0$ ) 500 ohms 7M CO BL

- |   |    |   |    |    |    |
|---|----|---|----|----|----|
| 6 | a) | Derive the Equations of attenuation constant & phase constant of Transmission Lines in terms of R, L, G, C?   | 7M | CO | BL |
|   | b) | Determine the approximation values of $Z_0$ , alpha, beta for underground cable at 1600 Hz and it has<br>$R=44 \text{ ohm/km}$ , $G=1 \text{ } \mu\text{mho/km}$ , $L=0.001 \text{ H/km}$ , $C=0.065 \text{ } \mu\text{F/km}$ . | 7M | CO | BL |
| 7 | a) | Define the attenuation & derive the condition for minimum attenuation?  | 7M | CO | BL |
|   | b) | What are applications of Smith Chart and also Describe the Single stub matching?  | 7M | CO | BL |
| 8 | a) | Derive the expression for characteristic impedance of lossless line and obtain the expression for input impedance at quarter wave line.   | 7M | CO | BL |
|   | b) | Derive the expressions for VSWR in terms of reflection coefficient  | 7M | CO | BL |

---oo0oo---