



II B.Tech I Sem Supplementary Examination, February-2022

Network Analysis and Transmission Lines

(ECE)


Time: 3 Hours.**Max. Marks: 70**

Note: 1. Answer any FIVE questions.

2. Each question carries 14 marks and may have a, b as sub questions.

Design and solve the tie test matrix schedule

1 a)

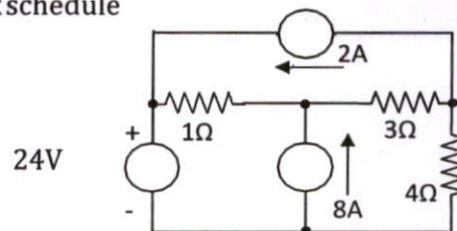

7M CO1 BL6

Two identical coils with $L=0.02\text{H}$ have a coefficient of coupling of 0.8.

b) Determine the mutual inductance and the two equivalent inductances with the two coils connected in series aiding and series opposing

7M CO1 BL5

Define and explain the following with an example:

- 2
- Oriented Graph
 - Tree of a Graph
 - Tie set and a basic Tie set
 - Cut set and a basic Cut set.

14M CO1 BL1

3 a) A Series Resonant Circuit has a B.W of 100Hz & it contains a 20mh inductance, 20uf capacitance. Using the above Data Determine the f_0, Q, Z_{in} (at resonance) ?

7M CO2 BL5

b) Derive and design the response of a series RLC circuit for step input.

7M CO2 BL5


4 Illustrate the expression for total impedance of the circuit having (i) R-L parameters (ii) R-C parameters (iii) R-L-C parameters. with neat sketches of diagrams

14M CO2 BL3


5 a) Evaluate the relationship between Z parameters and Y parameters Determine the y-parameters of the pi (π) network shown in Figure

7M CO3 BL5

b)

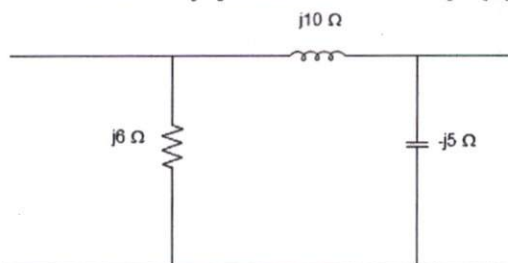

7M CO3 BL5

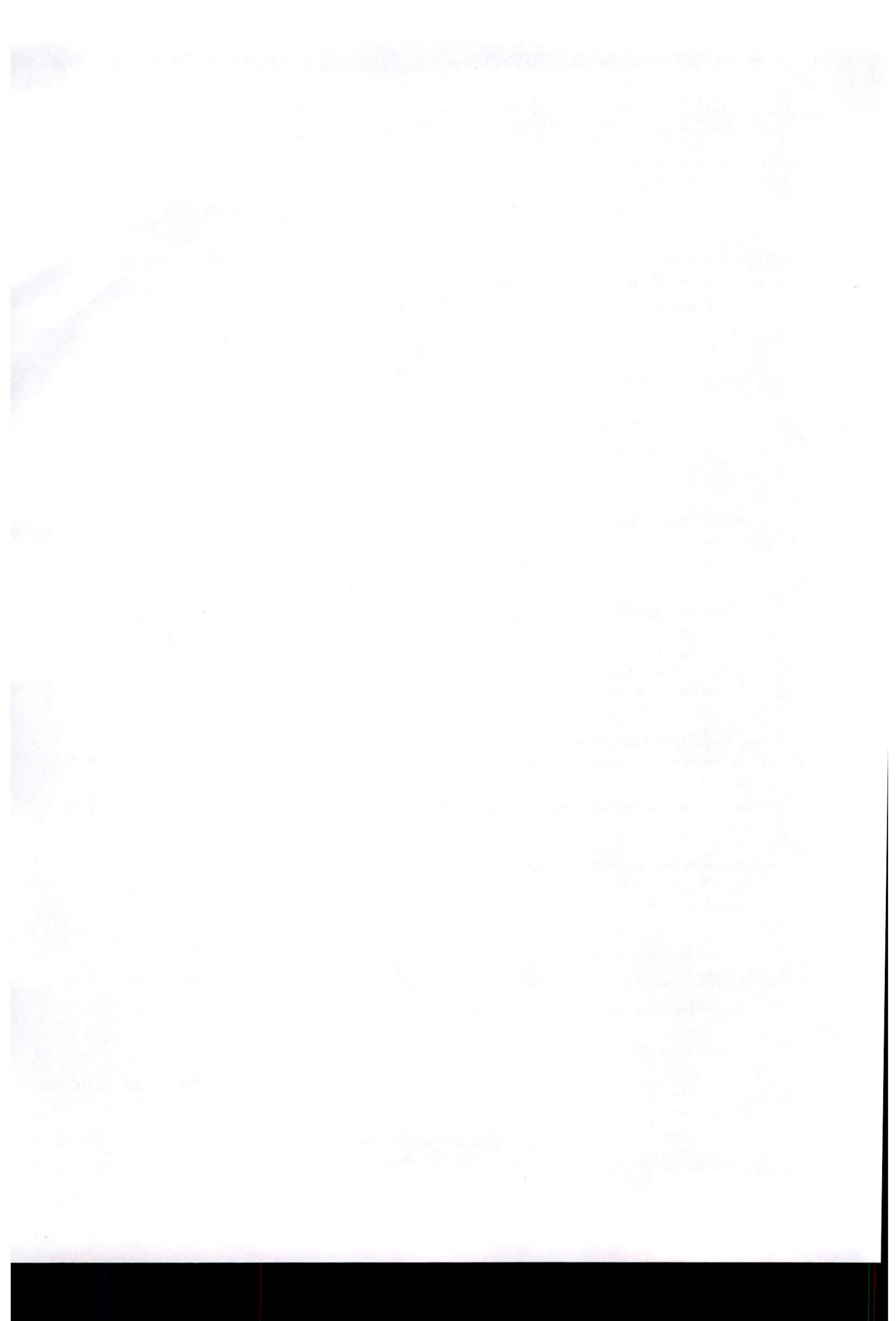

6	Explain clearly the terms: a) Characteristic Impedance and b) Image Transfer Constant	14M	CO3	BL2
7	a) Explain about waveform distortion and distortion less line condition?	7M	CO4	BL2
	b) Evaluate the equation of attenuation constant and phase constant of TL in terms of R,L, C, G?	7M	CO4	BL5
8	Explain the single stub matching ,mention its types. Determine the expressions for length and location of stub to achieve impedance matching	14M	CO5	BL5

---oo0oo---