



# MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi &amp; Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade &amp; Recognized Under Section 2(f) &amp; 12(B) of the UGC act, 1956

II B.Tech II Sem Supply End Examination, March 2022

## Linear IC Applications

(ECE)

**Time: 3 Hours.****Max. Marks: 70**

Note: 1. Answer any FIVE questions.

2. Each question carries 14 marks and may have a, b as sub questions.

- |   |    |  |    |     |     |
|---|----|--|----|-----|-----|
| 1 | a) | Explain the Differential Amplifier circuit using Op-Amp  | 7M | C01 | BL5 |
|   | b) | Define Slew Rate and how it effects Op- Amp performance explain  | 7M | C01 | BL1 |
| 2 | a) | Define CMRR, Input offset current, Gain, Bandwidth, and Input offset Voltage   | 7M | C01 | BL1 |
|   | b) | Write the characteristics of ideal and practical Op -Amp   | 7M | C01 | BL4 |
| 3 | a) | Compare the difference between Differentiator and Integrator   | 7M | C02 | BL2 |
|   | b) | Explain Bistable multivibrator in detail using 741   | 7M | C02 | BL2 |
| 4 | a) | Explain about the Schmitt Trigger and how it can be used as a wave form generator  | 7M | C02 | BL2 |
|   | b) | Explain about the RC Phase Shift Oscillator and Derive the expression for frequency of oscillator.                               | 7M | C03 | BL2 |
| 5 | a) | What is VCO and draw and explain the functional block diagram of VCO   | 7M | C03 | BL1 |
|   | b) | Draw the circuit diagram of first order high pass filter and its frequency response and derive the expression for output voltage | 7M | C03 | BL6 |
| 6 | a) | Configure a 555 timer as Astable multivibrator and Explain.  | 7M | C04 | BL3 |
|   | b) | Draw and Explain the basic block diagram of PLL  | 7M | C04 | BL2 |
| 7 | a) | Derive the expression for Capture range and lock in range  | 7M | C04 | BL5 |
|   | b) | Explain 4-bit R -2R ladder type D/A converter in detail  | 7M | C05 | BL2 |
| 8 | a) | With neat diagram explain about the DAC in detail  | 7M | C05 | BL4 |
|   | b) | Draw the block diagram of parallel Comparator type ADC and explain the operation of it.  | 7M | C05 | BL6 |