



## II B.Tech II Sem Regular End Examination, August 2021

**ELECTRONIC CIRCUIT ANALYSIS****(ECE)****Time: 3 Hours.****Max. Marks: 70**

Note: 1. Answer any FIVE questions.

2. Each question carries 14 marks and may have a, b as sub questions.

- |   |   |    |     |    |
|---|---|----|-----|----|
| 1 | a) Design a small-signal low-frequency model of two-stage CE-Amplifier.   | 7M | C01 | L6 |
|   | b) Design a BJT Cascade Amplifier circuit diagram and then derive the expressions for $A_i$ , $A_v$ , $R_i$ and $R_o$ .   | 7M | C01 | L6 |
| 2 | a) Describe the effect of coupling and bypass capacitors on low-frequency response of BJT Amplifiers.   | 7M | C01 | L2 |
|   | b) Classify Amplifiers based on different parameters. Also, correlate each one of them with the other type.   | 7M | C01 | L2 |
| 3 | a) Explain the method of analysis of feedback amplifier.  | 7M | C02 | L4 |
|   | b) Calculate the voltage gain, input impedance and output impedance of a voltage series feedback amplifier having an open loop gain $A=300$ , $R_i=1.5K\Omega$ , $R_o=50K\Omega$ and $\beta=1/20$ . | 7M | C02 | L3 |
| 4 | a) Show how bandwidth of an amplifier increases with negative feedback.   | 7M | C02 | L4 |
|   | b) State the conditions for oscillations.   | 7M | C03 | L1 |
| 5 | a) Draw the circuit of Hartley oscillator and explain its working. Derive the expression for frequency of oscillation and condition for sustaining of oscillations.                                 | 7M | C03 | L4 |
|   | b) Derive the expression for frequency of oscillation of BJT RC phase-shift oscillator with necessary explanation.  | 7M | C03 | L4 |
| 6 | a) Draw and explain the operation of Complementary symmetry class B Push-pull amplifier.  | 7M | C04 | L4 |
|   | b) What is a tuned amplifier? Give any one practical application of it.   | 7M | C04 | L1 |
| 7 | a) Briefly discuss the distortion in power amplifiers.  | 7M | C04 | L2 |
|   | b) Design Astable Multivibrator and explain its operation with help of circuit diagram and waveforms.   | 7M | C05 | L6 |
| 8 | a) Draw the circuit of Bi-stable Multivibrator and explain its operation.   | 7M | C05 | L2 |
|   | b) Discuss the concepts of transistor Bootstrap Time Base Generator.  | 7M | C05 | L2 |