



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

II B.Tech II SEM Supply End Examination, March 2022

Electronic Circuit Analysis

(ECE)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Answer any FIVE questions.

2. Each question carries 14 marks and may have a, b as sub questions.

- | | | | | | |
|---|----|--|-----|-----|----|
| 1 | a) | Derive an expression for hybrid- Π conductance in terms of low-frequency h-parameters. | 7M | C01 | BL |
| | b) | Draw the circuit diagram of Darlington emitter follower and derive the expression for input impedance. | 7M | C01 | BL |
| 2 | a) | Explain the working of cascade amplifier with neat circuit diagram. | 7M | C01 | BL |
| | b) | A transistor biased at 5mA, 10V, $h_{ie} = 600\Omega$, $h_{fe} = 100$, $C_C = 3pF$ and current gain of 10 at a frequency of 20MHz. Find β cut off frequency, gain band width product, $r_{b'e}$ and $r_{b'b'}$. | 7M | C01 | BL |
| 3 | a) | Outline the general characteristics of Negative Feedback Amplifiers. | 7M | C02 | BL |
| | b) | Draw the practical circuit for voltage series feedback amplifier and then find the voltage gain, input impedance and output impedance. | 7M | C02 | BL |
| 4 | a) | Design a class-B power amplifier to deliver 25W to a load resistors $R_L = 8\Omega$, using transformer coupling $V_m = V_{cc} = 25V$, Assume reasonable data wherever necessary. | 7M | C02 | BL |
| | b) | Briefly explain the concept of Thermal Stability. | 7M | C03 | BL |
| 5 | a) | Draw Wein Bridge Oscillator circuit diagram and then derive the expression for condition for Oscillations and Frequency of Oscillations. | 10M | C03 | BL |
| | b) | Explain why RC Phase shift oscillators are not used at high frequencies. | 4M | C03 | BL |
| 6 | a) | Explain the basic operation of small-signal single Tuned Amplifier and then derive the expression for its bandwidth. | 7M | C04 | BL |
| | b) | In what way Tuned Amplifier is different from other normal Voltage Amplifier? | 7M | C04 | BL |
| 7 | a) | Discuss the principle operation of series-fed Class-A Amplifier with the help of circuit diagram and then prove that its maximum conversion efficiency is 25%. | 7M | C04 | BL |
| | b) | What is a monostable multivibrator? Explain with the help of a neat circuit diagram the principle of operation of a monostable multivibrator. | 7M | C05 | BL |
| 8 | a) | Design a one-shot multivibrator to develop an output pulse of 140 μ s duration. Assume $h_{femin} = 20$, $i_{csat} = 6mA$, $V_{cc} = 6V$, $V_{bb} = -1.5V$ | 9M | C05 | BL |
| | b) | Discuss different methods improving linearity. | 5M | C05 | BL |