



## II B.Tech II Sem Regular End Examination, August 2021

**DIGITAL ELECTRONICS****(EEE)****Time: 3 Hours.****Max. Marks: 70**

Note: 1. Answer any FIVE questions.

2. Each question carries 14 marks and may have a, b as sub questions.

- |   |    |   |    |     |   |
|---|----|---|----|-----|---|
| 1 | a) | (i) Convert the $(1432)_8$ to decimal.  | 8M | CO1 | 1 |
|   |    | (ii) $(292)_{10} = (1204)_b$ find the value of b?   |    |     |   |
|   |    | (iii) Multiply 10100.01 and 011   |    |     |   |
|   |    | (iv) Divide 1010.1 and 101.01   |    |     |   |
|   | b) | Prove that in a self complementing code the sum of the weights must be 9.   | 6M | CO1 | 3 |
| 2 | a) | (i) Simplify the following:<br>$(x'+xyz')+(x'+xyz')(x+x'y'z)$   | 9M | CO1 | 1 |
|   |    | (ii) Prove the following:<br>$y+x'y'+x'yz=xyz'+x'y'+yz$   |    |     |   |
|   |    | (iii) simplify the following such that the resultant expression has the least number of literals: $wxyz+w'x'y'z'+w'xy'z+wx'yz'$   |    |     |   |
|   | b) | How to interface CMOS to TTL gate?  | 5M | CO1 | 2 |
| 3 | a) | Find the minimal product-of-sum expression using k-map.<br>$f(w, x, y, z) = \sum (1, 2, 6, 7, 9, 13, 14, 15)$   | 7M | CO2 | 2 |
|   | b) | Find all minimal four-variable functions that assume the value 1 when the minterms 4,10,11,13 are equal to 1, and the value 0 when the minterms 1,3,6,7,8,9,12,14 are equal to 1? | 7M | CO2 | 3 |
| 4 | a) | Design a BCD to Seven segment decoder and draw a logic diagram and explain its working.   | 7M | CO2 | 3 |
|   | b) | Write excitation table, truth table and explain function of SR flip-flop with neat logic diagram.   | 7M | CO3 | 1 |
| 5 | a) | Design a modulo-5 binary counter and write its transition and output tables and implement it using T flip-flops.  | 9M | CO3 | 3 |
|   | b) | Compare asynchronous and synchronous counters in all aspects.   | 5M | CO3 | 2 |
| 6 | a) | What is the largest value of output voltage from an 8-bit DAC that produces 1.0V for a digital input of 00110010?   | 5M | CO4 | 1 |
|   | b) | Draw the R-2R ladder circuit and explain its working.   | 9M | CO4 | 2 |

- |   |    |   |    |     |   |
|---|----|---|----|-----|---|
| 7 | a) | Explain the working of dual slope A/D converter with neat circuit diagram.                            | 9M | C04 | 2 |
|   | b) | What are the different semiconductor memory technologies and compare them.                            | 5M | C05 | 1 |
| 8 | a) | What is DRAM? What are the disadvantages of it? How to read and write operations are performed in it? | 7M | C05 | 2 |
|   | b) | Design the following function using PLAs:<br>F1= $b'c+a'bc+a'b'c'+b'c'$<br>F2= $ab'c+ab'c'+a'c'+b'c$  | 7M | C05 | 2 |

---oo0oo---