



# MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

## II B.Tech II Sem Supply End Examination, July 2022 Basic Electrical and Electronics Engineering (CIVIL & MECH)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

### PART- A

(10\*2 Marks = 20 Marks)

- |   |    |     |     |
|---|----|-----|-----|
| 1. a) State and explain KCL.                                | 2M | CO1 | BL1 |
| b) Define Peak value and RMS value.                         | 2M | CO1 | BL1 |
| c) What is MCB?   | 2M | CO2 | BL2 |
| d) What is the need of earthing?                            | 2M | CO2 | BL2 |
| e) Can DC be applied to transformers?                       | 2M | CO3 | BL1 |
| f) State Faraday's laws of electromagnetic induction.       | 2M | CO3 | BL1 |
| g) Write some applications of PN junction diode.            | 2M | CO4 | BL1 |
| h) Why Zener diode is called voltage regulator.             | 2M | CO4 | BL1 |
| i) Why an ordinary transistor is called bipolar transistor. | 2M | CO5 | BL1 |
| j) Explain about the various regions in a transistor.       | 2M | CO5 | BL4 |


### PART- B

(10\*5 Marks = 50 Marks)

- |  |    |     |     |
|--|----|-----|-----|
| 2. a) Find the RMS value for sinusoidal wave form.   | 5M | CO1 | BL3 |
| b) Derive the relation ship between line voltage and phase voltage in star connected system. | 5M | CO1 | BL6 |

OR

- |   |     |     |     |
|---|-----|-----|-----|
| 3. Find the current through 30ohms and 300 ohms resistor. | 10M | CO1 | BL3 |
|---|-----|-----|-----|

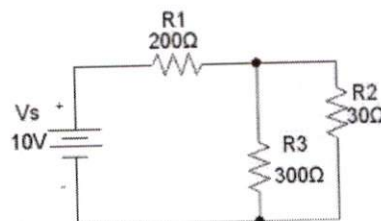

- |           |  |     |     |     |
|-----------|--|-----|-----|-----|
| 4         | a) Explain the operation of SFU.   | 5M  | C02 | BL4 |
|           | b) Explain the earthing procedure.   | 5M  | C02 | BL4 |
| <b>OR</b> |  |     |     |     |
| 5         | Explain different types of batteries.  | 10M | C02 | BL4 |
| 6         | a) Explain the principle operation of transformer.                                       | 5M  | C03 | BL4 |
|           | b) Draw the speed torque characteristics of DC series motor.                             | 5M  | C03 | BL1 |
| <b>OR</b> |  |     |     |     |
| 7         | Derive the EMF equation of DC generator.   | 10M | C03 | BL6 |
| 8         | a) Explain the VI characteristics of PN junction diode with neat diagram.                | 5M  | C04 | BL4 |
|           | b) Derive an expression for average output voltage for half wave rectifier.              | 5M  | C04 | BL4 |
| <b>OR</b> |  |     |     |     |
| 9         | What is Zener diode? Explain how voltage regulation can be achieved using Zener diode.   | 10M | C04 | BL5 |
| 10        | a) Explain the principle operation of CE amplifier.                                      | 5M  | C05 | BL2 |
|           | b) Draw the input and output characteristics of transistor in common base configuration. | 5M  | C05 | BL3 |
| <b>OR</b> |  |     |     |     |
| 11        | Discuss the working of BJT and FET.  | 10M | C05 | BL4 |

---oo0oo---