

Course Code: 1950208

Roll No:

MLRS- R19



MARRI LAXMAN REDDY
INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

III B.Tech I Sem Regular End Examination, January 2022

POWER ELECTRONICS

(EEE)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

PART- A

(10*2 Marks = 20 Marks)

- | | | | | |
|-------|--|----|-----|-----|
| 1. a) | Draw the V-I characteristics of SCR | 2M | C01 | BL1 |
| b) | How SCR is protected from high voltages | 2M | C01 | BL2 |
| c) | Define firing angle | 2M | C02 | BL1 |
| d) | How a freewheeling diode can improve the power factor | 2M | C02 | BL2 |
| e) | What is the expression of output voltage of a boost converter | 2M | C03 | BL1 |
| f) | What are the various voltage control techniques of chopper | 2M | C03 | BL1 |
| g) | Define total harmonic distortion | 2M | C04 | BL1 |
| h) | How fifth harmonic is eliminated using single pulse width modulation | 2M | C04 | BL2 |
| i) | What type of commutation is used in step down cyclo converter | 2M | C05 | BL1 |
| j) | Mention the applications of ac voltage controller | 2M | C05 | BL1 |

PART- B

(10*5 Marks = 50 Marks)

- | | | | | |
|------|--|----|-----|-----|
| 2 a) | Explain the dynamic characteristics of SCR? | 5M | C01 | BL4 |
| b) | Discuss the firing pulse generation of UJT triggering? | 5M | C01 | BL2 |

OR

- | | | | | |
|------|---|-----|-----|-----|
| 3 | Discuss load commutation and current commutation techniques | 10M | C01 | BL2 |
| 4 a) | Describe the operation of single phase full converter with R-load. | 5M | C02 | BL2 |
| b) | A single phase full converter feeds power to RLE load with R=5 ohm, L=6 mH and E=60V. The ac source voltage is 230V, 50Hz. For continuous conduction, find the average value of load current for a firing angle delay of 30°. | 5M | C02 | BL3 |

OR

5 What are the various three phase converters available and describe the operation of three phase full converter with R-load with 120° 10M C02 BL2

6 a) Explain the operation of boost converter. 5M C03 BL4

b) An RLE load is operating in a chopper circuit from 600V dc source. For a load, $L=0.06H$ and $R=5\Omega$. For a duty cycle of 0.2, Find the chopping frequency to limit the amplitude of load current excursion to 10A. 5M C03 BL3

OR

7 Obtain the steady state analysis step down chopper for RL load with neat circuit diagram. 10M C03 BL3

8 a) What are the various PWM techniques ,discuss the operation of single pulse width modulation 5M C04 BL2

b) A single phase full bridge inverter has RL load of $R=4\text{ ohm}$, $L=35mH$. The dc input voltage is 230V and output frequency is 50Hz. Find the rms value of fundamental current 5M C04 BL3

OR

9 Draw the circuit of three phase full bridge inverter and explain the operation during 180° mode of operation 10M C04 BL3

10 a) Explain the operation of single phase AC voltage controller with R-L load 5M C05 BL4

b) A single phase voltage controller feeds power to a resistive load of 3Ω from 230V, 50Hz source. Calculate the maximum value of average and rms thyristor currents for any firing angle α . 5M C05 BL3

OR

11 Explain the operation of step up and step down cyclo converter 10M C05 BL4

---oo0oo---