



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

III B.Tech I Sem Supply End Examination, July 2022

Power Electronics

(EEE)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

PART- A

(10*2 Marks = 20 Marks)

- | | | | | |
|-------|---|----|-----|-----|
| 1. a) | On state voltage drop across a thyristor used in a 230-V supply system is of the order of | 2M | C01 | BL1 |
| b) | Turn on time of an SCR in series with RL circuit can be reduced by | 2M | C01 | BL1 |
| c) | In a single phase semi converter, for continuous conduction, freewheeling diode conducts for | 2M | C02 | BL1 |
| d) | What is the expression of three phase full converter the average output voltage expression is | 2M | C02 | BL1 |
| e) | In dc chopper, per unit ripple is maximum for duty cycle α | 2M | C03 | BL1 |
| f) | A step-up chopper has V_s as the source voltage and α as the duty cycle. The output voltage for this chopper is given by | 2M | C03 | BL3 |
| g) | Draw the circuit of single phase half bridge inverter | 2M | C04 | BL1 |
| h) | What should be the pulse width in case of single pulse width modulation to eliminate third harmonic | 2M | C04 | BL3 |
| i) | Mention the applications of ac voltage controller | 2M | C05 | BL1 |
| j) | What is a cyclo converter | 2M | C05 | BL1 |

PART- B

(10*5 Marks = 50 Marks)

- | | | | | | |
|-----------|----|--|-----|-----|-----|
| 2 | a) | Explain turn on methods of SCR | 5M | C01 | BL4 |
| | b) | Explain the operation and characteristics of MOSFET | 5M | C01 | BL4 |
| OR | | | | | |
| 3 | | Discuss the various ratings and protection circuits of thyristor | 10M | C01 | BL2 |
| 4 | a) | Describe the operation of single phase half controlled converter with RLE load | 5M | C02 | BL2 |
| | b) | A single phase full converter is supplied from 230V, 50Hz source. The load consists of $R=10$ and a large inductance so as to render the load current constant. For a firing angle of delay of 30° determine average output voltage and average output current. | 5M | C02 | BL3 |

OR

5 Discuss the effect of source inductance on the performance of single phase full converter with necessary waveforms and derive the output voltage expression. 10M C02 BL2

- 6 a) Explain the operation of buck boost converter 5M C03 BL4
b) A step up chopper has input voltage of 200V and output voltage of 600V. If the non conducting time of thyristor chopper is 100 μ s, compute the pulse width of output voltage. 5M C03 BL3

OR

7 Obtain the steady state analysis of buck converter with RLE load 10M C03 BL3

- 8 a) Explain the operation of single phase bridge inverter with R-L load 5M C04 BL4
b) Explain sinusoidal pulse width modulation of single phase inverter 5M C04 BL4

OR

9 Discuss the operation of three phase full bridge inverter with 120 $^\circ$ mode of operation 10M C04 BL2

- 10 a) Explain the operation of step down cyclo converter 5M C05 BL4
b) A single phase voltage controller feeds power to a resistive load 3 Ω from 230V, 50Hz source. Calculate the maximum values of average and rms thyristor currents for any firing angle α 5M C05 BL3

OR

11 Discuss the operation of single phase ac voltage controller with R and RL loads 10M C05 BL2

---0000---