



# MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi &amp; Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade &amp; Recognized Under Section 2(f) &amp; 12(B) of the UGC act, 1956

## III B.Tech I SEM Regular End Examination, January 2022

### Measurements and Instrumentation

(EEE)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

#### PART- A

(10\*2 Marks = 20 Marks)

- |       |   |     |     |
|-------|---|-----|-----|
| 1. a) | Why do we use a multiplier with a voltmeter?  | C01 | BL1 |
| b)    | Why is damping required for an electromechanical measuring instrument?  | C01 | BL1 |
| c)    | Why is secondary of a CT is never left open circuited?  | C02 | BL1 |
| d)    | A potentiometer is standardized using a known voltage of 2V by keeping the slide wire at 50cm position of the scale. The total length of the scale is 2meters. Find the unknown battery voltage which is balanced at 150cm. | C02 | BL3 |
| e)    | What is creeping error? How is it prevented.  | C03 | BL1 |
| f)    | What is meant by phantom loading?   | C03 | BL1 |
| g)    | Draw a suitable AC bridge used for measurement of frequency.  | C04 | BL1 |
| h)    | Why Maxwell bridge is limited to the measurement of medium-Q coils?   | C04 | BL1 |
| i)    | Define gauge factor of a strain gauges. How is related to positions ratio $\mu$ .   | C05 | BL1 |
| j)    | What do you mean by active and passive transducer? Give suitable examples.  | C05 | BL1 |

#### PART- B

(10\*5 Marks = 50 Marks)

- |       |   |    |     |     |
|-------|---|----|-----|-----|
| 2. a) | Explain the construction and working of an attracted disc type Kelvin absolute electrometer | 5M | C01 | BL4 |
| b)    | Derive the expression for the Extension range of ammeter and series voltmeter.              | 5M | C01 | BL4 |

OR

- |       |   |     |     |     |
|-------|---|-----|-----|-----|
| 3.    | Describe the constructional details and working of a moving iron attraction type meter. Derive its torque equation. Draw the relevant figures.  | 10M | C01 | BL2 |
| 4. a) | Draw the circuit diagram of Crompton's D.C potentiometer and explain the principle of operation.  | 5M  | C02 | BL4 |
| b)    | A Maxwell's capacitance bridge is used to measure an unknown inductance in comparison with capacitance. The various values at balance $R_2=400\Omega$ , $R_3=600\Omega$ , $R_4=1000\Omega$ , $C_2=0.5\mu F$ . Calculate the | 5M  | C02 | BL3 |

values of  $R_1$  &  $L_1$  and also calculate the value of storage factor(Q) of coil frequency is 1000Hz.

**OR**

5 Draw the equivalent circuit and phasor diagram of a potential transformer and derive the expression for actual transformation ratio and phase angle. 10M C02 BL4

6 a) Explain how power in high voltage circuits is measured using instrument transformer? 5M C03 BL4

b) A single phase energy meter makes 500 revolutions per kwh. It is found on testing as making 40 revolutions in 58.1 sec at 5 kw full load. Find out the percentage error. 5M C03 BL3

**OR**

7 Derive the torque equation for an electrodynamicometer type wattmeter and write its working principle and operation. 10M C03 BL6

8 a) Describe in brief the different methods used for measurement of medium resistance. 5M C04 BL2

b) Describe how relative permittivity of a specimen of insulating material can be determined using a Schering bridge. 5M C04 BL2

**OR**

9 Explain the working of Hay's bridge for measurement of inductance with a circuit diagram. Derive equation for balance and draw the phasor diagram under balance condition. 10M C04 BL4

10 a) What are the differences between thermocouple and thermistor? 5M C05 BL2

b) Explain the input and output characteristics of transducers? 5M C05 BL4

**OR**

11 Define strain gauge. Classify and explain electrical strain gauges. 10M C05 BL4

---oo0oo---