



I B.Tech II Sem Regular End Examination, September 2021

Basic Electrical Engineering

(EEE)


Time: 3 Hours.

Max. Marks: 70


Note: 1. Answer any FIVE questions.

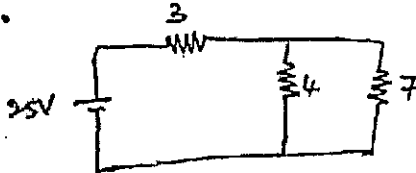2. Each question carries 14 marks and may have a, b as sub questions.

- 1 a) Define the electrical circuit elements. 7M CO1 BL1
 b) For the circuit as shown in following figure, calculate the current in the various branches? (All resistances are in ohms). 7M CO1 BL3



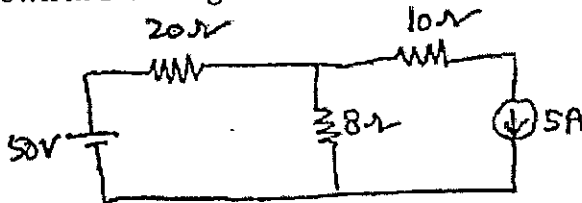- 2 a) Using superposition theorem, find the current through the 8 Ω resistor, as shown in below figure. 7M CO1 BL3



- b) Define and give symbols of the following: 7M CO1 BL1
 i) Dependent sources
 ii) Independent Sources
 iii) Practical Sources
 iv) Ideal Sources
- 3 a) Derive the expressions for average value, RMS value and form factor for a sinusoidal wave form. 7M CO2 BL3
 b) Derive the relation between line and phase quantities of voltage and current for a star system. 7M CO2 BL3
- 4 a) Illustrate following terms: i) Impedance ii) Reactance iii) Phase deference iv) Power factor. 7M CO2 BL3
 b) Explain the operation of an auto transformer with a neat diagram. 7M CO3 BL2
- 5 a) From the fundamentals, derive the expression for the EMF equation of a single phase transformer. 7M CO3 BL3
 b) A 50 kVA, single phase transformer has 500 turns on the primary and 200 turns on the secondary. The primary is connected to 2000V, 50 Hz Supply. Determine: i) The secondary voltage and ii) The maximum value of flux. 7M CO3 BL3

- | | | | | |
|---|--------------------------------------------------------------------------------------------------------------------------------|----|-----|-----|
| 6 | a) Explain the principle of operation of 3-Phase induction Motor. | 7M | CO4 | BL2 |
| | b) A 10-pole, 3-phase induction motor runs at a speed of 485 rpm at 50 Hz supply. Determine i) synchronous speed and ii) slip. | 7M | CO4 | BL3 |
| 7 | a) Describe the torque speed characteristics of separately excited dc motor. | 7M | CO4 | BL2 |
| | b) What is the difference between MCB and MCCB, describe their schematic diagrams? | 7M | CO5 | BL4 |
| 8 | a) What are the different types of wires and cables? Explain. | 7M | CO5 | BL2 |
| | b) What is the purpose of earthing? Write the advantages of earthing? | 7M | CO5 | BL1 |

---oo0oo---