



I B.Tech II Sem Supply End Examination, March 2022

Basic Electrical Engineering

(EEE)


Time: 3 Hours.

Max. Marks: 70

Note: 1. Answer any FIVE questions.


2. Each question carries 14 marks and may have a, b as sub questions.

1 a) Explain the Kirchoff's current and voltage laws. 7M CO1 BL2

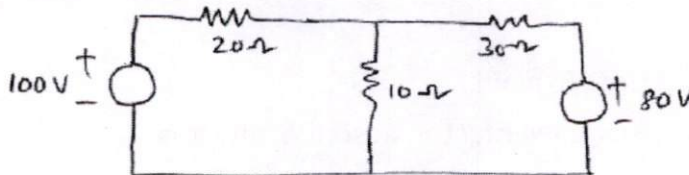b) Find the current in the 10Ω resistance of the following circuit shown in figure. 7M CO1 BL3

2 a) State and explain superposition theorem with an example. 7M CO1 BL2

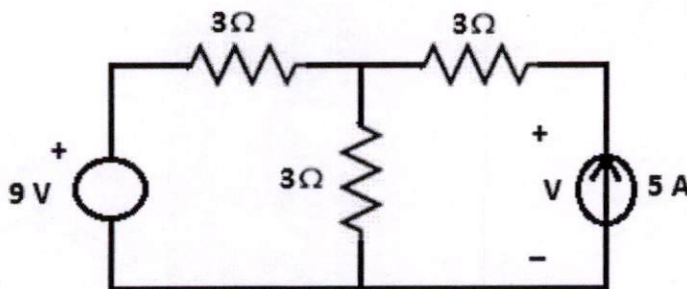b) In the circuit shown in figure, determine 'V' using Thevenin's theorem 7M CO1 BL3



3 a) Define the following terms: 7M CO2 BL1

i) Frequency

ii) Peak factor

iii) Form factor

iv) Average value of an alternating quantity.

b) Describe phasor representation of RL,RC series circuits? 7M CO2 BL2

4 a) Derive the relation between line and phase quantities of voltage and current for a delta system. 7M CO2 BL3

b) With the help of diagram explain the principle of operation of transformer. 7M CO3 BL2

- | | | | | | |
|---|----|---|----|-----|-----|
| 5 | a) | Define and explain efficiency and regulation of a transformer. | 7M | C03 | BL2 |
| | b) | Discuss the various three phase transformer connections with diagrams. | 7M | C03 | BL2 |
| 6 | a) | Explain the principle of production of rotating magnetic field in a 3-phase induction Motor. | 7M | C04 | BL2 |
| | b) | Analyze the torque -slip characteristics vary with the variation in input voltage of induction motor? | 7M | C04 | BL3 |
| 7 | a) | Explain the working principle of synchronous generator. | 7M | C04 | BL2 |
| | b) | Calculate total energy consumed per day by the use of following loads:
i) 5 number of 40 W lights operated 5 hours per day
ii) 1 h.p. motor is operated 2 hours per day
iii) 1 k.W heater is operated 1 hour per day
iv) 1 computer 150W is used for 6 hours per day with printer about 30 minutes. | 7M | C05 | BL3 |
| 8 | a) | What are the types of batteries? Explain. | 7M | C05 | BL2 |
| | b) | What are the drawbacks of low power factor, describe how it is improved? | 7M | C05 | BL2 |

---oo0oo---