



# MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

II B.Tech I Sem Regular End Examination, February-2022

**Basic Electrical and Electronics Engineering**

**(CIVIL & MECH)**

**Time: 3 Hours.**

**Max. Marks: 70**

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part – A, answer all questions which carries 20 marks.

3. In Part – B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

### PART- A

**(10\*2 Marks = 20 Marks)**

- |       |   |    |     |     |
|-------|---|----|-----|-----|
| 1. a) | State KCL.  | 2M | CO1 | BL1 |
| b)    | Define active power.  | 2M | CO1 | BL1 |
| c)    | What is the function of MCCB?   | 2M | CO2 | BL1 |
| d)    | Why do you require earthing?  | 2M | CO2 | BL1 |
| e)    | State various losses of a transformer.  | 2M | CO3 | BL1 |
| f)    | State the various parts of 3-phase Induction Motor.                             | 2M | CO3 | BL1 |
| g)    | Define ripple factor of a Half wave rectifier and mention its value.            | 2M | CO4 | BL1 |
| h)    | Draw the circuit diagram of a PN junction diode under forward biased condition. | 2M | CO4 | BL1 |
| i)    | Draw the circuit diagram of CB configuration of BJT.                            | 2M | CO5 | BL1 |
| j)    | Draw the symbol of FET and Identify its terminals.                              | 2M | CO5 | BL1 |

### PART- B

**(10\*5 Marks = 50 Marks)**

- |   |    |   |    |     |     |
|---|----|---|----|-----|-----|
| 2 | a) | Determine the power factor and the input power for a circuit with $v = 50 \sin (t+10^\circ)$ and $I = 2 \sin (t+20^\circ)$ A  | 5M | CO1 | BL3 |
|   | b) | A series circuit consists of $20\Omega$ resistance and inductance of 50mH is connected in series with a single phase AC voltage source of 230V with frequency of 50Hz. Calculate impedance, current, resistive voltage drop, inductive drop | 5M | CO1 | BL3 |

**OR**

- |   |    |   |     |     |     |
|---|----|---|-----|-----|-----|
| 3 |    | Obtain the relation between line and phase quantities of a 3-phase star connected balanced load connected to a balanced 3-phase supply. | 10M | CO1 | BL3 |
| 4 | a) | What is a cable? Explain various types of cables used in electrical installations.  | 5M  | CO2 | BL4 |
|   | b) | Draw the schematic of ELCB. Explain its working.  | 5M  | CO2 | BL2 |

**OR**

- |   |  |     |     |     |
|---|--|-----|-----|-----|
| 5 | Explain different types of batteries with their characteristics. | 10M | CO2 | BL4 |
| 6 | a) Derive the torque equation of a d.c motor.                    | 5M  | CO3 | BL6 |
|   | b) Explain the working principle of a d.c generator.             | 5M  | CO3 | BL4 |

**OR**

- |   |  |     |     |     |
|---|--|-----|-----|-----|
| 7 | Obtain the equivalent circuit of a single phase transformer.   | 10M | CO3 | BL3 |
| 8 | a) Draw the V-I characteristics of a P-N junction diode. Explain in brief.   | 5M  | CO4 | BL4 |
|   | b) In a bridge rectifier circuit the peak value of secondary voltage is $230\sqrt{2}$ V and frequency is 50Hz. Determine the (i) no-load output dc voltage (ii) PIV and (iii) output frequency | 5M  | CO4 | BL3 |

**OR**

- |    |  |     |     |     |
|----|--|-----|-----|-----|
| 9  | What is filter? Explain the working of different filters used in power supplies. | 10M | CO4 | BL4 |
| 10 | a) Sketch typical CC configuration of an PNP transistor. Label all variables.    | 5M  | CO5 | BL2 |
|    | b) Compare CB and CE configuration of a BJT.                                     | 5M  | CO5 | BL2 |

**OR**

- |    |  |     |     |     |
|----|--|-----|-----|-----|
| 11 | Explain the construction and working of FET with a neat diagram. | 10M | CO5 | BL4 |
|----|--|-----|-----|-----|

---oo0oo---