



II B.Tech I Sem Supply End Examination, July-2022
Network Analysis
(EEE)


Max. Marks: 70

- Note: 1. Question paper consists: Part-A and Part-B.
 2. In Part - A, answer all questions which carries 20 marks.
 3. In Part - B, answer any one question from each unit.
 Each question carries 10 marks and may have a, b as sub questions.


PART- A

(10*2 Marks = 20 Marks)

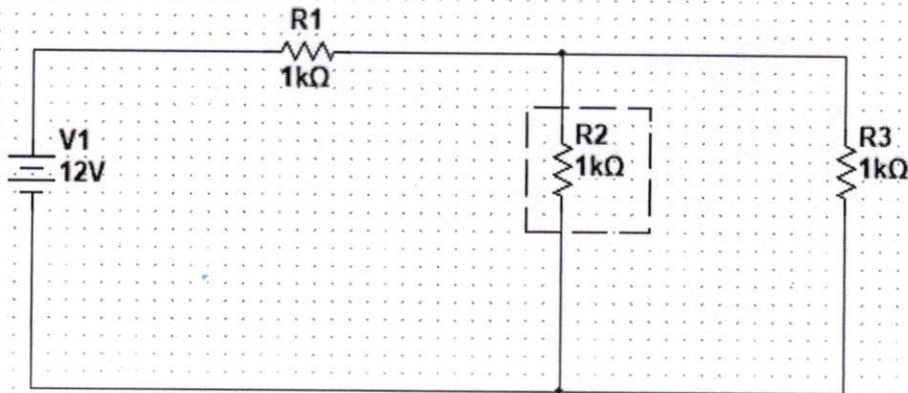1. a) Explain the Mesh analysis and determine the voltage (V_{R3}) in the given circuit 2M C01 BL-5



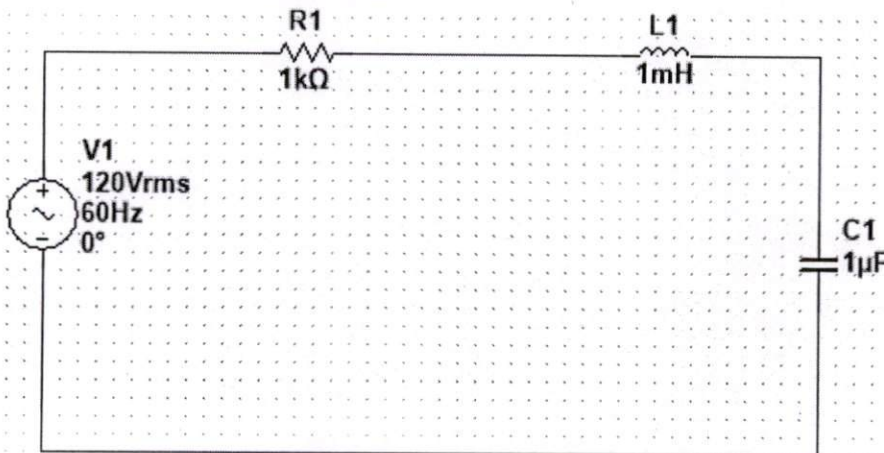- b) Design the dual of the network 2M C01 BL-6




- c) Explain the phasor relationship in Series RL and series RC circuit? 2M C02 BL-2
 d) Compare the difference between steady state and transient state analysis ? 2M C02 BL-5
 e) Define the Ideal transformer with neat sketch? 2M C03 BL-1
 f) Explain the three phase circuits? 2M C03 BL-2
 g) Illustrate the pole & zero in a transfer function? 2M C04 BL-2

h)


2M CO4 BL-5

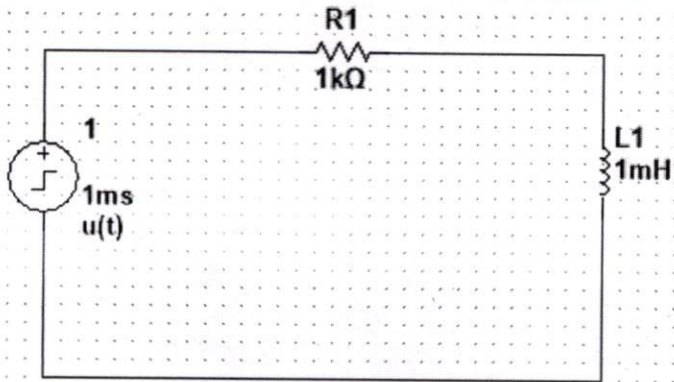Determine the transfer function using Laplace transform




i) Determine the Z-parameters of the given two-port networks are connected in series

2M CO5 BL-5

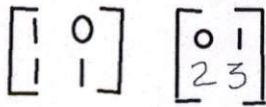

j) Evaluate the Y-parameters for the following circuit

2M CO5 BL-5

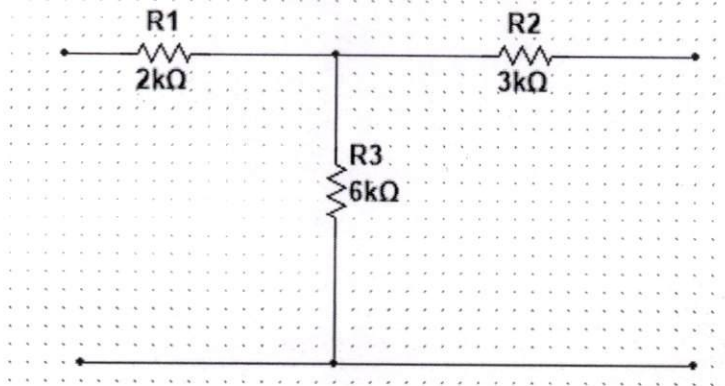


PART- B

(10*5 Marks = 50 Marks)

2 a) Define the Telligence theorem and determine power across 2v using Telligence theorem


5M CO1 BL-1 & BL-6

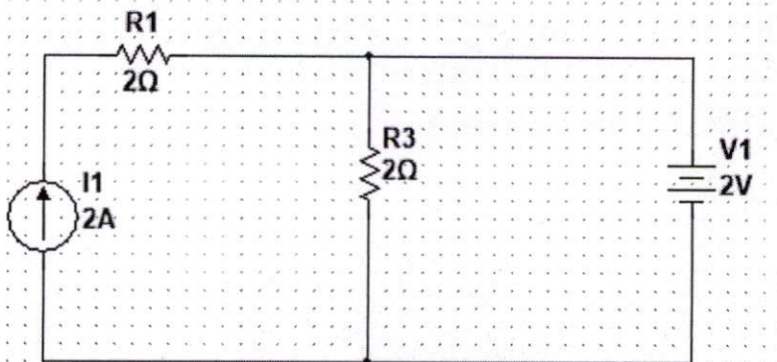

b)

5M C01 BL-6

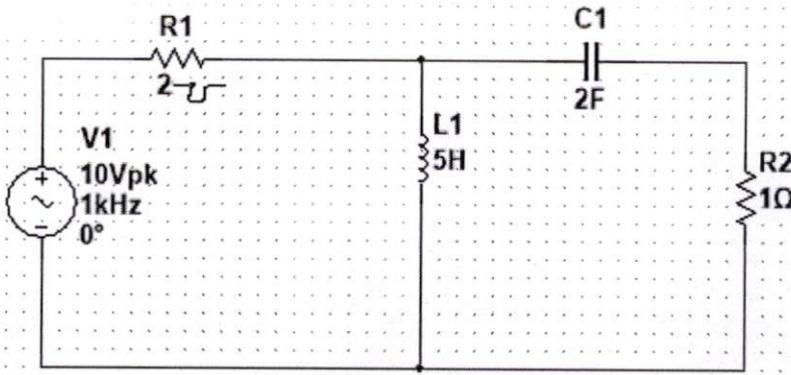
Design the dual of the network and determine the voltage across the 1ohm resistor?



OR

3 Determine the V_{pq}

10M C01 BL-5

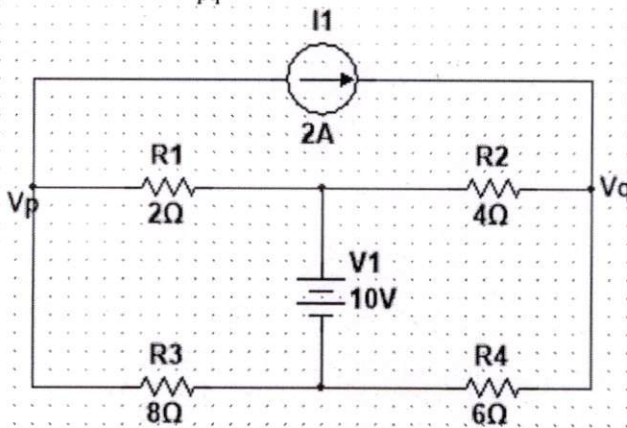

4 a) Develop the complete response first order Differential Equation for step input in series RLC circuit

5M C02 BL-3


b) What is time constant? What are the time constants of series RL and RC circuits?

5M C02 BL-1

OR

5 In the below circuit is the switch for a long time and It is opened at $t=0$. Determine the $I_1(t)$, $V_1(0+)$?

10M C02 BL-5

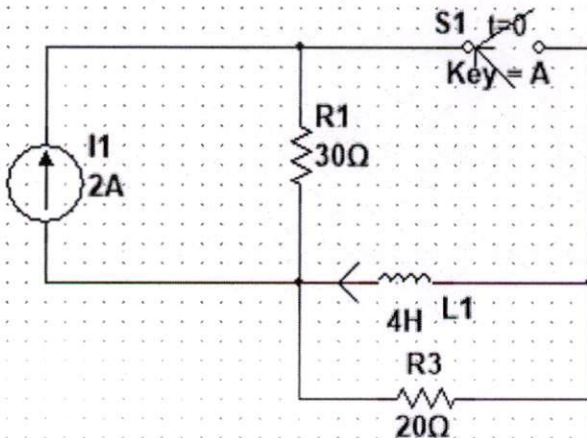

- 6 a) Determine the resonance ,Bandwidth for parallel RLC circuit 5M C03 BL-5
 b) Explain briefly about 5M C03 BL-2
 i) Mutual inductance
 ii) Dot convention method
 iii) Self inductance


OR

- 7 A Series RLC circuit has $R=10\text{ohm}$, $L=0.5\text{H}$, $C=4\text{uf}$ & $V(t)=100\text{v}$. 10M C03 BL-5
 Using above data determine the i) Quality factor
 ii) upper & lower half power frequencies
 iii) V across the load
 iv) Voltage across capacitor


- 8 a) Design the transfer function $I(s)$ in series RL circuit using Laplace 5M C04 BL-6
 transform with the given input is $V\sin(\omega t)$
 b) Evaluate the 2nd order series RLC using Laplace transform 5M C04 BL-5

OR

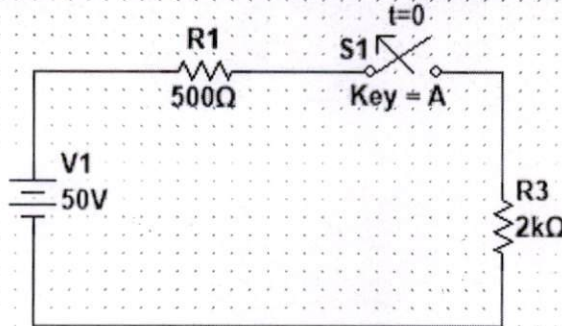- 9 In the given circuit the switch is closed for a long time and it is 10M C04 BL-5
 opened at $t=0$. determine the initial and final value conditions



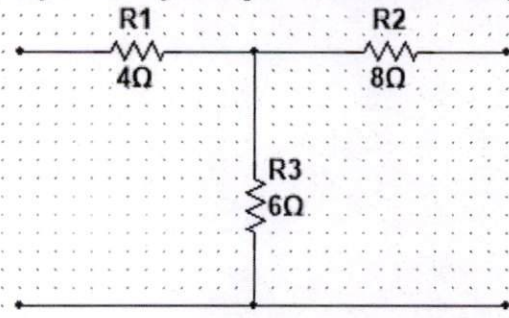- 10 a) Analyze the hybrid parameters for the given circuit 5M C05 BL-4



- b) Justify the interrelation between the Z parameters in terms of T 5M C05 BL-5
 parameters

OR

- 11 Explain the symmetrical, reciprocal two port network and Evaluate 10M C05 BL-5
 the Z-parameters for following network

