



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

II B.Tech I Sem Supply End Examination, July-2022

Basic Electrical and Electronics Engineering

(CIVIL, MECH)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

PART- A

(10*2 Marks = 20 Marks)

- | | | | |
|---|----|-----|-----|
| 1. a) State KVL. | 2M | C01 | BL1 |
| b) Define reactive power. | 2M | C01 | BL1 |
| c) What is the function of switch fuse unit (SFU)? | 2M | C02 | BL1 |
| d) State different types of wires used in houses. | 2M | C02 | BL1 |
| e) Define efficiency of a transformer. | 2M | C03 | BL1 |
| f) State the different parts of a d.c motor. | 2M | C03 | BL1 |
| g) Give the applications of a Zener Diode. | 2M | C04 | BL1 |
| h) What is the need for a filter? | 2M | C04 | BL1 |
| i) Draw the circuit diagram of CC configuration of BJT. | 2M | C05 | BL1 |
| j) What is the difference between BJT and FET in any two aspects? | 2M | C05 | BL1 |

PART- B


(10*5 Marks = 50 Marks)

- | | | | |
|---|----|-----|-----|
| 2 a) Explain various voltage and current sources. | 5M | C01 | BL4 |
| b) Explain the following: (i) R.M.S. value (ii) Average value and (iii) Form Factor of a sinusoidal quantity. | 5M | C01 | BL4 |

OR

- | | | | |
|---|-----|-----|-----|
| 3 | 10M | C01 | BL3 |
|---|-----|-----|-----|

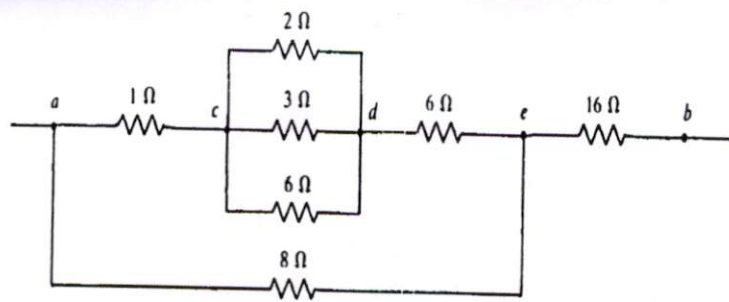Find the equivalent resistance across the terminals of 'a' and 'b' of the circuit shown below. Also, calculate the total current and each current flowing through each resistance, if 230V battery is connected across the terminals "a" and "b".



- 4 a) What is the need for power factor improvement? Explain. 5M C02 BL4
 b) State various types of earthing methods. Explain any one of them. 5M C02 BL4
- OR**
- 5 Explain the working principle of MCCB with a neat sketch. 10M C02 BL4
- 6 a) Derive the e.m.f equation of a single phase transformer. 5M C03 BL6
 b) Explain the speed control methods of D.C motor. 5M C03 BL4
- OR**
- 7 Explain the construction and working principle of 3-phase Induction motor. 10M C03 BL4
- 8 a) Draw and explain Volt-ampere characteristics of P-N junction diode. 5M C04 BL4
 b) Draw the equivalent circuit of a PN junction diode. 5M C04 BL1
- OR**
- 9 Draw the circuit diagram of a full-wave bridge rectifier circuit. Explain its working with waveforms. 10M C04 BL4
- 10 a) What is biasing of a transistor? Explain. 5M C05 BL4
 b) Compare CB, CC and CE configurations of a BJT. 5M C05 BL2
- OR**
- 11 Draw the typical CE configuration of an NPN transistor. Label all variables. Also, explain its working. 10M C05 BL4

---oo0oo---