



II B.Tech II Sem Regular End Examination, July 2022

Basic Electrical Engineering
(CSC, CSD, CSE, CSI, CSM, IT)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

PART- A


(10*2 Marks = 20 Marks)

- | | | | | |
|-------|---|----|-----|-----|
| 1. a) | State Kirchhoff's voltage law. | 2M | CO1 | BL1 |
| b) | Define the following: Junction point and Branch. | 2M | CO1 | BL1 |
| c) | Define: RMS and Average value. | 2M | CO2 | BL1 |
| d) | Write the relations of Voltages and Currents of a Three phase star connections. | 2M | CO2 | BL2 |
| e) | Write the e.m.f equation of a transformer and brief the terms in the equation. | 2M | CO3 | BL2 |
| f) | Explain the working principle of auto transformer. | 2M | CO3 | BL4 |
| g) | Explain the working principle of three phase Induction motor. | 2M | CO4 | BL4 |
| h) | Brief the torque speed characteristics of single-phase induction motor. | 2M | CO4 | BL2 |
| i) | Define earthing and brief its importance. | 2M | CO5 | BL1 |
| j) | List the types of batteries. | 2M | CO5 | BL1 |

PART- B

(10*5 Marks = 50 Marks)

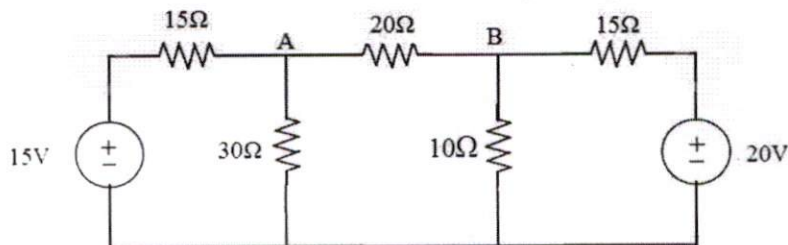- 2 a) Determine the current in branch A-B by using KVL 5M CO1 BL3




- b) State and explain Thevenin's theorem. 5M CO1 BL1

OR

- 3 Use KCL to find node voltages for the circuit shown below.

10M C01 BL3

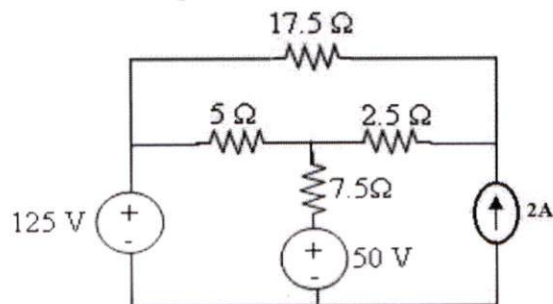

- 4 a) Derive an expression for RMS values of sine wave form.

5M C02 BL6

- b) Define power factor, apparent power, active power and reactive power

5M C02 BL1

OR

- 5 Derive an expression for the current and impedance for a series RL and RC circuit excited by a Sinusoidally alternating voltage. Draw the phasor diagrams.

10M C02 BL3

- 6 a) Draw the constructional diagram of a single-phase transformer and explain all the parts.

5M C03 BL2

- b) Write the short notes on Voltage Regulation & Efficiency.

5M C03 BL1

OR

- 7 Draw the constructional diagram of auto transformer and three-phase transformer connections and explain all the parts.

10M C03 BL4

- 8 a) Explain squirrel cage type Rotor of induction motor briefly.

5M C04 BL4

- b) Derive the emf equation of an alternator

5M C04 BL6

OR

- 9 Derive the conditions for maximum torque for 3-phase induction motor under (i) Starting condition (ii) Under running condition.

10M C04 BL6

- 10 a) Define Wiring system & list the types of wiring systems.

5M C05 BL1

- b) Compare Fuse & Circuit breaker based on various aspects.

5M C05 BL2

OR

- 11 With neat diagrams, explain various types of earthing used in electrical systems.

10M C05 BL4