



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

II B.Tech II Sem Regular End Examination, July 2022

Digital System Design

(ECE)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

PART- A

(10*2 Marks = 20 Marks)

- | | | | | |
|-------|-------------------------------------------------------------------------------|----|-----|-----|
| 1. a) | Perform the operation $21_{(10)} - 42_{(10)}$ by using 2's complement method. | 2M | C01 | BL3 |
| b) | Convert the number $(125F)_{16}$ to Decimal and then to octal. | 2M | C01 | BL3 |
| c) | Find the complement of $F=WX+YZ$ then show that $FF'=0$ and $F+F'=1$. | 2M | C02 | BL3 |
| d) | Implement the function with only NAND gates: $F(x,y,z) = \Sigma(0,6)$. | 2M | C02 | BL5 |
| e) | Compare Latch and Flip-Flop. | 2M | C03 | BL2 |
| f) | Differentiate combinational and sequential circuits. | 2M | C03 | BL2 |
| g) | Define: i) State table ii) State Diagram. | 2M | C04 | BL1 |
| h) | What is ring counter? | 2M | C04 | BL1 |
| i) | Compare Mealy and Moore machines. | 2M | C05 | BL2 |
| j) | What is an ASM Block? | 2M | C05 | BL1 |

PART- B

(10*5 Marks = 50 Marks)

- | | | | | |
|------|-------------------------------------------------------------------------|----|-----|-----|
| 2 a) | i) Convert the given Octal number $(2564.603)_8$ to Hexadecimal number. | 5M | C01 | BL3 |
| | ii) Given that $(81)_{10} = (100)_b$, Find the value of b. | | | |
| b) | Encode data bits 1101 into 7 bit even parity Hamming Code | 5M | C01 | BL4 |

OR

- | | | | | |
|------|-----------------------------------------------------------------------------------------------------------------|-----|-----|-----|
| 3 | Generate Hamming code for the given 11 bit message 10001110101 and rewrite the entire message with hamming code | 10M | C01 | BL3 |
| 4 a) | Design the full adder circuit using two half adder circuits. | 5M | C02 | BL6 |
| b) | Realize the expression $F = \Sigma m(0,1,3,5,8,11,12,14,15)$ using 8×1 MUX. | 5M | C02 | BL4 |

OR

- | | | | | |
|---|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|-----|-----|
| 5 | For the given function $F(A, B, C, D, E) = \Sigma(0,1, 2, 3, 4, 5, 9, 10, 16, 17, 18, 19, 20, 22, 25, 26) + \Sigma d(7, 11, 12, 13, 15, 23, 27, 28, 29, 30)$. Obtain minimal SOP expression using K-Map. | 10M | C02 | BL3 |
|---|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-----|-----|-----|

- 6 a) With the block diagram, Truth table, describe the principle operation of edge triggered negative SR flip flop. 5M C03 BL2
b) With a neat diagram, explain operation of T flip-flop and derive its truth table, characteristic equation and excitation table. 5M C03 BL4
- OR**
- 7 With a neat circuit diagram and waveforms, explain the operation of Master Slave JK flip flop. 10M C03 BL4
- 8 a) Draw a state diagram of a sequence detector which can detect 101 5M C04 BL1
b) Design a parity-bit generator circuit with neat diagrams. 5M C04 BL6
- OR**
- 9 Design a 4 bit ring counter with initial count 1100 loaded in it. Prepare a state table and draw the state diagram including those of unused states and also the output waveforms 10M C04 BL6
- 10 a) What are the Moore and Melay machines? Compare them. 5M C05 BL2
b) Write about PLD in detail. 5M C05 BL1
- OR**
- 11 Implement PLA circuit for full-adder circuit. 10M C05 BL5

---oo0oo---