



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

II B.Tech II Sem Regular End Examination, July 2022

Digital Electronics and IC Applications

(EEE)

Time: 3 Hours.

Max. Marks: 70

Note: 1. Question paper consists: Part-A and Part-B.

2. In Part - A, answer all questions which carries 20 marks.

3. In Part - B, answer any one question from each unit.

Each question carries 10 marks and may have a, b as sub questions.

PART- A

(10*2 Marks = 20 Marks)

- | | | | | |
|-------|--|----|-----|-----|
| 1. a) | Convert the hexadecimal number E3FA to binary | 2M | CO1 | BL3 |
| b) | Simplify using Demorgan's theorems to $(A+BC)'$. | 2M | CO1 | BL3 |
| c) | Design Half adder using NAND gate | 2M | CO2 | BL6 |
| d) | Design a 2-bit comparator using logic gates | 2M | CO2 | BL6 |
| e) | Difference between combinational and sequential circuits | 2M | CO3 | BL2 |
| f) | Write the applications of shift register | 2M | CO3 | BL1 |
| g) | Write down the drawback of weighted resistor type D/A converter. | 2M | CO4 | BL1 |
| h) | What are the advantages and disadvantages of R-2R ladder DAC? | 2M | CO4 | BL1 |
| i) | Explain what are the two basic modes in which 555 timer operates | 2M | CO5 | BL4 |
| j) | List the applications of 555 timer | 2M | CO5 | BL1 |

PART- B

(10*5 Marks = 50 Marks)

- | | | | | |
|-----------|---|-----|-----|-----|
| 2 a) | Implement AND gate using NAND and NOR. | 5M | CO1 | BL5 |
| b) | Simplify the following Boolean expression $A'C'+ABC+AC'$ | 5M | CO1 | BL3 |
| OR | | | | |
| 3 | Explain with examples Error Detecting and Correcting Codes. | 10M | CO1 | BL4 |
| 4 a) | Simplify the following Boolean function using K-Map
$F(w,x,y,z)=\sum(1,4,5,6,12,14,15)$ | 5M | CO2 | BL3 |
| b) | Simplify the following Boolean function using K-Map
$F(A,B,C,D)=\pi(1,3,5,7,13,15)$ | 5M | CO2 | BL3 |
| OR | | | | |
| 5 | Simplify the following Boolean function using Tabulation method
$F(w,x,y,z)=\sum(0,1,2,8,10,11,14,15)$ | 10M | CO2 | BL3 |

- 6 a) What is race around condition? How it is avoided? 5M C03 BL1
b) Explain about the ring and twisted ring counter 5M C03 BL4
- OR**
- 7 Design a Mod-5 synchronous counter 10M C03 BL6
- 8 a) Explain about the Successive Approximation ADC 5M C04 BL4
b) With circuit diagram, explain the operation of a dual slope A/D Converter. 5M C04 BL4
- OR**
- 9 What are the limitations in weighted resistor type D/A converters and explain how this problem can solve in R-2R ladder type D/A converters 10M C04 BL4
- 10 a) Explain about the analysis of 1st order LPF Butterworth Filter 5M C05 BL4
b) Write about the Monostable multivibrator 5M C05 BL1
- OR**
- 11 Explain in detail how would you obtain a square wave in 555 timer 10M C05 BL4

---oo0oo---