



MARRI LAXMAN REDDY
INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

LABORATORY MANUAL

ELECTRONIC CIRCUITS LAB

II B. TECH -II SEMESTER (ECE)

MLRS-R24 REGULATION



AY-2025-2026

**Prepared by
Lab In-charge:**

**Mr. G. Siva Sankar Varma
Mrs. CH. Krishnaveni
Mrs. R. Anuja**

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

CERTIFICATE

This is to certify that this manual is a bonafide record of practical work in the *Electronic Circuits Laboratory* in **Second Semester of II-Year B. Tech (ECE) Programme** during the academic year **2025-2026**. This book is prepared by **Mr. G. Siva Sankar Varma (Assistant Professor)**, **Mrs. CH. Krishnaveni (Assistant Professor)** and **Mrs. R. Anuja (Assistant Professor)** Department of Electronics and Communication Engineering.

Lab I/C

Head of the Department

PREFACE

This laboratory lays the foundation for the Electronics and Communication Engineering students during second year of their course.

Circuits and components of EC Lab can be divided into two batches: Hardware & Software. In Hardware lab, the students design, construct and test the working of analog circuits such as transistor amplifiers, and oscillators and also pulse circuits like multivibrators and Time Base generators. In Software, the students will execute verify the outputs of few experiments using Multisim software. After performing all the experiments included in this Laboratory, it is hoped the student receives good training to handle any electronic equipment available in electronics field.

Basic electronic equipment used in electronics laboratory

- Cathode Ray Oscilloscope to view and measure AC waveforms.
- Function Generator used to design, develop and to trouble shoot electronic equipments
- Regulated power supply to supply DC voltage to electronic circuits.
- Breadboard to mount the components temporarily for experimental work.

By,

**Mr. G. SIVA SANKAR VARMA,
Mrs. CH. KRISHNAVENI,
Mrs. R. ANUJA**

ACKNOWLEDGEMENT

It was really a good experience, working with *Electronic Circuits* lab. First we would like to thank **Dr. Srinivas Nallagonda, Professor, HOD** of Department of Electronics and Communication Engineering, Marri Laxman Reddy Institute of technology & Management for his concern and giving the technical support in preparing the document.

We are deeply indebted and gratefully acknowledge the constant support and valuable patronage of **Dr. Ravi Prasad, Dean Academics**, Marri Laxman Reddy Institute of technology & Management for giving us this wonderful opportunity for preparing the with *Electronic Circuits* laboratory manual.

We express our hearty thanks to **Dr. R. Murali Prasad, Principal**, Marri Laxman Reddy Institute of Technology and Management for timely corrections and scholarly guidance.

We wish to express deepest gratitude and thanks to **Dr. P. Sridhar, Director**, Marri Laxman Reddy Institute of Technology and Management, for his constant support and encouragement in providing all the facilities in the college.

At last, but not the least I would like to thanks the entire ECE Department faculty those who had inspired and helped us to achieve our goal.

By,

**G. SIVA SANKAR VARMA,
R. KIRAN**

GENERAL INSTRUCTIONS

1. Students are instructed to come to *Electronic Circuits* laboratory on time. Late comers are not entertained in the lab.
2. Students should be punctual to the lab. If not, the conducted experiments will not be repeated.
3. Students are expected to come prepared at home with the experiments which are going to be performed.
4. Students are instructed to display their identity cards before entering into the lab.
5. Students are instructed not to bring mobile phones to the lab.
6. Any damage/loss of equipments like transformers, transistors, CRO's etc., during the lab session, it is student's responsibility and penalty or fine will be collected from the student.
7. Students should update the records and lab observation books session wise. Before leaving the lab the student should get his lab observation book signed by the faculty.
8. Students should submit the lab records by the next lab to the concerned faculty members in the staffroom for their correction and return.
9. Students should not move around the lab during the lab session.
10. If any emergency arises, the student should take the permission from faculty member concerned in written format.
11. The faculty members may suspend any student from the lab session on disciplinary grounds.
12. Never copy the output from other students. Write down your own outputs.

Vision of the Institute

To be a globally recognized institution that fosters innovation, excellence, and leadership in education, research, and technology development, empowering students to create sustainable solutions for the advancement of society.

Mission of the Institute

To foster a transformative learning environment that empowers students to excel in engineering, innovation, and leadership.

To produce skilled, ethical, and socially responsible engineers who contribute to sustainable technological advancements and address global challenges.

To shape future leaders through cutting-edge research, industry collaboration, and community engagement.

Quality Policy

The management is committed in assuring quality service to all its stakeholders, students, parents, alumni, employees, employers, and the community.

Our commitment and dedication are built into our policy of continual quality improvement by establishing and implementing mechanisms and modalities ensuring accountability at all levels, transparency in procedures, and access to information and actions.

Vision of the Department

To provide quality technical education in Electronics and Communication Engineering through research, innovation, striving for global recognition in specified domain, leadership, and sustainable societal solutions.

Mission of the Department

- **DM1:** To create a transformative learning environment that empowers students in electronics and communication engineering, fostering excellence in technical skills and leadership.
- **DM2:** To drive innovation through research, deliver a transformative education grounded in ethical principles, and nurture the development of professionals
- **DM3:** To cultivate strong industry partnerships, and engaging actively with the community for societal and technological progress.

Program Educational Objectives (PEO)

PEO 1: Have successful careers in Industry.

PEO 2: Show excellence in higher studies/ Research.

PEO 3: Show good competency towards Entrepreneurship.

Program Outcomes (POs)

Engineering Graduates will be able to:

1. **Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
2. **Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
3. **Design/development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate

consideration for the public health and safety, and the cultural, societal, and environmental considerations.

4. **Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.

5. **Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.

6. **The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.

7. **Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.

8. **Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.

9. **Individual and team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.

10. **Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.

11. **Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.

12. **Life-long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

Program Specific Outcomes (PSOs)

1. Analyze and design analog & digital circuits or systems for a given specification and function.
2. Implement functional blocks of hardware-software co-designs for signal processing and communication applications.

After successful completion of the course, Students will be able to:

CO No	Course Outcomes	Knowledge Level (Bloom's Taxonomy)
CO 1	Review transistor operation at high frequencies based on an understanding of multistage amplification, feedback, and its performance.	L4 (Analyze)
CO 2	Acquire a deep understanding of oscillator theory, focusing on both RC and LC oscillators and their stability along with applications in electronic systems.	L2(Understand)
CO 3	Evaluate the performance of power and tuned amplifiers, by considering Q-factor, frequency response.	L5(Evaluate)
CO 4	Design and test monostable, bistable, and a stable multivibrators, including Schmitt triggers, for pulse and waveform generation in digital circuits.	L6(Create)
CO 5	Comprehend the general features and methods of transistor-based generating time base waveforms, for improving linearity.	L2 (Understand)

Justifications for CO - PO Mapping:

Course Outcomes (COs)	POs / PSOs	Justification for mapping (Students will be able to)	No. of key competencies
CO 1	PO2	1. Problem or opportunity identification 2. Problem statement and system definition 3. Information and data collection 4. Solution development or experimentation /Implementation	4
	PO3	1. Investigate and define a problem and identify constraints including environmental and sustainability limitations, health and safety and risk assessment issues; 2. Use creativity to establish innovative solutions; 3. Understanding of the requirement for engineering activities to promote sustainable development.	3
	PO4	1. Knowledge of characteristics of particular materials, equipment, processes, or products; 2. Workshop and laboratory skills; 3. Understanding of contexts in which engineering knowledge can be applied (example, operations and management, technology development, etc.)	3
	PO5	1. Computer software / simulation packages / diagnostic	1

		equipment / technical library resources / literature search tools.	
	PSO1	1. Analyze response of a circuit or system	1
	PSO2	1. Implement Operational block diagrams	1
CO 2	PO1	1. Scientific principles and methodology 2. Mathematical principles	2
	PO2	1. Problem or opportunity identification 2. Problem statement and system definition 3. Problem formulation and abstraction 4. Information and data collection 5. Experimental design 6. Solution development or experimentation /Implementation.	6
	PO3	1. Investigate and define a problem and identify constraints including environmental and sustainability limitations, health and safety and risk assessment issues; 2. Use creativity to establish innovative solutions; 3. Understanding of the requirement for engineering activities to promote sustainable development;	3
	PO5	1. Computer software / simulation packages / diagnostic equipment / technical library resources / literature search tools.	1
	PSO1	1. Analyze response of a circuit or system 2. Design of a circuit or system for a given specifications	2
	PSO2	1. Implement Operational block diagrams 2. Applications of a circuit or system	2
CO3	PO1	1. Scientific principles and methodology	1
	PO2	1. Problem or opportunity identification 2. Problem statement and system definition 3. Problem formulation and abstraction	3
	PO3	1. Investigate and define a problem and identify constraints including environmental and sustainability limitations, health and safety and risk assessment issues; 2. Knowledge and understanding of commercial and economic context of engineering processes; 3. Knowledge of management techniques which may be used to achieve engineering objectives within that context.	3
	PO5	1. Computer software / simulation packages / diagnostic equipment / technical library resources / literature search tools.	1
	PSO1	1. Analyze response of a circuit or system	1
	PSO2	1. Implement Operational block diagrams	1
CO 4	PO2	1. Problem or opportunity identification 2. Problem statement and system definition 3. Information and data collection 4. Solution development or experimentation /Implementation	4

	PO4	1. Knowledge of characteristics of particular materials, equipment, processes, or products; 2. Workshop and laboratory skills; 3. Understanding of contexts in which engineering knowledge can be applied (example, operations and management, technology development, etc.).	3
	PO5	1. Computer software / simulation packages / diagnostic equipment / technical library resources / literature search tools.	1
	PSO1	1. Analyze response of a circuit or system	1
	PSO2	1. Implement Operational block diagrams	1
CO 5	PO2	1. Problem or opportunity identification 2. Problem statement and system definition 3. Problem formulation and abstraction 4. Information and data collection	4
	PO4	1. Knowledge of characteristics of particular materials, equipment, processes, or products; 2. Workshop and laboratory skills; 3. Understanding of contexts in which engineering knowledge can be applied (example, operations and management, technology development, etc.).	3
	PO5	1. Computer software / simulation packages / diagnostic equipment / technical library resources / literature search tools.	1
	PSO1	1. Analyze response of a circuit or system 2. Design of a circuit or system for a given specifications	2
	PSO2	1. Implement Operational block diagrams	1

Percentage of Key Competencies for CO – PO Mapping:

Course Outcomes (COs)	Program Outcomes (POs) / Number of Vital Features												Program Specific Outcomes (PSOs) / Number of Vital Features	
	1	2	3	4	5	6	7	8	9	10	11	12	1	2
	3	10	10	11	1	5	3	3	12	5	12	8	2	2
CO 1		40	30	27	100								50	50
CO 2	66	60	30		100								100	100
CO 3	33	30	30		100								50	50
CO 4		40	30		100								50	50
CO 5		40		27	100								100	50

Course Articulation Matrix (CO - PO / PSO Mapping):

COs and POs and COs and PSOs on the scale of 0 to 3, **0** being **no correlation**, **1** being the **low correlation**, **2** being **medium correlation** and **3** being **high correlation**.

0 – $0 \leq C \leq 5\%$ –No correlation; **2** – $40\% < C < 60\%$ –Moderate.

1 – $5 < C \leq 40\%$ – Low/ Slight; **3** – $60\% \leq C < 100\%$ – Substantial /High

Course Outcomes (COs)	Program Outcomes (POs)												Program Specific Outcomes (PSOs)	
	1	2	3	4	5	6	7	8	9	10	11	12	1	2
CO 1		2	1	1	3								2	2
CO 2	3	3	1		3								3	3
CO 3	1	1	1		3								2	2
CO 4		2	1		3								2	2
CO 5		2		1	3								3	2
TOTAL	4	10	4	1	15								12	11
AVERAGE	2	2	1	0.5	3								2.4	2.2



MARRI LAXMAN REDDY INSTITUTE OF TECHNOLOGY AND MANAGEMENT

(AN AUTONOMOUS INSTITUTION)

(Approved by AICTE, New Delhi & Affiliated to JNTUH, Hyderabad)

Accredited by NBA and NAAC with 'A' Grade & Recognized Under Section 2(f) & 12(B) of the UGC act, 1956

L T P C
0 0 2 1

(2440473) ELECTRONIC CIRCUITS LAB

Course Objectives:

The students will try to learn

- Single stage and multi stage amplifiers
- The feedback amplifiers and oscillators through simulation.
- Frequency response of Power Amplifiers
- The Implementation of circuits for linear and nonlinear wave shaping
- The characteristics of different multivibrators

Course Outcomes:

After successful completion of the course, students shall be able to

- Review transistor operation at high frequencies based on an understanding of multistage amplification, feedback, and its performance.
- Acquire a deep understanding of oscillator theory, focusing on both RC and LC oscillators and their stability along with applications in electronic systems.
- Evaluate the performance of power and tuned amplifiers, by considering Q-factor, frequency response.
- Design and test monostable, bistable, and a stable multivibrators, including Schmitt triggers, for pulse and waveform generation in digital circuits.
- Comprehend the general features and methods of transistor-based generating time base waveforms, for improving linearity.

LIST OF EXPERIMENTS:

Experiments marked with * has to be designed, simulated and verify in hardware laboratory.

1. Two Stage RC Coupled Amplifier(*).
2. Cascade amplifier Circuit/ Darlington Pair Circuit (*).
3. Current Shunt Feedback amplifier Circuit(*).
4. Voltage Series Feedback amplifier Circuit (*).
5. RC Phase shift Oscillator Circuit (*).
6. Hartley and Colpitt's Oscillators Circuit(*).
7. Class A power amplifier(Transformer less) (*).
8. Class B Complementary symmetry amplifier (*).
9. Single Tuned Amplifier Circuit(*).
10. Monostable Multivibrator(*).
11. Bistable Multivibrator(*).
12. Astable Multivibrator(*).
13. Schmitt Trigger using transistor(*).

14. The output voltage waveform of Miller Sweep Circuit.

15. The output voltage waveform of Bootstrap Time Base Generator.

NOTE: Minimum of 12 experiments to be conducted

COURSE STRUCTURE, OBJECTIVES & OUTCOMES

COURSE STRUCTURE

Level	Credits	Periods/week	Prerequisites
UG	1	3	Entire subject of Electronic Devices and Circuits.

Evaluation Scheme:

MID (Internal Lab) Semester Test	20 marks
Day to day evaluation	20 marks
End Semester Lab external Examination	60 marks

The end semester examination shall be conducted with an external examiner and internal examiner.

The external examiner shall be appointed by the principal / Chief Controller of examinations.

Course Objectives:

The students will try to learn

- Single stage and multi stage amplifiers
- The feedback amplifiers and oscillators through simulation.
- Frequency response of Power Amplifiers
- The Implementation of circuits for linear and nonlinear wave shaping
- The characteristics of different multivibrators

Course Outcomes:

After successful completion of the course, students shall be able to

- Review transistor operation at high frequencies based on an understanding of multistage amplification, feedback, and its performance.
- Acquire a deep understanding of oscillator theory, focusing on both RC and LC oscillators and their stability along with applications in electronic systems.
- Evaluate the performance of power and tuned amplifiers, by considering Q-factor, frequency response.
- Design and test monostable, bistable, and a stable multivibrators, including Schmitt triggers, for pulse and waveform generation in digital circuits.
- Comprehend the general features and methods of transistor-based generating time base waveforms, for improving linearity.

INDEX

S. No	Name of the Experiment	Page No:
1	Two Stage RC Coupled Amplifier.	17-25
2	Cascade Amplifier Circuit/ Darlington Pair Circuit.	26-40
3	Current Shunt Feedback Amplifier.	41-47
4	Voltage Series Feedback Amplifier.	48-56
5	RC Phase Shift Oscillator using Transistors.	57-62
6	Hartley and Colpitt's Oscillator Circuit.	63-75
7	Class A Power Amplifier (Transformer less).	76-82
8	Class B Complementary Symmetry Amplifier.	83-89
9	Single tuned amplifier circuit.	90-95
10	Design a Monostable Multivibrator.	96-102
11	Design a Bistable Multivibrator.	103-109
12	Design a Astable Multivibrator.	110-117
13	Schmitt Trigger using transistor.	118-124
14	The output voltage waveform of Miller Sweep Circuit.	125-128
15	The output voltage waveform of Bootstrap Time Base Generator.	129-132
16	Cascode Amplifier circuit.	133-140

EXP NO: 1**TWO STAGE RC COUPLED AMPLIFIER (Software)****PRELAB:**

1. Study the purpose of using multistage amplifiers.
2. Learn the different types of coupling methods.
3. Study the effect of cascading on Bandwidth.
4. Identify all the formulae you will need in this Lab.
5. Study the procedure of using Multisim tool (Schematic & Circuit File).


OBJECTIVE:

1. To simulate the Two Stage RC Coupled Amplifier in Multisim and study the transient and frequency response.
2. To determine the phase relationship between the input and output voltages by performing the transient analysis.
3. To determine the maximum gain, 3dB gain, lower and upper cutoff frequencies and bandwidth of Two Stage RC Coupled Amplifier by performing the AC analysis.
4. To determine the effect of cascading on gain and bandwidth.

SOFTWARE TOOL: Multisim 13.0

APPARATUS:

1. Regulated power supply	-	1 No.
2. Function generator	-	1 No.
3. CRO	-	1 No.
4. Transistor (BC 107 or 2N2222)	-	2 No.
5. Resistors (5K Ω , 47 K Ω , 2 K Ω , , 1 K Ω)	-	2 No. each
6. Resistor (10 K Ω)	-	4 Nos.
7. Capacitors (10 μ F, 1 μ F)	-	2, 3 No. each
8. Bread Board	-	1 No.
9. Connecting wires		

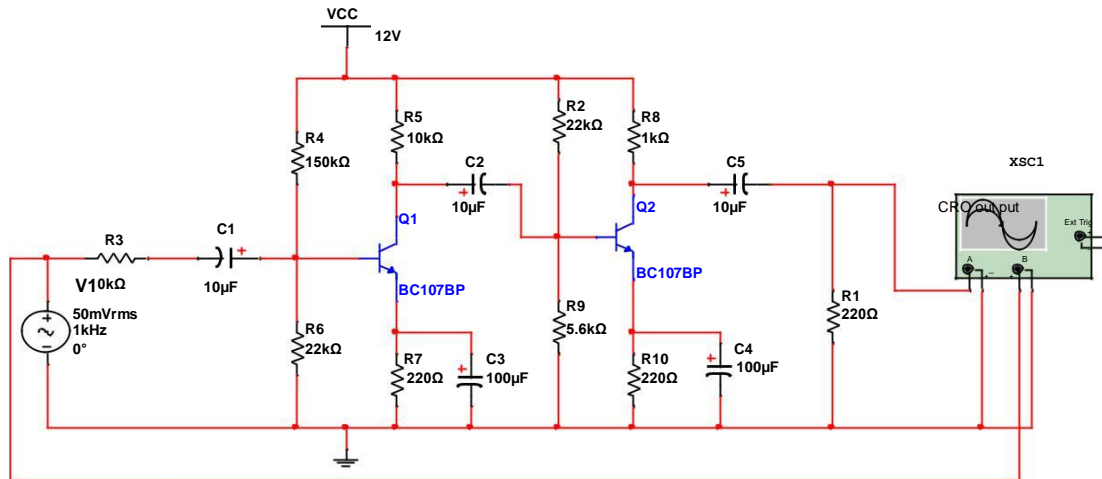CIRCUIT DIAGRAM:**Fig: 1.a Two Stage RC Coupled Amplifier Circuit Diagram****THEORY:**

An amplifier is the basic building block of most electronic systems. Just as one brick does not make a house, a single-stage amplifier is not sufficient to build a practical electronic system. The gain of the single stage is not sufficient for practical applications. The voltage level of a signal can be raised to the desired level if we use more than one stage. When a number of amplifier stages are used in succession (one after the other) it is called a multistage amplifier or a cascade amplifier. Much higher gains can be obtained from the multi-stage amplifiers. In a multi-stage amplifier, the output of one stage makes the input of the next stage. We must use a suitable coupling network between two stages so that a minimum loss of voltage occurs when the signal passes through this network to the next stage. Also, the dc voltage at the output of one stage should not be permitted to go to the input of the next. If it does, the biasing conditions of the next stage are disturbed.

Figure shows how to couple two stages of amplifiers using RC coupling scheme. This is the most widely used method. In this scheme, the signal developed across the collector resistor R_C (R_2) of the first stage is coupled to the base of the second stage through the capacitor C_c (C_2). The coupling capacitor blocks the dc voltage of the first stage from reaching the base of the second stage. In this way, the dc biasing of the next stage is not interfered with. For this reason, the capacitor C_c (C_2) is also called a blocking capacitor.

As the number of stages increases, the gain increases and the bandwidth decreases. RC coupling scheme finds applications in almost all audio small-signal amplifiers used in record players, tape recorders, public-address systems, radio receivers, television receivers, etc.

PROCEDURE:

1. Open Multisim Software to design Two stage RC coupled amplifier circuit
2. Select on New editor window and place the required component CS amplifier on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Indicate the node names and go for AC Analysis with the output node
6. Observe the Transient response and Ac Analysis for the first stage and second stage separately and draw the magnitude response curve
7. Calculate the bandwidth of the amplifier

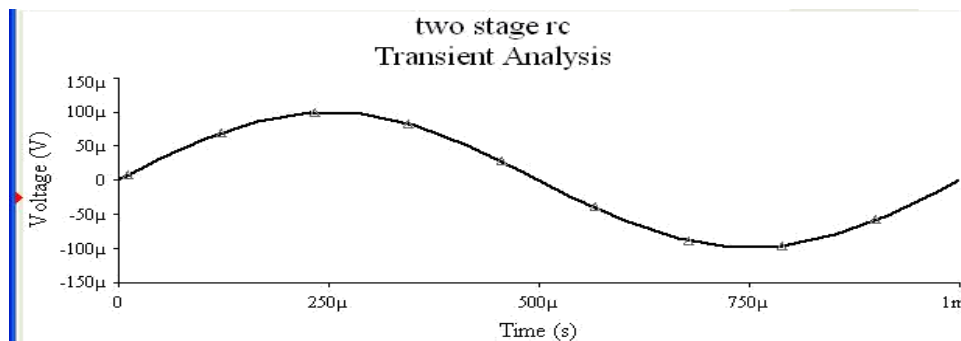
OBSERVATIONS/GRAPHS:**TRANSIENT RESPONSE:**

Fig 1.b: Transient response of First stage in Two stage RC coupled amplifier

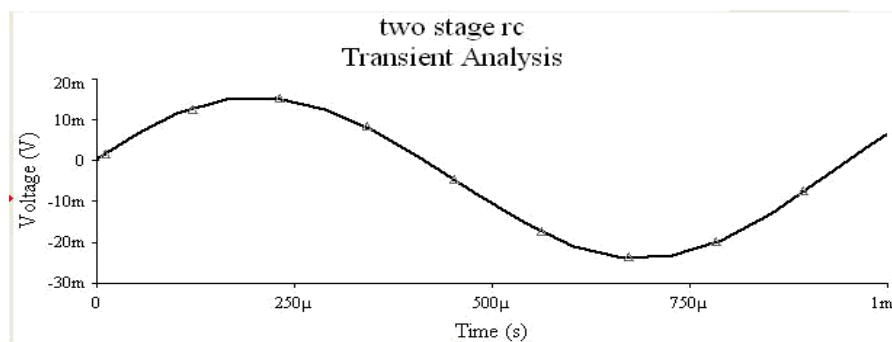


Fig 1.c: Transient response of second stage in Two stage RC coupled amplifier

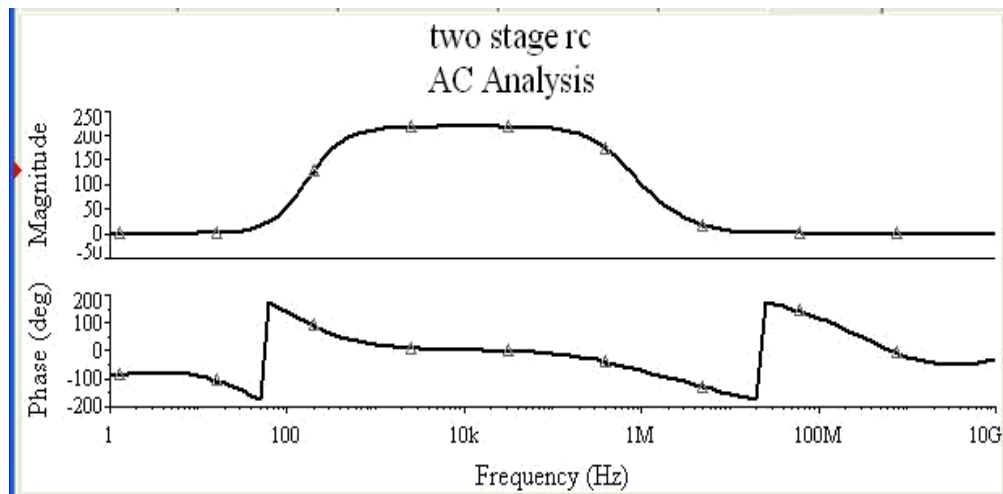
FREQUENCY RESPONSE:

Fig 1.d: Frequency response of Two stage RC coupled amplifier

RESULTS :

1. From the transient analysis, it is observed that, _____
2. From the frequency response curve the following results are calculated.
3. From the AC response, it is observed that, _____


S. No.	Parameter	Value
1	Max. Gain in dB	
2	3dB Gain	
3	Lower Cutoff Frequency	
4	Upper Cutoff Frequency	
5	Bandwidth of I stage	
6	Bandwidth of 2 stage	

EXPT NO :1**TWO STAGE RC COUPLED AMPLIFIER (Hardware)****AIM: -**

1. Plot the frequency response of a Two Stage Amplifier.
2. Calculate gain.
3. Calculate bandwidth.

COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	1
	(c) Capacitors	10 F	2
		100 F	1
	(d) Resistors	100 ,470 4.7K ,8.2k	1 1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

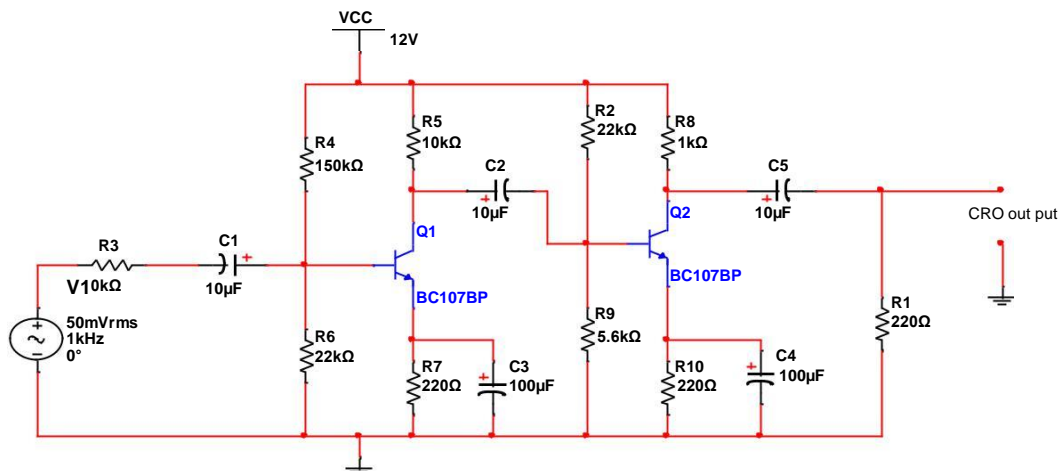CIRCUIT DIAGRAM:**Fig: 1.e: circuit diagram of Two Stages RC coupled amplifier**

PROCEDURE :

1. Connect the circuit diagram as shown in figure.
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, vary the input signal frequency from 0 to 1MHz in steps as shown in tabular column and note the corresponding output voltages.

PRECAUTIONS:

Avoid loose connections and give proper input Voltage

TABULAR COLUMN:

Frequency(in Hz)	Output Voltage (V_o)		Gain $A_v = V_o/V_i$		Gain(in dB) $= 20\log_{10}(V_o/V_i)$	
	With feedback	Without feedback	With feedback	Without feedback	With feedback	Without feedback
20						
40						
80						
100						
1K						
10k						
50k,100K						
1M						

RESULT: -

1. Frequency response of Two stage RC coupled amplifier graph is plotted.
2. Gain = _____dB (maximum).
3. Bandwidth= $f_H - f_L$ = _____Hz. At stage I
4. Bandwidth= $f_H - f_L$ = _____Hz. At stage 2

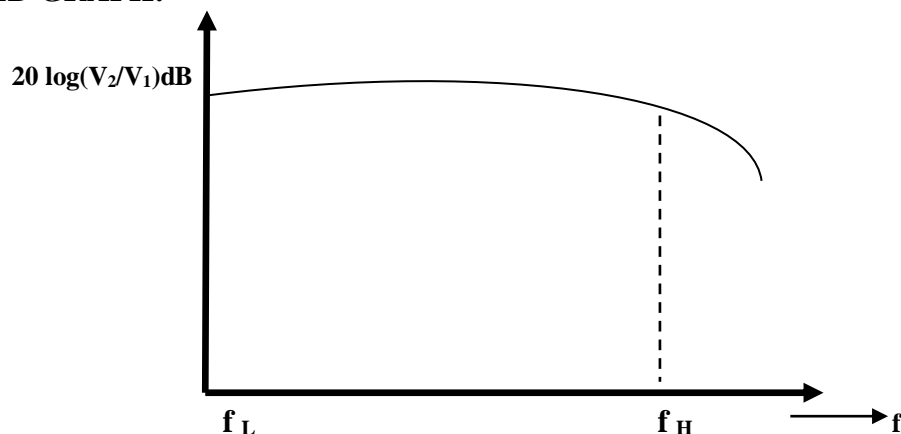
EXPECTED GRAPH:

Fig: 1.f: Expected waveform of Two Stages RC coupled amplifier

VIVA QUESTIONS:

1. Why do you need more than one stage of amplifiers in practical circuits?
2. What is the effect of cascading on gain and bandwidth?
3. What happens to the 3dB frequencies if the number of stages of amplifiers increases?
4. Why we use a logarithmic scale to denote voltage or power gains, instead of using the simpler linear scale?
5. What is loading effect in multistage amplifiers?
6. What is the necessity of cascading?
7. What is 3dB bandwidth?
8. Why RC coupling is preferred in audio range?
9. Which type of coupling is preferred and why?
10. Explain various types of Capacitors?
11. What is loading effect?
12. Why it is known as RC coupling?
13. What is the purpose of emitter bypass capacitor?
14. Which type of biasing is used in RC coupled amplifier?
15. What is difference between Amplifier and Attenuator?
16. Which Amplifier will amplify voltage and current?
17. What are the advantages over single stage amplifier?
18. What are the classifications of multistage amplifiers?
19. What are the different BJT multistage amplifier configurations?
20. Define cut off frequency?
21. What Is the pin configuration on bread board used in the lab?
22. What is two stages RC coupled amplifier?
23. Which type of coupling is preferred and why?
24. Explain various types of Capacitors?
25. What is two stages RC coupled amplifier?
26. Plot the frequency response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
27. Plot the frequency response of BC 547 amplifier with $C_2 = 5 \mu\text{F}$ with i/p.
28. Plot the frequency response of BC 2N2222 amplifier with $R_1 = 4.1 \text{ K}$.
29. Plot the frequency response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
30. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.

EXERCISE PROBLEMS:

1. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
2. Plot the frequency response of amplifier with $C_2 = 5 \mu\text{F}$, i/p.
3. Plot the frequency response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
4. Plot the frequency response of BC107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
5. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
6. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \mu\text{F}$.
7. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \mu\text{F}$ with i/p.
8. Plot the frequency response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
9. Plot the frequency response of BC 107 amplifier with $R_2 = 5.4 \text{ K}$ i/p.
10. Plot frequency response of BC 107 amplifier $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.
11. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 2 \mu\text{F}$.
12. Plot the frequency response of amplifier with $C_2 = 2 \mu\text{F}$, i/p.
13. Plot the frequency response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
14. Plot the frequency response of BC 107 amplifier with $R_2 = 2.4 \text{ K}$ i/p.
15. Plot frequency response of $R_1 = 2.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p

APPLICATIONS:

1. They are widely used as voltage amplifiers (ie. In the initial stages of public address systems) because of their excellent audio-fidelity over a wide range of frequency. However because of poor impedance matching this type of coupling transistor circuits is rarely employed in final stages impedance matching voltage amplifier in initial stage of public addressing system.
2. To increase the power gain, high input impedance, low output impedance, and increase the weakened signal.
3. To increase the power gain, high input impedance, low output impedance, and increase the weakened signal.
4. In a two stage RC coupled amplifier, the two transistors are identical and a common power supply is used. The input is provided to the first stage of the amplifier where it is amplified and this output is used as input for the second stage.
5. This is amplified once again by the other transistor in the second stage and the final output is obtained.
6. There will be a 180 degree phase shift after the first stage amplification which is nullified by the 180 degree phase shift of the second stage amplification. Thus, we obtain an output which is an amplified signal of the input and is in phase with the input signal.

EXP NO 2: CASCADE AMPLIFIER CIRCUIT /DARLINGTON PAIR CIRCUIT**EXPT NO: 2.A****CASCADE AMPLIFIER (Software)**

AIM: To study the frequency response of amplifier, calculate voltage gain and bandwidth from the response.

APPARATUS:

1.Regulated power supply	-	1 No.
2.Function generator	-	1 No.
3.CRO	-	1 No.
4.Transistor (BC 547BG or 2N2222)	-	2 No.
5.Resistors (22K Ω ,1.2K Ω , 4.7K Ω ,300 Ω)	-	2 No. each
6.Capacitors (0.1 μ F, 4.7 μ F)	-	2,1No. each
7.Bread Board	-	1 No.
8.Connecting wires		

SOFTWARE USED: Multisim V13.0

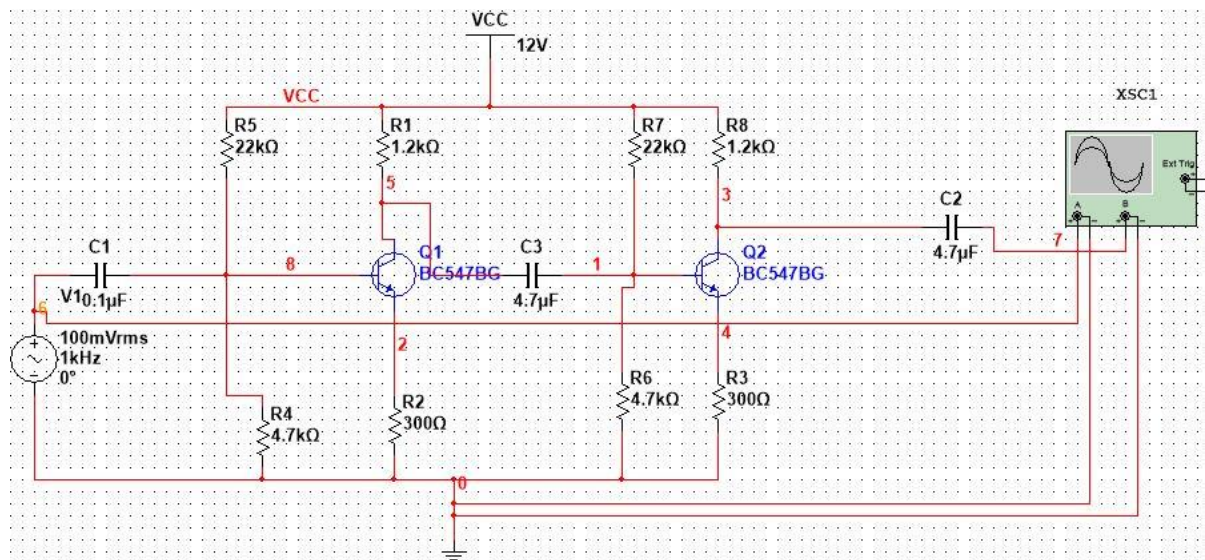
CIRCUIT DIAGRAM:

Fig: 2A.a Cascade Amplifier circuit diagram

THEORY:

A cascade amplifier is a multi-stage amplifier configuration where the output of one amplifier stage is connected to the input of the next stage. This arrangement is used to achieve a higher overall gain than what a single stage could provide. Each stage typically consists of a common-emitter or common-source configuration in the case of BJTs or MOSFETs, respectively. The main advantage of cascading amplifier stages is the multiplication of individual stage gains, allowing for significant amplification of weak signals. Additionally, cascade amplifiers improve input and output impedance matching, which enhances signal transfer efficiency between stages. However, careful design is required to minimize issues like phase shift, distortion, and bandwidth limitations that can arise due to the interaction between stage

PROCEDURE:

1. Switch ON the computer and open the multisim software.
2. Check whether the icons of the instruments are activated and enable.
3. Now connect the circuit using the designed values of each and every component.
4. Connect the function generator with sine wave of 50mVp-p as input at the input of terminals of the circuit.
5. Connect the Cathode Ray Oscilloscope (CRO) to the out put terminals of the circuit.
6. Go to simulation button click it for simulation process.
7. From the CRO note the following values
 1. Input voltage $V_i =$
 2. Output voltage $V_0 =$
 3. Voltage gain $A_v = V_0/V_i =$
 4. Phase shift $\theta =$
8. To study the frequency response click the AC analysis, so that a screen displays the following options
 1. Start frequency
9. Assign the proper values for start frequency, stop frequency and vertical scale according to the circuit requirements and observe the frequency response.
10. From the frequency response calculate the

maximum gain $A_{Vmax} =$

lower cutoff frequency (f_1) at $A_{Vmax}-3\text{dB}$ (decibel scale) value

at $A_{Vmax}/\sqrt{2}$ (linear scale) =

Higher cutoff frequency (f_2) at $A_{Vmax}-3\text{dB}$ (decibel scale) valu

at $A_{V_{max}}/\sqrt{2}$ (linear scale) =

OBSERVATIONS:

From CRO:



Fig: 2A.b Output waveform of cascade amplifier

1. Input voltage V_i =
2. Output voltage V_o =
3. Voltage gain $A_v = V_o/V_i$ =
4. Phase shift θ =

From Frequency response:

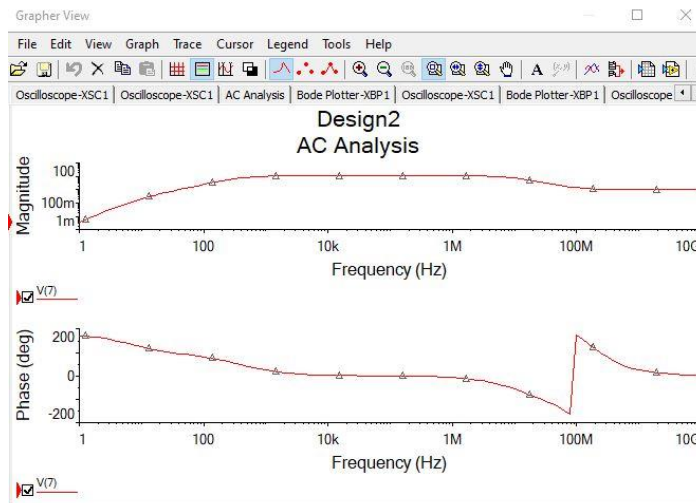


Fig: 2A.c Frequency response of cascade amplifier

1. Maximum gain $A_{V_{max}}$ =
2. Lower cutoff frequency(f_1) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value
at $A_{V_{max}}/\sqrt{2}$ (linear scale) =
3. Higher cutoff frequency(f_2) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value
at $A_{V_{max}}/\sqrt{2}$ (linear scale) =



CALCULATIONS:

$$\text{Band width (BW)} = f_2 - f_1$$

RESULT: Cascade amplifier is design with the given specifications and from observed frequency response, gain and band width are calculated.

APPLICATION:

1. It is used in RF tunner.
2. Used in Amplitude Modulation.

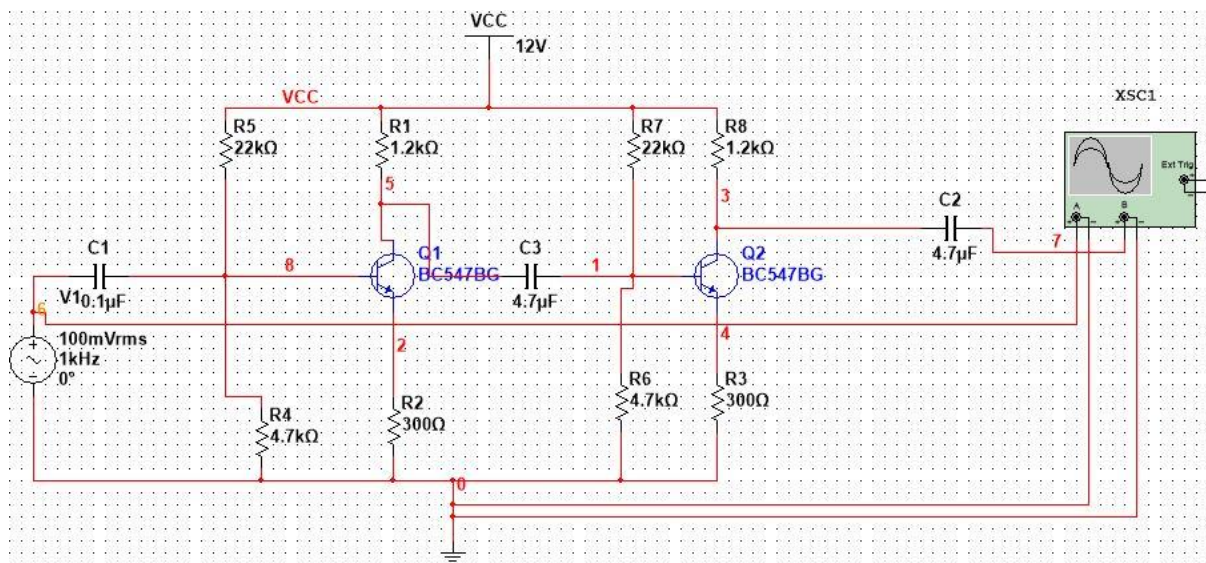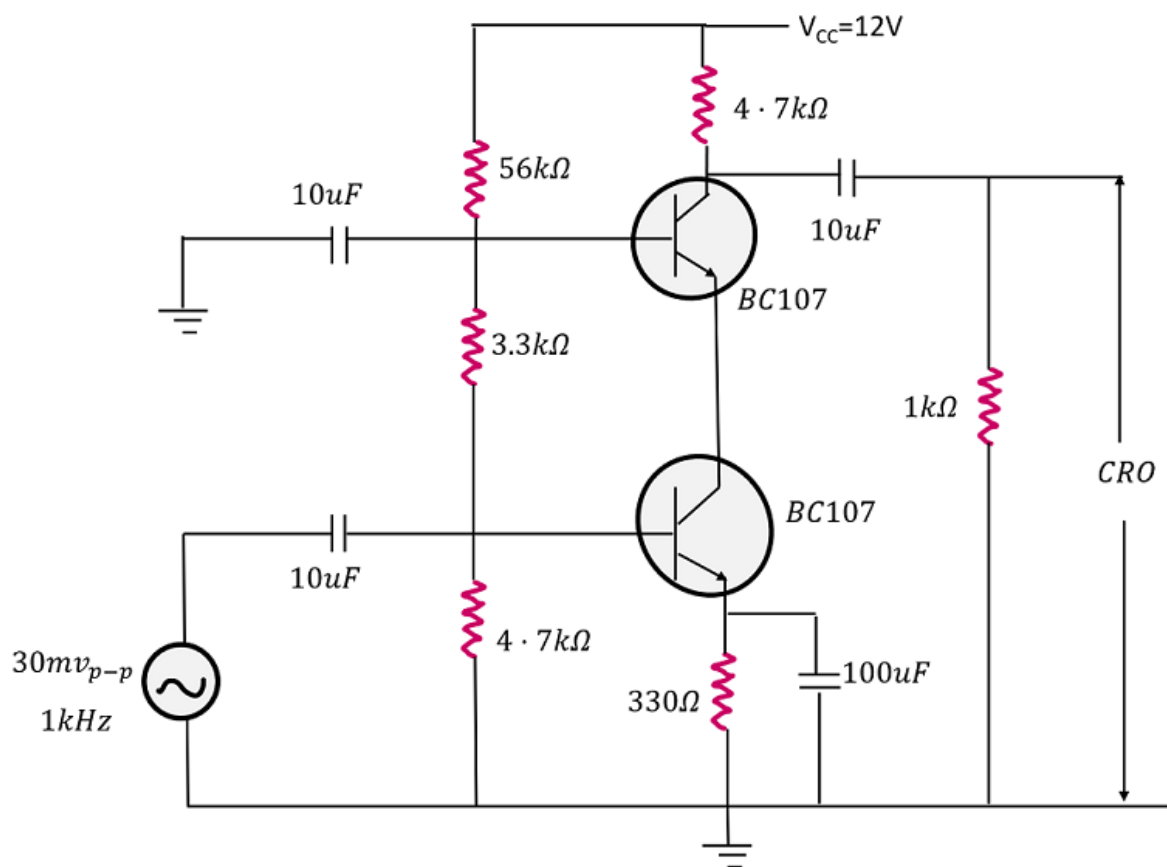EXP NO: 2.A**CASCADE AMPLIFIER (HARDWARE)****Fig: 2A.d Cascade Amplifier circuit diagram**

PROCEDURE: -

1. Connect the circuit diagram as shown in figure.
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, vary the input signal frequency from 0 to 1MHz in steps as shown in tabular column and note the corresponding output voltages.

PRECAUTIONS:

Avoid loose connections and give proper input Voltage

TABULAR COLUMN :

Input $V_i = 50\text{mV}$

Frequency(Hz)	Output voltage V_o	Gain $= V_o / V_i$	Gain in dB $= 20\log(V_o / V_i)$
50Hz			
100Hz			
1KHz			
10KHz			
50KHz			
100KHz			
500KHz			
1MHz			

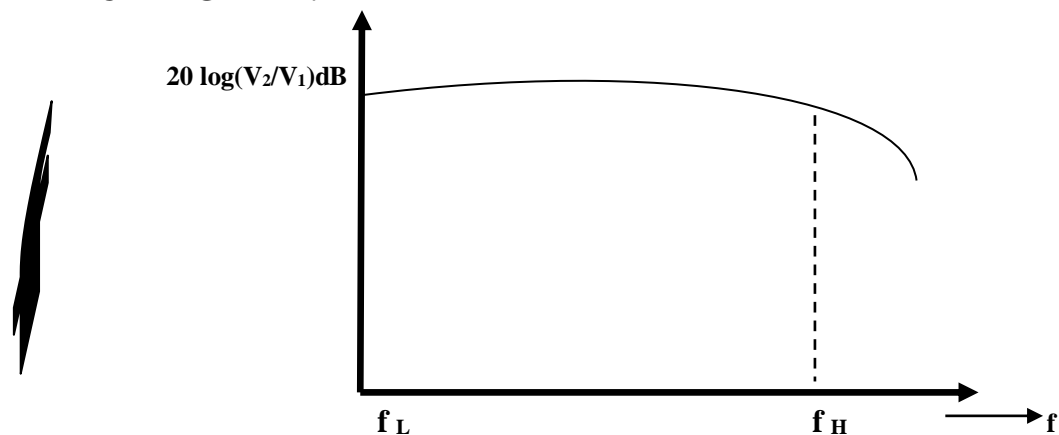
EXPECTED GRAPH:

Fig: 2.e: Expected waveform of Cascade Amplifier

RESULT:

1. Frequency response of Cascade amplifier graph is plotted.
2. Gain = _____ dB (maximum).
3. Bandwidth = $f_H - f_L =$ _____

EXP NO:2B**DARLINGTON PAIR AMPLIFIER (SOTWARE)**

AIM: To study the frequency response of amplifier, calculate voltage gain and bandwidth from the response.

APPARATUS:

1.Regulated power supply	-	1 No.
2.Function generator	-	1 No.
3.CRO	-	2 No.
4.Transistor (BC 107 or 2N2222)	-	2 No.
5.Resistors (57.3K Ω ,3.15K Ω , 300 Ω ,1K Ω)	-	1 No. each
6.Resistor (4.7K Ω)	-	2 Nos.
7.Capacitors (10 μ F, 100 μ F)	-	3,1No. each
8.Bread Board	-	1 No.
9.Connecting wires		

SOFTWARE USED: Multisim V13.0

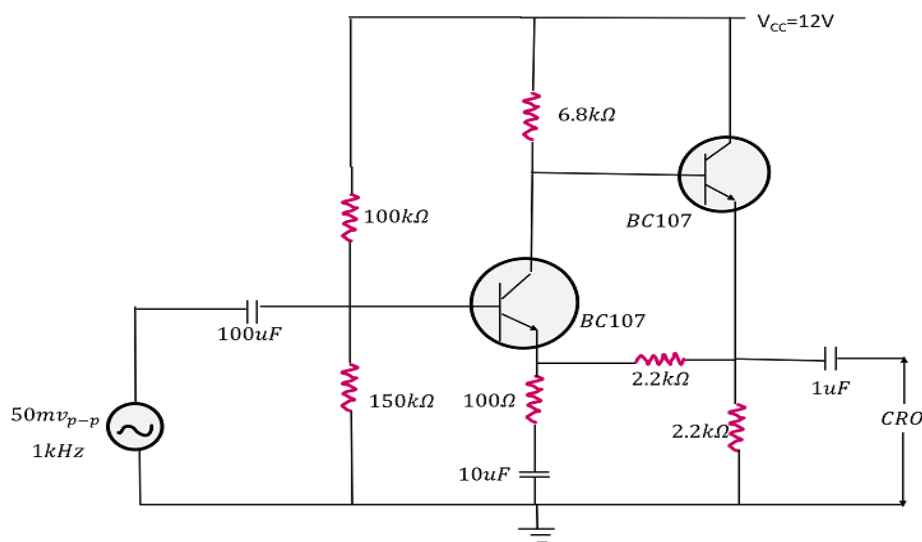
CIRCUIT DIAGRAM:

Fig: 2B.a circuit diagram of Darlington pair amplifier

THEORY:

The Darlington pair is a configuration of two bipolar junction transistors (BJTs) connected in such a way that the current amplified by the first transistor is further amplified by the second transistor. In this setup, the emitters of both transistors are connected together, with the collector of the first transistor connected to the base of the second. The result is a composite transistor with a much higher current gain (β) than a single transistor, often in the range of several thousand. This makes the Darlington pair highly effective in applications requiring large current amplification, such as in power amplifiers and switching circuits. However, this configuration also has a higher base-emitter voltage drop (approximately 1.2V instead of the typical 0.6V for a single BJT) and slower response times, which can limit its use in high-speed applications. Additionally, the increased gain can make the circuit more susceptible to noise and instability if not properly managed.

PROCEDURE:

1. Switch ON the computer and open the multisim software.
2. Check whether the icons of the instruments are activated and enable.
3. Now connect the circuit using the designed values of each and every component.
4. Connect the function generator with sine wave of 50mVp-p as input at the input of terminals of the circuit.
5. Connect the Cathode Ray Oscilloscope (CRO) to the out put terminals of the circuit.
6. Go to simulation button click it for simulation process.
7. From the CRO note the following values
 - a. Input voltage $V_i =$
 - b. Output voltage $V_o =$
 - c. Voltage gain $A_v = V_o/V_i =$
 - d. Phase shift $\theta =$
8. To study the frequency response click the AC analysis, so that a screen displays the following options
 - a. Start frequency
 - b. Stop frequency
 - c. Vertical scale
9. Assign the proper values for start frequency, stop frequency and vertical scale according to the circuit requirements and observe the frequency response.
10. From the frequency response calculate the maximum gain $A_{V_{max}} =$

a. lower cutoff frequency (f_1) at $A_{V_{\max}}-3\text{dB}$ (decibel scale) value

a. at $A_{V_{\max}}/\sqrt{2}$ (linear scale) =

b. Higher cutoff frequency (f_2) at $A_{V_{\max}}-3\text{dB}$ (decibel scale) value

a. at $A_{V_{\max}}/\sqrt{2}$ (linear scale) =

OBSERVATIONS:

From CRO :

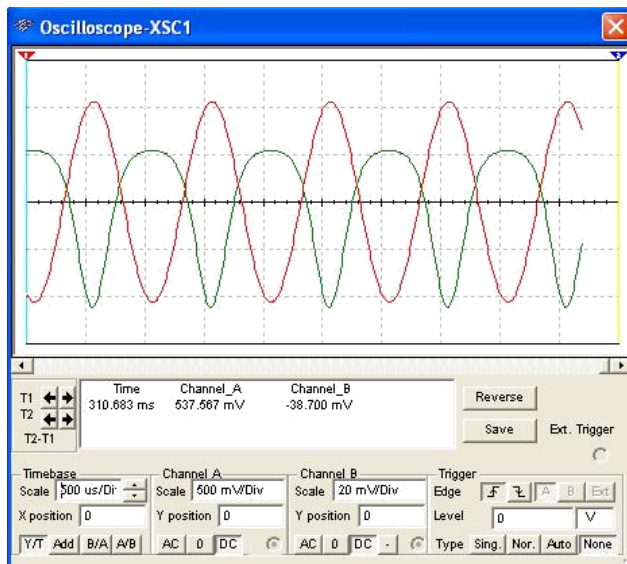


Fig 2B.b output waveform of Darlington Pair circuit

1. Input voltage V_i =
2. Output voltage V_o =
3. Voltage gain $A_v = V_o/V_i$ =
4. Phase shift θ =

From Frequency response:

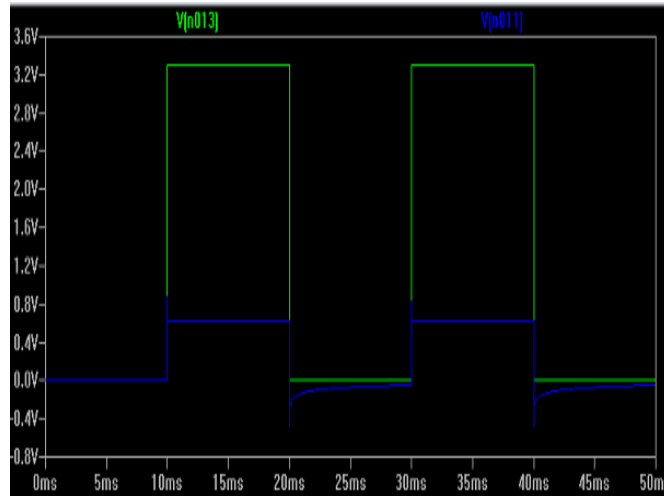


Fig 2B.c Frequency response of Darlington Pair circuit

1. Maximum gain $A_{V_{max}}$ =
2. Lower cutoff frequency(f_1) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value
at $A_{V_{max}}/\sqrt{2}$ (linear scale) =
3. Higher cutoff frequency(f_2) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value
at $A_{V_{max}}/\sqrt{2}$ (linear scale) =

CALCULATIONS:

$$\begin{aligned} \text{Band width (BW)} &= f_2 - f_1 \\ &= \text{Hz} \end{aligned}$$

RESULT: Darlington pair amplifier is design with the given specifications and from observed frequency response, gain and band width are calculated.

EXP NO:2B**DARLINGTON PAIR CIRCUIT (HARDWARE)**

AIM: To study the frequency response of amplifier, calculate voltage gain and bandwidth from the response.

COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Device	Range/Rating	Qty
1.	(a) DC supply voltage	12V	1
	(b) BJT	BC107 BP	2
	(c) Capacitors	100 F, 10 F	2,1
	(d) Resistors	5.6K ,10k ,22K ,1k 220 ,	Each 1NO
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

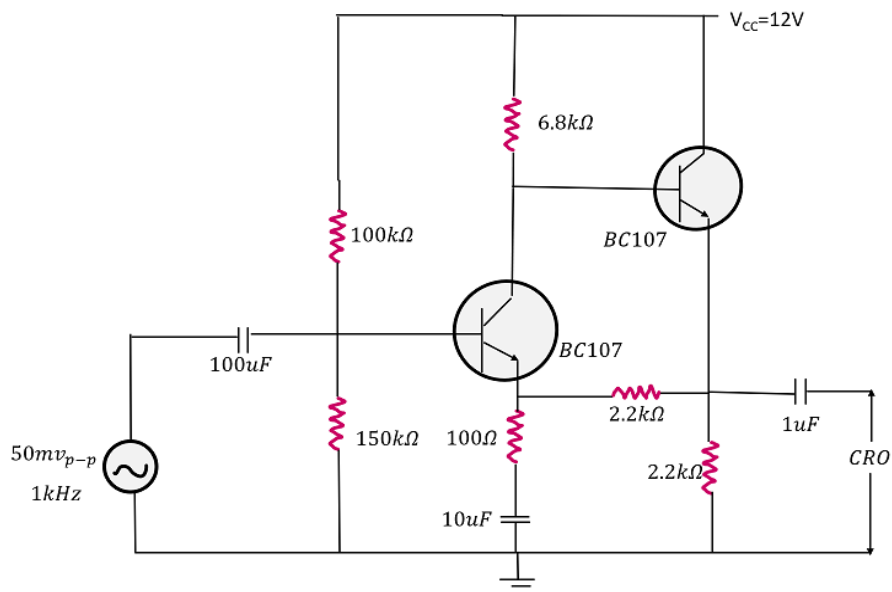
CIRCUIT DIAGRAM:

Fig: 2B.a circuit diagram of Darlington pair amplifier

PROCEDURE:

1. Connect the circuit as per the circuit diagram
2. Now connect the function generator to the input terminals of the amplifier circuit and keep the input voltage constant i.e., 30 mV, 1KHz.
3. Connect the CRO to the output of the amplifier
4. By varying the input frequency from 50 Hz to 100 MHz in steps take the output voltages from CRO.

5. Then calculate Voltage gain $A_V = \frac{V_o}{V_i}$

$$\text{In dB magnitude } A_V = 20 \log \frac{V_o}{V_i}$$

6. Then plot frequency Vs gain in dB on semilog sheet.
7. From semilog sheet find bandwidth ($f_H - f_L$)

$$\text{Band width} = f_H - f_L$$

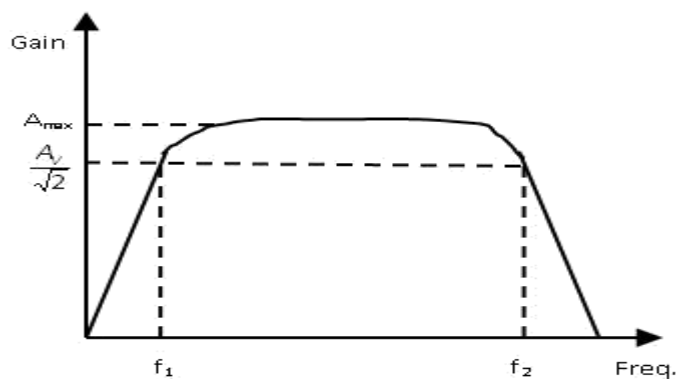
Expected Graph:

Fig: 2B.b: Expected waveform of Darlington pair amplifier

OBSERVATION TABLE:Input Voltage $V_{in} = 50 \text{ mV}$ (constant)

Freq (Hz)	Output voltage V_0 (V)	Gain $A_v = V_0/V_i$	Gain in dB = $20\log(A_v)$
50Hz			
100Hz			
500Hz			
1kHz			
10kHz			
50kHz			
100kHz			
500kHz			
1MHz			

APPLICATIONS

1. Power Regulators.
2. Audio Amplifier o/p stages.
3. Controlling of motors.
4. Display drivers.
5. Controlling of Solenoid.
6. Light and touch sensors.

RESULT: -

1. Frequency response of Darlington pair amplifier Graph is plotted.
2. Gain = _____dB (maximum).
3. Bandwidth= $f_H - f_L =$ _____Hz

VIVA QUESTIONS:

1. Why the cascade amplifier provides a phase reversal?
2. In the dc equivalent circuit of an amplifier, how are capacitors treated?
3. What is the effect of bypass capacitor on frequency response?
4. Define lower and upper cutoff frequencies for an amplifier.
5. State the reason for fall in gain at low and high frequencies.
6. What is meant by unity gain frequency?
7. Define Bel and Decibel.
8. What do we represent gain in decibels?
9. Why do you plot the frequency response curve on a semi-log paper?
10. Explain the function of emitter bypass capacitor C_E ?
11. What is the equation for voltage gain?
12. What is cut off frequency? What is lower 3dB and upper 3dB cut off frequency?
13. What are the applications of Case code amplifier?
14. What is active region?
15. What is Bandwidth of an amplifier?
16. What is the importance of gain bandwidth product?
17. Draw h parameter equivalent circuit of Case code amplifier.
18. What is the importance of coupling capacitors in Case code amplifier?
19. What is the importance of emitter by pass capacitor?
20. What type of feedback is used in case code amplifier?
21. What are the various types of biasing a Transistor?
22. What is Q point of operation of the transistor? What is the region of operation of the transistor when it is working as an amplifier?
23. Why frequency response of the amplifier is drawn on semi-log scale graph?
24. If Q point is not properly selected, then what will be the effect on the output waveform?
25. What are the typical values of the input impedance and output impedance of case code amplifier?
26. What is meant by unity gain frequency?
27. In the dc equivalent circuit of an amplifier, how are capacitors treated?
28. What is the effect of bypass capacitor on frequency response?
29. Define lower and upper cutoff frequencies for an amplifier.
30. State the reason for fall in gain at low and high frequencies.
31. What is meant by unity gain frequency?
32. What is active region?
33. What is Bandwidth of an amplifier?
34. What is the importance of gain bandwidth product?
35. Draw h parameter equivalent circuit of Case code amplifier.
36. What is the importance of coupling capacitors in Case code amplifier?
37. What is the importance of emitter by pass capacitor?
38. What type of feedback is used in case code amplifier?
39. Why the case code amplifier provides a phase reversal?
40. In the dc equivalent circuit of an amplifier, how are capacitors treated?

EXERCISE PROBLEMS:

1. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
2. Plot the frequency response of BC 107 amplifier with $C_2 = 5 \mu\text{F}$ with triangular i/p.
3. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
4. Plot the amplitude response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
5. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
6. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
7. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
8. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \mu\text{F}$.
9. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \mu\text{F}$ with i/p.
10. Plot the amplitude response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
11. Plot the amplitude response of BC 107 amplifier with $R_2 = 5.4 \text{ K}$ i/p.
12. Plot frequency response of BC 107 amplifier $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.
13. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 2 \mu\text{F}$.
14. Plot the frequency response of amplifier with $C_2 = 2 \mu\text{F}$, i/p.
15. Plot the amplitude response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
16. Plot the amplitude response of BC 107 amplifier with $R_2 = 2.4 \text{ K}$ i/p.
17. Plot frequency response of $R_1 = 2.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
18. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
19. Plot the frequency response of BC 107 amplifier with $C_2 = 5 \mu\text{F}$ with i/p.
20. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.

EXP NO: 3**CURRENT SHUNT FEED BACK AMPLIFIER (SOFTWARE)****AIM: -**


1. Study the concept of feedback in amplifiers.
2. Study the characteristics of current shunt feedback amplifier.
3. Identify all the formulae will need in this experiment.

OBJECTIVE:

1. To simulate the Current Shunt Feedback Amplifier in Multisim and study the transient and frequency response.
2. To determine the maximum gain, 3dB gain, lower and upper cutoff frequencies and bandwidth of Current Shunt Feedback Amplifier by performing the AC analysis.
3. To determine the effect of feedback on gain and bandwidth and compare with Multisim results.

REQUIREMENTS:

1. Transistor – 2n2222(2)
2. Resistors – as per circuit diagram
3. Capacitors – as per circuit diagram
4. RPS – 0-30V.
5. CRO.
6. Breadboard.
7. Connecting wires and Probes.

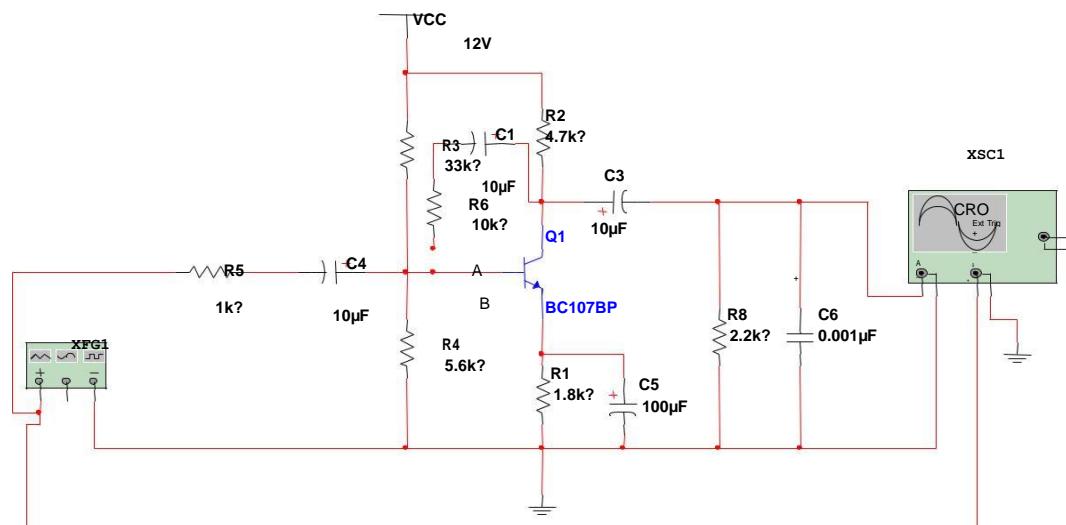CIRCUIT DIAGRAM:**Fig: 3.a Current shunt feedback Amplifier circuit diagram**

THEORY:

Feedback plays a very important role in electronic circuits and the basic parameters, such as input impedance, output impedance, current and voltage gain and bandwidth, may be altered considerably by the use of feedback for a given amplifier.

A portion of the output signal is taken from the output of the amplifier and is combined with the normal input signal and thereby the feedback is accomplished.

There are two types of feedback. They are i) Positive feedback and ii) Negative feedback. Negative feedback helps to increase the bandwidth, decrease gain, distortion, and noise, modify input and output resistances as desired.

A current shunt feedback amplifier circuit is illustrated in the figure. It is called a series-derived, shunt-fed feedback. The shunt connection at the input reduces the input resistance and the series connection at the output increases the output resistance. This is a true current amplifier.

PROCEDURE:

1. Open Multisim Software to design Common Emitter amplifier circuit
2. Select on New editor window and place the required component on the circuit window.
3. Make the connections using wire and set oscillator (FG) frequency & amplitude.
4. Check the connections and the specification of components value properly.
5. Go for simulation using Run Key observe the output waveforms on CRO
6. Indicate the node names and go for AC Analysis with the output node
7. Observe the Ac Analysis and draw the magnitude response curve
8. Calculate the bandwidth of the amplifier

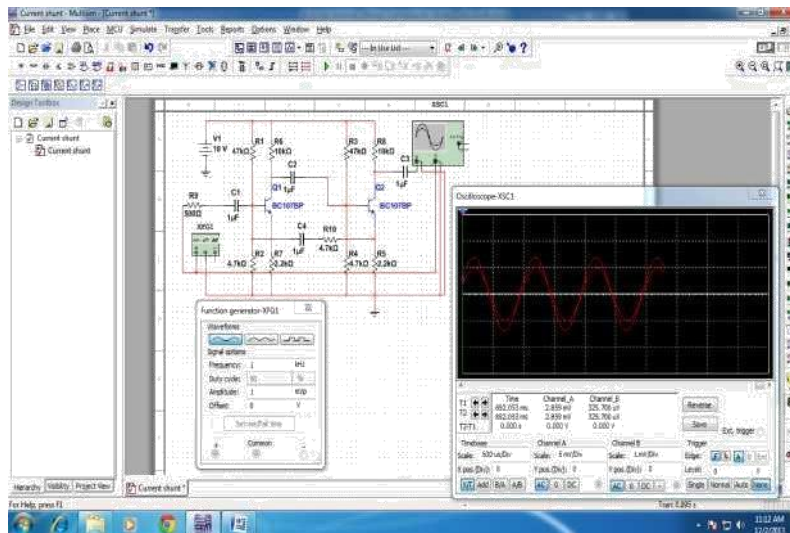
Observations/Graphs:

Fig: 3.b Output waveform Current shunt feedback Amplifier

i) Transient Response:

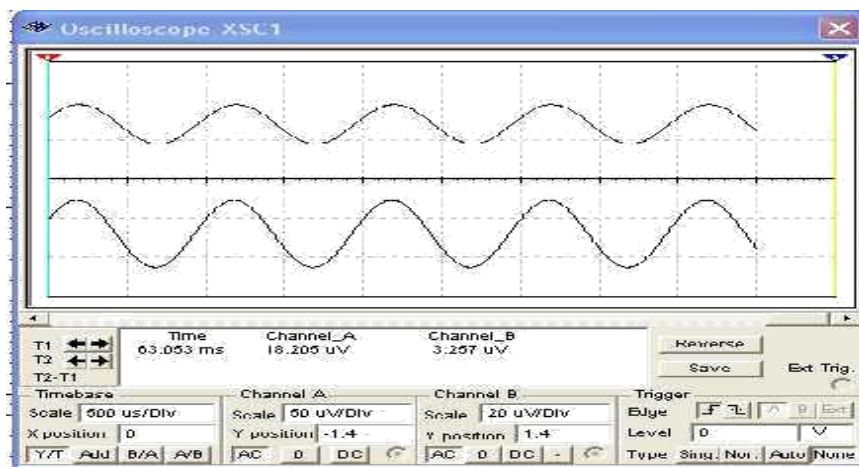


Fig: 3.b Transient response of Current shunt feedback Amplifier

ii) Frequency Response:

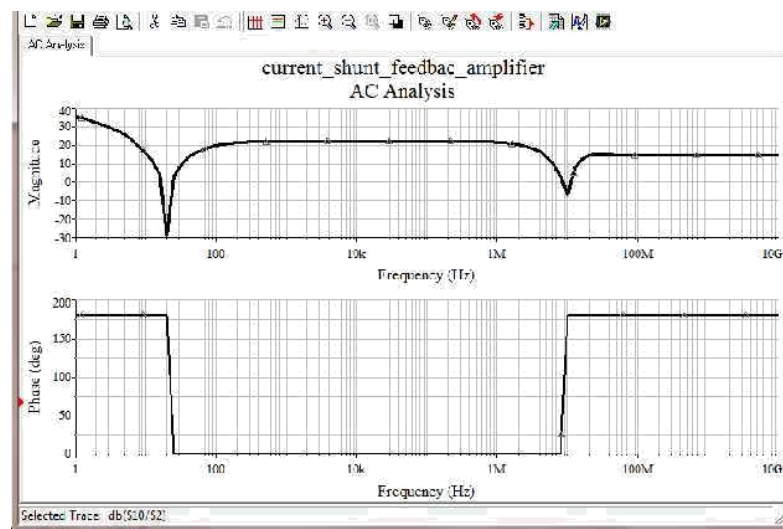


Fig: 3.b Frequency response of Current shunt feedback Amplifier

RESULTS:

1. From the frequency response curve the following results are calculated:

S. No.	Parameter	Value
1	Max. Gain in dB	
2	3dB Gain	


2. From the AC response, it is observed that, _____.

EXP NO:3**CURRENT SHUNT FEED BACK AMPLIFIER (HARDWARE)****AIM:**

1. Plot the frequency response of a Current Shunt Feedback Amplifier.
2. Calculate gain.
3. Calculate bandwidth.

COMPONENTS & EQUIPMENTS REQUIRED:

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	1
	(c) Capacitors	10 μ F	2
		100 μ F	1
	(d) Resistors	3.3K Ω ,5.6K Ω 4.7K Ω ,1.8K Ω ,10K Ω	1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

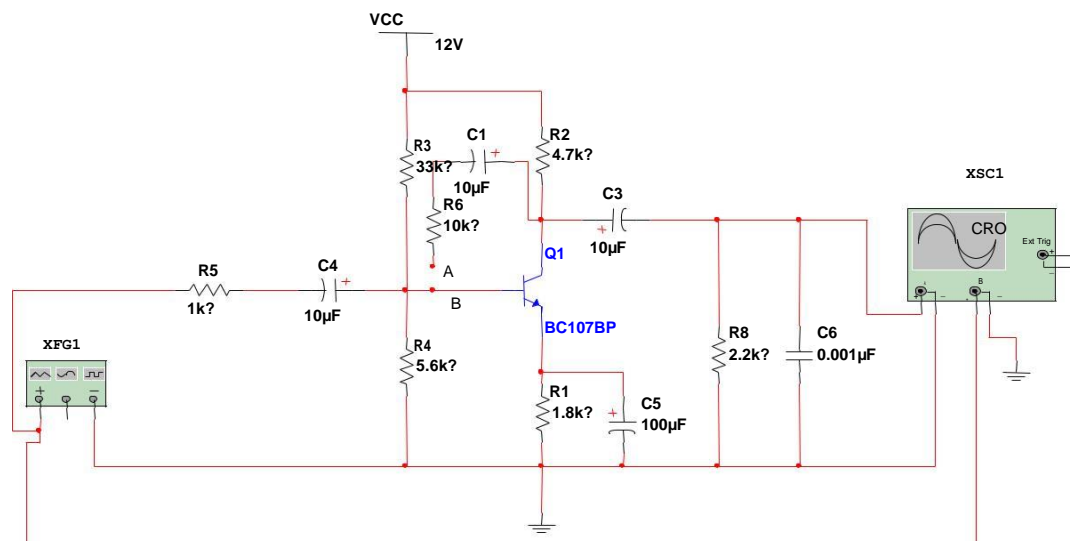CIRCUIT DIAGRAM:**Fig: 3.a Current shunt feedback Amplifier circuit diagram**

PROCEDURE :

1. Connect the circuit diagram as shown in figure.
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, vary the input signal frequency from 0 to 1MHz in steps as shown in tabular column and note the corresponding output voltages.


PRECAUTIONS:

Avoid loose connections and give proper input Voltage

TABULAR COLUMN :

Input $V_i = 50\text{mV}$

Frequency(Hz)	Output voltage V_o	Gain $=V_o / V_i$	Gain in dB $=20\log(V_o / V_i)$
50Hz			
100Hz			
1KHz			
10KHz			
50KHz			
100KHz			
500KHz			
1MHz			

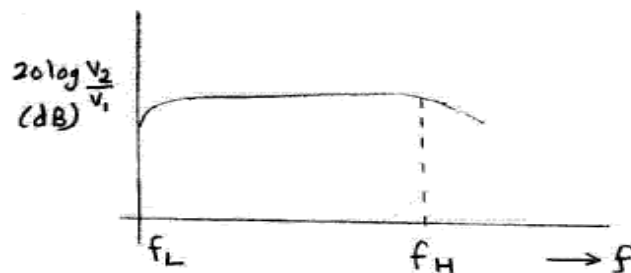EXPECTED GRAPH:**RESULT:**

1. Frequency response of Current Shunt feedback amplifier is plotted.
2. Gain = _____ dB (maximum).
3. Bandwidth = $f_H - f_L =$ _____ Hz

VIVA QUESTIONS :

1. State the merits and demerits of negative feedback in amplifiers.
2. If the bypass capacitor C_E in an RC coupled amplifier becomes accidentally open circuited, what happens to the gain of the amplifier? Explain.
3. When will a negative feedback amplifier circuit be unstable?
4. What is the parameter which does not change with feedback?
5. What type of feedback has been used in an emitter follower circuit?
6. Define Current shunt feedback amplifier?
7. Draw the current shunt feedback amplifier?
8. When will a negative feedback amplifier circuit be unstable?
9. What is the parameter which does not change with feedback?
10. What type of feedback has been used in an emitter follower circuit?
11. Transistor when it is working as an amplifier?
12. Why frequency response of the amplifier is drawn on semi-log scale graph?
13. If Q point is not properly selected, then what will be the effect on the output waveform?
14. What is active region?
15. Why is common base configuration used as current buffer even though it has properties of current amplifier?
16. What does the current shunt feedback amplifier amplify? And how?
17. If the bypass capacitor C_E in an RC coupled amplifier becomes accidentally open circuited, what happens to the gain of the amplifier? Explain.
18. When will a negative feedback amplifier circuit be unstable?
19. What is the parameter which does not change with feedback?
20. Transistor when it is working as an amplifier?
21. Why frequency response of the amplifier is drawn on semi-log scale graph?
22. If Q point is not properly selected, then what will be the effect on the output waveform?
23. What is active region?
24. What is Bandwidth of an amplifier?
25. Why is common base configuration used as current buffer even though it has properties of current amplifier?
26. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 2 \mu F$.
27. Plot the frequency response of amplifier with $C_2 = 2 \mu F$, i/p.
28. Plot the frequency response of BC 107 amplifier with $R_1 = 2.1 K$.
29. Plot the frequency response of BC 107 amplifier with $R_2 = 2.4 K$ i/p.
30. Plot frequency response of $R_1 = 2.1 K$, $R_2 = 9.4 K$ with i/p.

APPLICATIONS:

1. Voltage series feedback ($A_f = V_o/V_s$) –Voltage amplifier
2. Voltage shunt feedback ($A_f = V_o/I_s$) –Trans-resistance amplifier
3. Current series feedback ($A_f = I_o/V_s$) -Trans-conductance amplifier
4. Current shunt feedback ($A_f = I_o/I_s$) -Current amplifier

EXERCISE PROBLEMS:

1. Plot the frequency response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
2. Plot the frequency response of BC 547 amplifier with $C_2 = 5 \mu\text{F}$ with i/p.
3. Plot the frequency response of BC 2N2222 amplifier with $R_1 = 4.1 \text{ K}$.
4. Plot the frequency response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
5. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
6. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
7. Plot the frequency response of amplifier with $C_2 = 5 \mu\text{F}$, i/p.
8. Plot the frequency response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
9. Plot the frequency response of BC107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
10. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
11. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \mu\text{F}$.
12. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \mu\text{F}$ with i/p.
13. Plot the frequency response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
14. Plot the frequency response of BC 10 7 amplifier with $R_2 = 5.4 \text{ K}$ i/p.
15. Plot frequency response of BC 107 amplifier $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.

EXP NO: 4**VOLTAGE SERIES FEED BACK AMPLIFIER (SOFTWARE)**

AIM: To study the frequency response of amplifier, calculate voltage gain and bandwidth from the response.

OBJECTIVE:

1. To simulate the Voltage series feedback Amplifier in Multisim and study the transient and frequency response.
2. To determine the phase relationship between the input and output voltages by performing the transient analysis.
3. To determine the maximum gain, 3dB gain, lower and upper cutoff frequencies and bandwidth of Voltage series feedback Amplifier by performing the AC analysis.
4. To determine the effect of cascading on gain and bandwidth.

SOFTWARE USED:

Multisim V 13.0

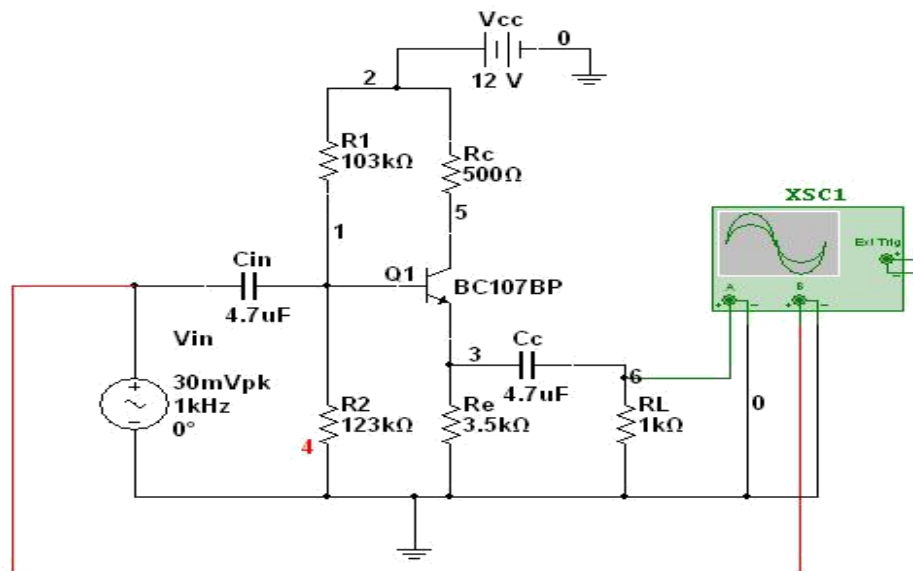
CIRCUIT DIAGRAM:

Fig:4.a Voltage series feedback Amplifier circuit diagram

THEORY:

A voltage series feedback amplifier is a type of feedback amplifier where a portion of the output voltage is fed back to the input in series with the signal source. In this configuration, the feedback is applied in such a way that it stabilizes the gain, reduces distortion, and improves the bandwidth of the amplifier. The feedback network typically consists of resistors or a combination of resistors and capacitors, and it is designed to ensure that the feedback voltage is proportional to the output voltage. This negative feedback lowers the overall gain of the amplifier, but it enhances linearity and reduces the effects of variations in transistor parameters, temperature changes, and power supply fluctuations. Additionally, voltage series feedback improves the input impedance of the amplifier, making it more suitable for interfacing with high-impedance sources, while slightly lowering the output impedance, which aids in better signal transfer to the load.

PROCEDURE:

1. Switch ON the computer and open the multisim software.
2. Check whether the icons of the instruments are activated and enable.
3. Now connect the circuit using the designed values of each and every component.
4. Connect the function generator with sine wave of 50 mV p-p as input at the input of terminals of the circuit.
5. Connect the Cathode Ray Oscilloscope (CRO) to the out put terminals of the circuit.
6. Go to simulation button click it for simulation process.
7. From the CRO note the following values
 1. Input voltage $V_i =$
 2. Output voltage $V_0 =$
 3. Voltage gain $A_v = V_0/V_i =$
 4. Phase shift $\theta =$
8. To study the frequency response click the AC analysis, so that a screen displays the following options
 1. Start frequency
 2. Stop frequency
 3. Vertical scale
9. Assign the proper values for start frequency, stop frequency and vertical scale according to the circuit requirements and observe the frequency response.
10. From the frequency response calculate the


maximum gain $A_{V_{max}} =$

lower cutoff frequency (f_1) at $A_{V_{max}} - 3\text{dB}$ (decibel scale) value


at $A_{V_{\max}}/\sqrt{2}$ (linear scale) =

Higher cutoff frequency (f2) at $A_{V_{\max}} - 3\text{dB}$ (decibel scale) value

at $A_{V_{\max}}/\sqrt{2}$ (linear scale) =

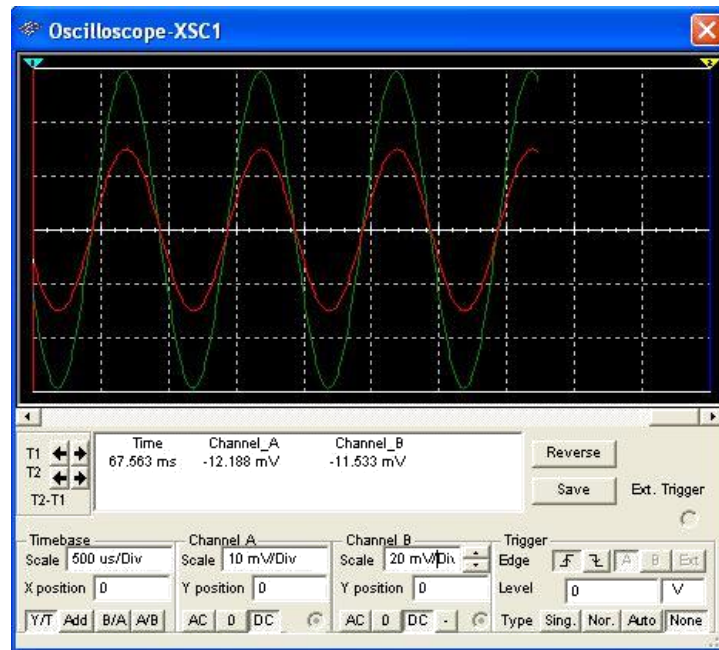OBSERVATIONS:**From CRO:****Fig: 4b Output waveform of voltage series feedback Amplifier**

1. Input voltage $V_i =$
2. Output voltage $V_o =$
3. Voltage gain $A_v = V_o/V_i =$
4. Phase shift $\theta =$

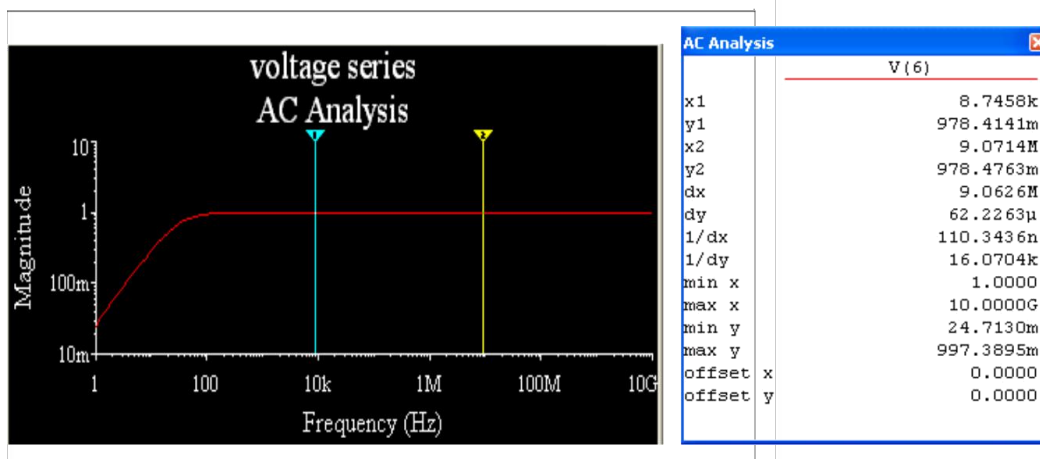From Frequency response:**Fig:4.c Frequency response of Voltage series feedback Amplifier**

RESULT: -

1. Maximum gain $A_{V_{max}}$ =
2. Lower cutoff frequency(f_1) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value
at $A_{V_{max}}/\sqrt{2}$ (linear scale) =
3. Higher cutoff frequency(f_2) at $A_{V_{max}}-3\text{dB}$ (decibel scale)
value at $A_{V_{max}}/\sqrt{2}$ (linear scale) =

APPLICATIONS:

1. Voltage series feedback ($A_f = V_o/V_s$) –Voltage amplifier.
2. Voltage shunt feedback ($A_f = V_o/I_s$) –Trans-resistance amplifier.
3. Current series feedback ($A_f = I_o/V_s$) -Trans-conductance amplifier.
4. Current shunt feedback ($A_f = I_o/I_s$) -Current amplifier.

EXPT NO: 4**VOLTAGE SERIES FEED BACK AMPLIFIER (HARDWARE)**

AIM: To study the frequency response of amplifier, calculate voltage gain and bandwidth from the response.

APPARATUS :

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	1
	(c) Capacitors	4.7 μ F	2
	(d) Resistors	100K Ω ,500 Ω	1
		3.5K Ω ,1K Ω	1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

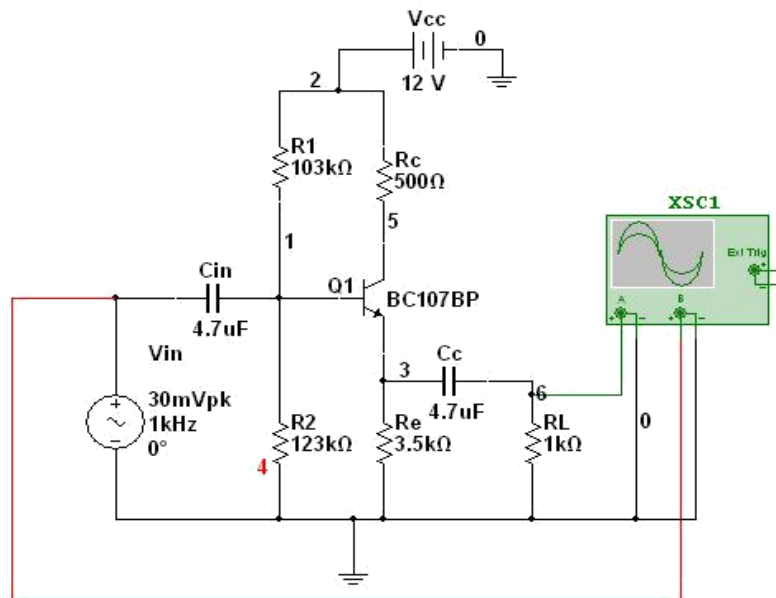
CIRCUIT DIAGRAM:

Fig: 4.e: Voltage series feedback Amplifier circuit diagram

PROCEDURE: -

1. Connect the circuit diagram as shown in figure.
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, vary the input signal frequency from 0 to 1MHz in steps as shown in tabular column and note the corresponding output voltages.

PRECAUTIONS:

Avoid loose connections and give proper input Voltage

TABULAR COLUMN :

Input $V_i = 50\text{mV}$

Frequency(Hz)	Output voltage V_o	Gain $= V_o / V_i$	Gain in dB $= 20\log(V_o / V_i)$
50Hz			
100Hz			
1KHz			
10KHz			
50KHz			
100KHz			
500KHz			
1MHz			

RESULT: -

3. Frequency response of Voltage series feedback Amplifier graph is plotted.
4. Gain = _____ dB (maximum).
5. Bandwidth $= f_H - f_L =$ _____ Hz.

VIVA QUESTIONS:

1. State the merits and demerits of negative feedback in amplifiers.
2. If the bypass capacitor C_E in an RC coupled amplifier becomes accidentally open circuited, what happens to the gain of the amplifier? Explain.
3. When will a negative feedback amplifier circuit be unstable?
4. What is the parameter which does not change with feedback?
5. What type of feedback has been used in an emitter follower circuit?
6. Define voltage series feedback amplifier?
7. Draw the voltage series feedback amplifier?
8. When will a negative feedback amplifier circuit be unstable?
9. What is the parameter which does not change with feedback?
10. What type of feedback has been used in an emitter follower circuit?
11. Transistor when it is working as an amplifier?
12. Why frequency response of the amplifier is drawn on semi-log scale graph?
13. If Q point is not properly selected, then what will be the effect on the output waveform?
14. What is active region?
15. Why is common base configuration used as current buffer even though it has properties of current amplifier?
16. What does the current shunt feedback amplifier amplify? And how?
17. If the bypass capacitor C_E in an RC coupled amplifier becomes accidentally open circuited,
18. What happens to the gain of the amplifier? Explain.
19. Transistor when it is working as an amplifier?
20. Why frequency response of the amplifier is drawn on semi-log scale graph?
21. If Q point is not properly selected, then what will be the effect on the output waveform?
22. What is active region?
23. What is Bandwidth of an amplifier?
24. Plot the amplitude response of BC 107 amplifier with $R_2 = 5.4 \text{ K}$ i/p.
25. Plot frequency response of BC 107 amplifier $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.
26. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 2 \mu\text{F}$.
27. Plot the frequency response of amplifier with $C_2 = 2 \mu\text{F}$, i/p.
28. Plot the amplitude response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
29. Plot the amplitude response of BC 107 amplifier with $R_2 = 2.4 \text{ K}$ i/p.
30. Plot frequency response of $R_1 = 2.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.

EXERCISE PROBLEMS:

1. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
2. Plot the frequency response of BC 107 amplifier with $C_2 = 5 \mu\text{F}$ with triangular i/p.
3. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
4. Plot the amplitude response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
5. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
6. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
7. Plot the frequency response of amplifier with $C_2 = 5 \mu\text{F}$, triangular i/p.
8. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.

9. Plot the amplitude response of BC107 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
10. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
11. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \text{ }\mu\text{F}$.
12. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \text{ }\mu\text{F}$ with i/p.
13. Plot the amplitude response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.

EXPT NO: 5**RC PHASE SHIFT OSCILLATOR (Software)****PRELAB:**

1. Study the different types of oscillator and their conditions.
2. Identify all the formulae you will need in this Lab.

OBJECTIVE:


1. To simulate RC phase shift oscillator in Multisim and study the transient response.
2. To determine the phase shift of RC network in the circuit.

SOFTWARE TOOL:

Multisim v 13.0

APPARATUS:

- | | | |
|--|---|------------|
| 1. Regulated power supply | - | 1 No. |
| 2. Function generator | - | 1 No. |
| 3. CRO | - | 1 No. |
| 4. Transistor (BC 107 or 2N2222) | - | 2 No. |
| 5. Resistors (47 K Ω , 2.2 K Ω , 1k) | - | 1 No. each |
| 6. Resistor (10 K Ω) | - | 3 Nos. |
| 7. Capacitors (10 μ F, 100 μ F) | - | 1No. each |
| (1nf,or 10nf) | - | 3 No. |

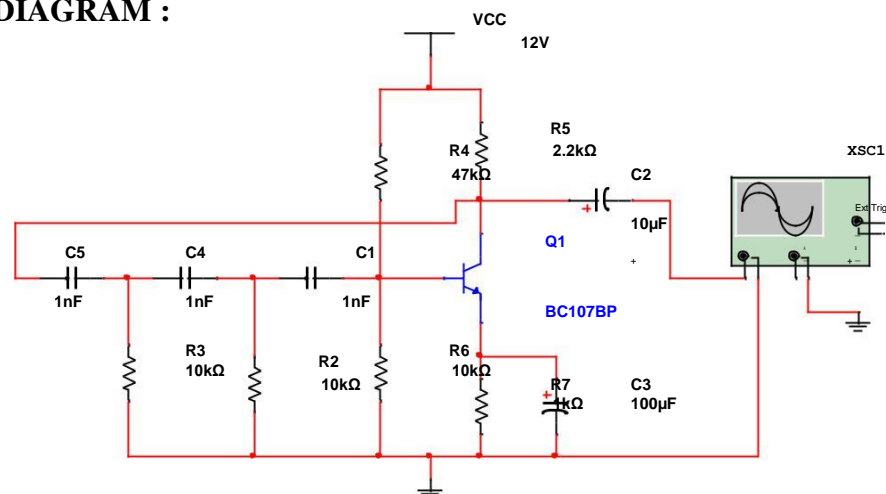CIRCUIT DIAGRAM :**Fig: 5.a RC Phase Shift oscillator circuit diagram**

THEORY:

An RC phase shift oscillator is a type of sinusoidal oscillator that generates continuous waveforms at a specific frequency determined by the components in the circuit. It consists of an amplifier, typically a transistor or an operational amplifier, and a feedback network made up of resistors and capacitors arranged in a series of three or more RC stages. Each RC stage shifts the phase of the input signal by 60 degrees, so that the total phase shift around the loop is 180 degrees. The amplifier provides an additional 180-degree phase shift, resulting in a total of 360 degrees, or zero phase shift, necessary for sustained oscillations. The frequency of oscillation is determined by the values of the resistors and capacitors in the feedback network, and it is typically chosen to be in the audio frequency range. RC phase shift oscillators are known for their simplicity and are commonly used in low-frequency applications, such as audio signal generators. However, they typically provide less frequency stability compared to other types of oscillators, like crystal oscillators.

PROCEDURE:

1. Open Multisim Software to design RC Phase shift oscillator
2. Select on New editor window and place the required component on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Observe the Transient Response and Calculate the Frequency of the oscillator

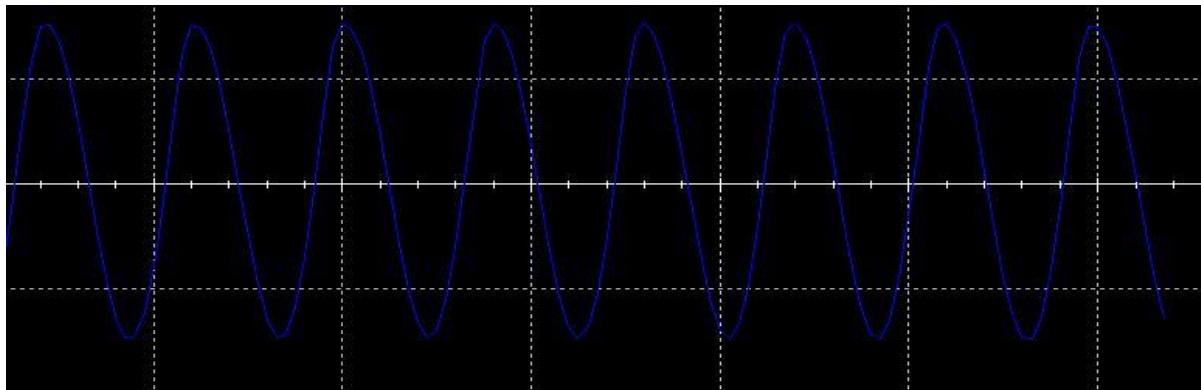
OBSERVATIONS/GRAPHS:**TRANSIENT RESPONSE:**

Fig: 5.b : Transient response of RC Phase Shift oscillator

RESULT:

1. For $C = 0.0022 \text{ F}$ & $R = 10\text{K}$
 - i. Theoretical frequency=
 - ii. Practical frequency=
2. For $C = 0.0033 \text{ F}$ & $R = 10\text{K}$
 - i. Theoretical frequency=
 - ii. Practical frequency=

3. For $C = 0.01 \text{ F}$ & $R = 10\text{K}$
 - i. Theoretical frequency=
 - ii. Practical frequency=

The frequency of oscillations of RC phase shift oscillator is calculated compared the theoretical and practical values.

APPLICATIONS:

FET phase-shift oscillator is used for generating signals over a wide frequency range. The frequency may be varied from a few Hz to 200 Hz by employing one set of resistor with three capacitors ganged together to vary over a capacitance range in the 1 : 10 ratio.

EXP NO:5**RC PHASE SHIFT OSCILLATOR (Hardware)****AIM:**

Find practical frequency of RC phase shift oscillator and to compare it with theoretical frequency for $R=10K$ and $C = 0.01 F, 0.0022 F \text{ \& } 0.0033 F$ respectively

COMPONENTS AND EQUIPMENTS REQUIRED:

S.No	Device	Range/ Rating	Qty
1	a) DC supply voltage	12V	1
	b) Capacitor	100 F	1
		10 F	2
	c) Resistor	10K ,5.6K	2
		22K ,100K	3
		1K ,	3
	d) NPN Transistor	BC 107	1
2	CRO	(0-20) MHz	1
3.	BNC Connector		1
3	Connecting wires	5A	6

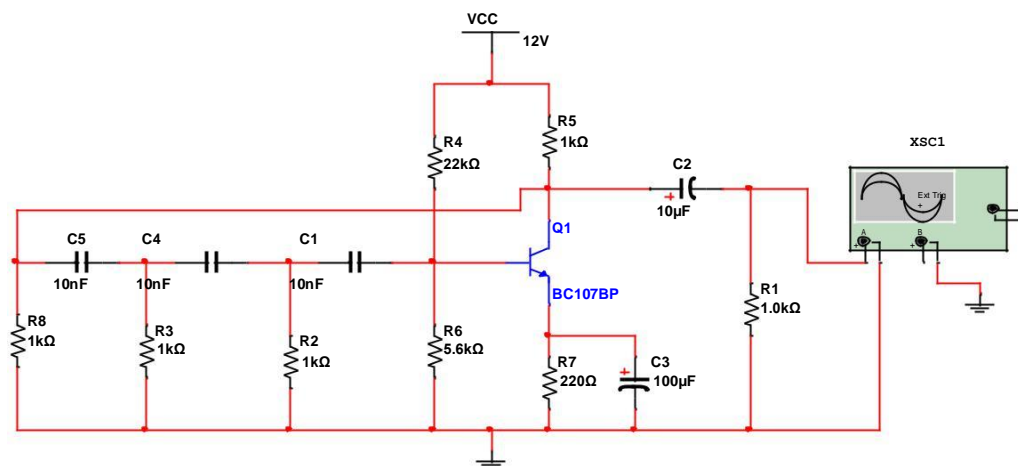
CIRCUIT DIAGRAM:

Fig. 5. c: Circuit diagram of RC Phase Shift oscillator

PROCEDURE:

1. Connect the circuit as shown in figure.
2. Connect the 0.0022 F capacitors in the circuit and observe the waveform.
3. Time period of the waveform is to be noted and frequency should be calculated by the formula $f = 1/T$.
4. Now fix the capacitance to 0.0033 F and 0.01 F and calculate the frequency and tabulate as shown.
5. Find theoretical frequency from the formula $f = \frac{1}{2\pi RC\sqrt{6}}$ and compare theoretical and practical frequencies.

PRECAUTIONS: -

No loose contacts at the junctions.

TABULAR COLUMN:

S.No	C (F)	R ()	Theoretical Frequency (KHz)	Practical Frequency (KHz)	V _o (p-p) (Volts)
1	10nf	1k			
2	1nf	1K			
3	10n	10K			

RESULT: -

1. For C = 0.0022 F & R=10K
 - i. Theoretical frequency=
 - ii. Practical frequency=
2. For C = 0.0033 F & R=10K
 - i. Theoretical frequency=
 - ii. Practical frequency=
3. For C = 0.01 F & R=10K
 - i. Theoretical frequency=
 - ii. Practical frequency=

VIVA QUESTIONS:

1. What are the conditions of oscillations?
2. Give the formula for frequency of oscillations?
3. What is the total phase shift produced by RC ladder network?
4. What are the types of oscillators?

5. What is the gain of RC phase shift oscillator?
6. What is the frequency of RC phase shift oscillator?
7. What is a phase shift oscillator?
8. Why RC oscillators cannot generate high frequency oscillations?
9. What are the applications of RC phase shift oscillators?
10. What phase shift does RC phase shift oscillator produce?
11. Why we need a phase shift between input and output signal?
12. How is phase angle determined in RC phase shift oscillator?
13. How can we get a maximum phase angle of 90 degrees in RC phase shift oscillator?
14. What is an Oscillator?.
15. Which feedback used in oscillators?
16. What is the output of an oscillator if transistor is ideal?
17. What are LC oscillators?
18. Why can't we use LC oscillator for low frequency oscillations?
19. How an oscillator generates oscillations without any input?
20. Classify oscillators?
21. Plot the Amplitude response of 2N3904 Oscillator with $C_1 = 5 \mu\text{F}$.
22. Plot the Amplitude response of 2N2222 Oscillator $C_2 = 5 \mu\text{F}$ with i/p.
23. Plot the Amplitude response of BC107 Oscillator with $R_1 = 4.1 \text{ K}$.
24. Plot the Amplitude response of BC 547 Oscillator with $R_2 = 9.4 \text{ K}$ i/p.
25. Plot the Amplitude response of BC 548 Oscillator $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
26. Plot the Amplitude response of BC 557 Oscillator with $C_1 = 5 \mu\text{F}$.
27. Plot the Amplitude response of BC 547 Oscillator with $C_2 = 5 \mu\text{F}$, i/p.
28. Plot the Amplitude response of 2N3904 Oscillator with $R_1 = 4.1 \text{ K}$.
29. Plot the Amplitude response of 2N3904 Oscillator with $R_2 = 9.4 \text{ K}$ i/p.
- 30.** Plot the Amplitude response of 2N3904 Oscillator $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.

EXP NO: 6 A**HARTLEY OSCILLATOR (SOFTWARE)****PRELAB:**

Study the operation and working principle Hartley oscillator.

OBJECTIVE:

To design Hartley oscillator using Multisim software and calculate the frequency

APPARATUS:

1. Transistor – BC 107
2. Resistors – 1K, 5K, 10K, 100K,
3. Capacitors – 100nF(3), 10nF
4. Inductor-10mH or 1mH.
5. RPS
6. CRO
7. Breadboard
8. Connecting wires and probes

SOFTWARE TOOL: Multisim V 13.0

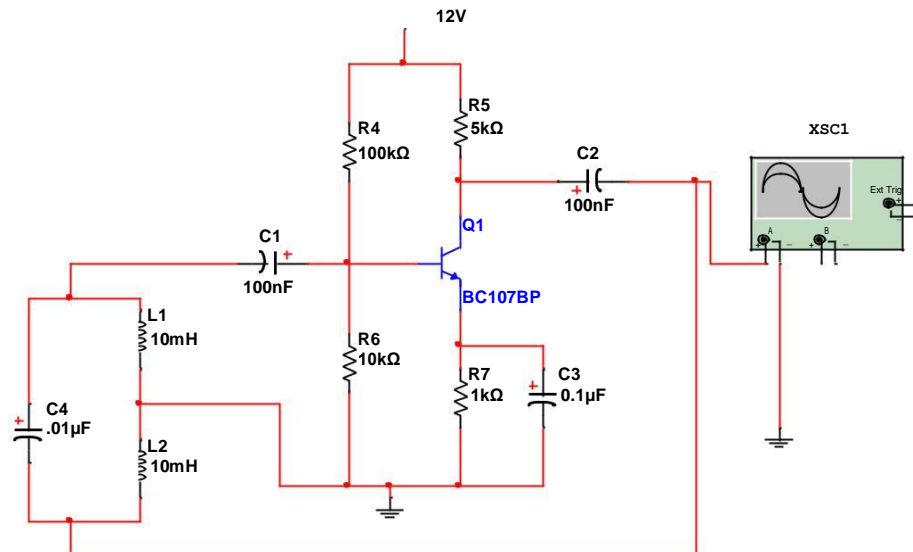
CIRCUIT DIAGRAM:

Fig:6A-a: Hartley oscillator circuit diagram

THEORY:

A Hartley oscillator is a type of LC oscillator that generates sinusoidal waveforms and is commonly used in radio frequency (RF) applications. The circuit consists of an amplifier, typically a transistor or an operational amplifier, and a tuned circuit composed of an inductor split into two sections and a capacitor. The two inductive sections are either separate inductors or a tapped inductor, with the tap point providing the necessary feedback to sustain oscillations.

PROCEDURE:

1. Open Multisim Software to design Hartley oscillator circuit
2. Select on New editor window and place the required component on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Calculate the frequency theoretically and practically.

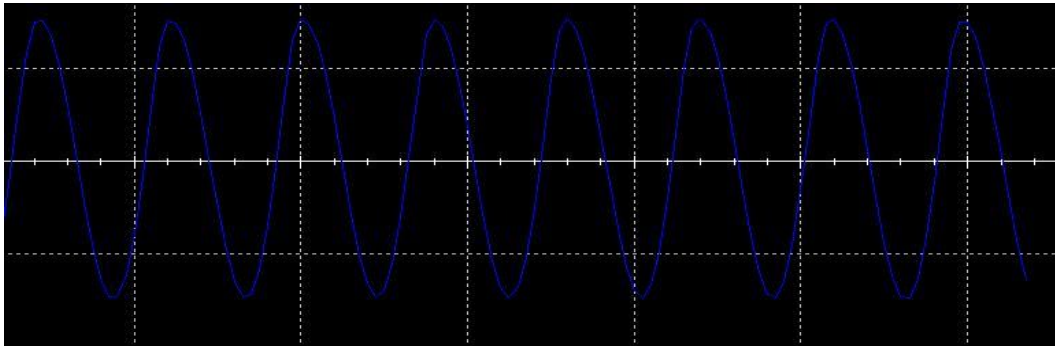
OBSERVATIONS/GRAPHS:

Fig:6A-b: Output waveform of Hartley oscillator

RESULT:

1. Out frequency for $L_1=L_2=10\text{mH}$, $C=10\text{nf}$ is _____
2. Out frequency for $L_1=L_2=10\text{mH}$, $C=100\text{nf}$ is _____
3. Out frequency for $L_1=L_2=20\text{mH}$, $C=10\text{nf}$ is _____
4. Out frequency for $L_1=5$, $L_2=10\text{mH}$, $C=10\text{nf}$ is _____

APPLICATIONS:

1. The Hartley oscillator is to produce a sine wave with the desired frequency.
2. Hartley oscillators are mainly used as radio receivers. Also note that due to its wide range of frequencies, it is the most popular oscillator.
3. The Hartley oscillator is Suitable for oscillations in RF (Radio-Frequency) range, up to 30MHZ.

EXP NO: 6 A**HARTLEY OSCILLATOR (HARDWARE)****AIM:**

Find practical frequency of a Hartley oscillator and to compare it with theoretical frequency for $L = 10\text{mH}$ and $C = 0.01\text{ F}$, 0.033 F and 0.047 F .

COMPONENTS AND EQUIPMENTS REQUIRED:

S.No	Device	Range/Rating	Quantity
1	a) DC supply voltage	12V	1
	b) Inductors	5mH	2
	c) Capacitor	0.01 F, 0.022 F; 0.033 F	1
		0.047 F	1
	d) Resistor	1K ,10K ,47K	1
	e) NPN Transistor	BC 107	1
2	Cathode Ray Oscilloscope	(0-20) MHz	1
3.	BNC Connector		1
4	Connecting wires	5A	4

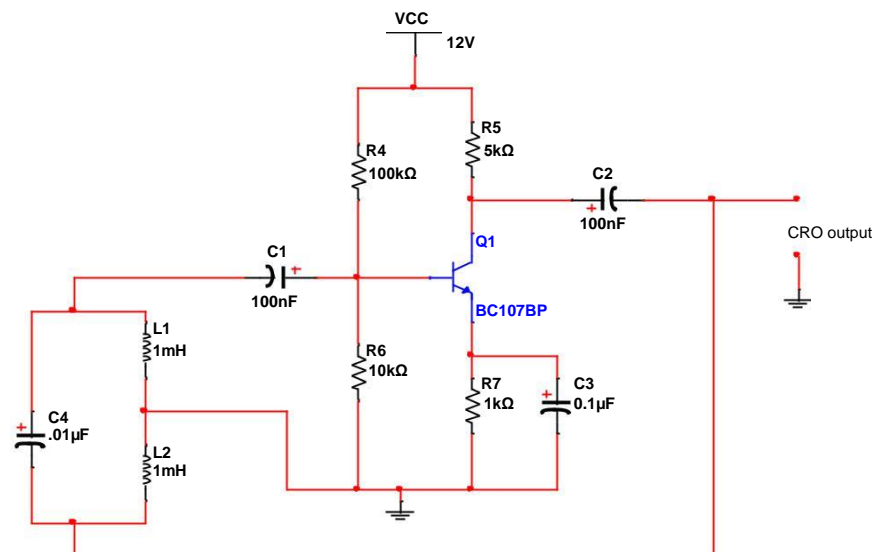
CIRCUIT DIAGRAM:

Fig: 6A.c: Hartley oscillator circuit diagram

PROCEDURE:

1. Connect the circuit as shown in figure.
2. With 0.1 F capacitor and 20mH in the circuit and observe the waveform.
3. Time period of the waveform is to be noted and frequency is to be calculated by the formula $f = 1/T$.
4. Now fix the capacitance to 0.033 F and 0.047 F and calculate the frequency and tabulate the readings as shown.
5. Find the theoretical frequency by using below formula

$$f = \frac{1}{2\pi\sqrt{L_T C}}$$

where $L_T = L_1 + L_2 = 5\text{mH} + 5\text{mH} = 10\text{mH}$

PRECAUTIONS: No loose contacts at the junctions.

TABULATIONS:

S.No	$L_T(\text{mH})$	C (F)	Theoretical frequency (KHz)	Practical frequency (KHz)	V_o (peak to peak)
1	10	0.01			
2	10	0.033			
3	10	0.047			

RESULT:

1. For $C = 0.01 \text{ F}$, & $L_T = 10 \text{ mH}$;
Theoretical frequency
= Practical frequency =
2. For $C = 0.033 \text{ F}$, & $L_T = 10 \text{ mH}$;
Theoretical frequency =
Practical frequency =
3. For $C = 0.047 \text{ F}$, & $L_T = 10 \text{ mH}$;
Theoretical frequency =
Practical frequency =

APPLICATIONS:

1. It is used for generation of sinusoidal output signals with very high frequencies.
2. The Colpitts oscillator using SAW device can be used as the different type of sensors such as temperature sensor. As the device used in this circuit is highly sensitive to perturbations, it senses directly from its surface.
3. It is frequently used for the applications in which very wide range of frequencies are involved.

VIVA QUESTIONS:

1. Give the difference between Hartley and colpitts oscillator.
2. Classification of oscillators.
3. Give an example for LC oscillator.
4. Which phenomenon is employed for colpitts oscillator?
5. Give the applications of oscillator.
6. Define barkhausen criteria
7. Which type of feedback is employed in oscillators
8. Give applications for oscillators
9. What is the condition for sustained oscillations
10. Draw an oscillator circuit with feedback network given below.
11. What is the principle behind operation of a colpits oscillator?
12. What are the advantages and disadvantages of *colpits* oscillators?
13. Mention two essential conditions for a circuit to maintain oscillations?
14. Define an oscillator?
15. Define barkhausen criteria
16. Which type of feedback is employed in oscillators
17. Give applications for oscillators
18. What is an Oscillator?
19. Which feedback used in oscillators?
20. Classify oscillators?
21. Which oscillators are AF oscillators?
22. Draw an oscillator circuit with feedback network given below.
23. What is the principle behind operation of a colpitts oscillator?
24. What are the advantages and disadvantages of colpitts oscillators?
25. Mention two essential conditions for a circuit to maintain oscillations?
26. Define an oscillator?
27. Define barkhausen criteria
28. What are RC oscillators?
29. Mention two essential conditions for a circuit to maintain oscillations?
30. Define an oscillator?

EXERCISE PROBLEMS:

1. Plot the Amplitude response of 2N3904 Oscillator with $C_1 = 5 \mu\text{F}$.
2. Plot the Amplitude response of 2N2222 Oscillator $C_2 = 5 \mu\text{F}$ with i/p.
3. Plot the Amplitude response of BC107 Oscillator with $R_1 = 4.1 \text{ K}$.
4. Plot the Amplitude response of BC 547 Oscillator with $R_2 = 9.4 \text{ K}$ i/p.
5. Plot the Amplitude response of BC 548 Oscillator $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
6. Plot the Amplitude response of BC 557 Oscillator with $C_1 = 5 \mu\text{F}$.
7. Plot the Amplitude response of BC 547 Oscillator with $C_2 = 5 \mu\text{F}$, i/p.
8. Plot the Amplitude response of 2N3904 Oscillator with $R_1 = 4.1 \text{ K}$.
9. Plot the Amplitude response of 2N3904 Oscillator with $R_2 = 9.4 \text{ K}$ i/p.
10. Plot the Amplitude response of 2N3904 Oscillator $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
11. Plot the Amplitude response of 2N3904 Oscillator with $C_1 = 10 \mu\text{F}$.
12. Plot the Amplitude response of CL100 Oscillator with $C_2 = 2 \mu\text{F}$ with i/p.
13. Plot the Amplitude response of CL 100 Oscillator with $R_1 = 2.1 \text{ K}$.
14. Plot the Amplitude response of CK 100 Oscillator with $R_2 = 5.4 \text{ K}$ i/p.
15. Plot the Amplitude response of 2N3904 Oscillator $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.
16. Plot the Amplitude response of 2N3904 Oscillator with $C_1 = 2 \mu\text{F}$.
17. Plot the Amplitude response of 2N3904 Oscillator with $C_2 = 2 \mu\text{F}$, i/p.
18. Plot the Amplitude response of 2N3904 Oscillator with $R_1 = 2.1 \text{ K}$.
19. Plot the Amplitude response of SL100 Oscillator with $R_2 = 2.4 \text{ K}$ i/p.
20. Plot the Amplitude response of 2N3904 Oscillator $R_1 = 2.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
21. Plot the Amplitude response of 2N3904 Oscillator with $C_1 = 5 \mu\text{F}$.
22. Plot the Amplitude response of 2N3904 Oscillator with $C_2 = 5 \mu\text{F}$ with i/p.
23. Plot the Amplitude response of 2N3904 Oscillator with $R_1 = 4.1 \text{ K}$.
24. Plot the Amplitude response of 2N3904 Oscillator with $R_2 = 9.4 \text{ K}$ i/p.
25. Plot the Amplitude response of 2N3904 Oscillator $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.

EXP NO: 6.B**COLPITTS OSCILLATOR (software)****PRELAB:**

Study the operation and working principle Colpitts oscillator.

OBJECTIVE:

To design Colpitts oscillator using Multisim software and calculate the frequency

APPARATUS:

1. Transistor – BC 107
2. Resistors – 1K, 5K, 10K, 100K,
3. Capacitors – 100nF(3), 10nF
4. RPS
5. CRO
6. Breadboard
7. Connecting wires and probes

SOFTWARE TOOL:

Multisim

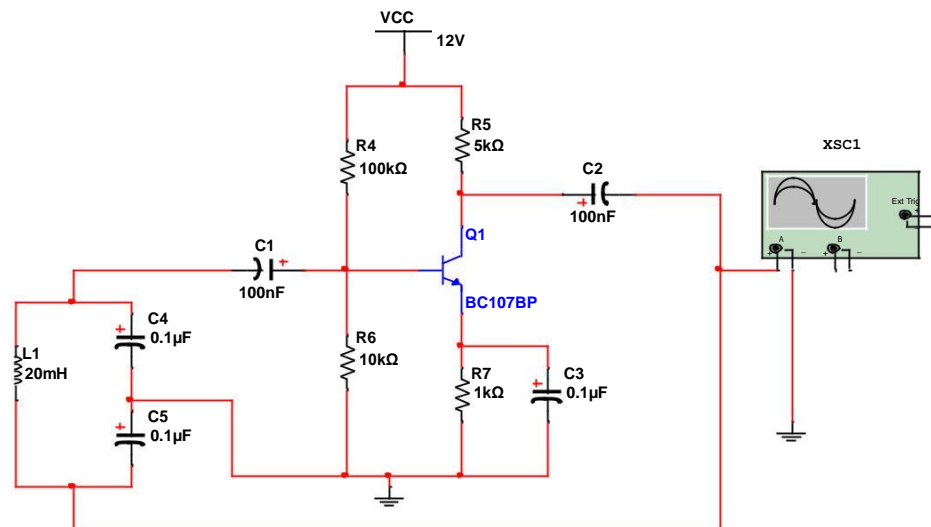
CIRCUIT DIAGRAM:

Fig:6B.a.Colpitts oscillator circuit diagram

THEORY:

A Colpitts oscillator is a type of LC oscillator that generates sinusoidal oscillations and is widely used in high-frequency applications such as RF signal generation. The key feature of the Colpitts oscillator is its use of a capacitive voltage divider as part of the feedback network. The circuit consists of an amplifier, typically a transistor or an operational amplifier, and an LC tank circuit that includes a single inductor and two capacitors connected in series, forming the capacitive voltage divider. The junction between the two capacitors is connected to the input of the amplifier to provide the necessary feedback.

PROCEDURE:

1. Open Multisim Software to design Colpitts oscillator circuit
2. Select on New editor window and place the required component on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Calculate the frequency theoretically and practically

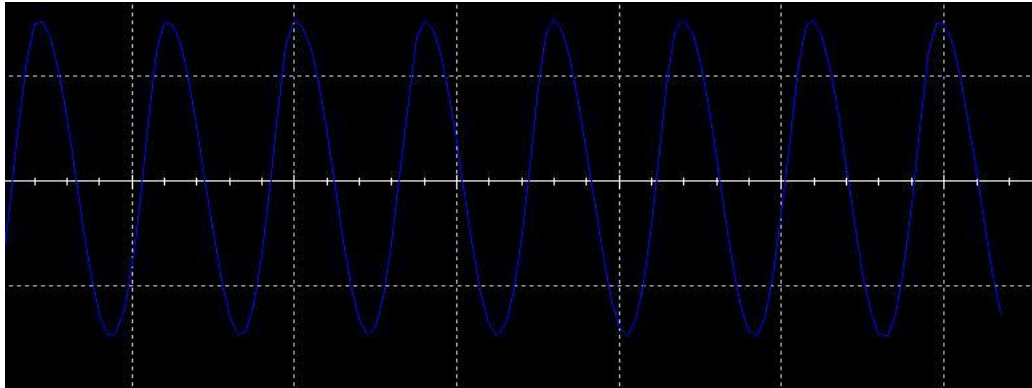
OBSERVATIONS/GRAPHS:

Fig:6B.b.Output waveform of Colpitts oscillator

RESULT: -

1. Out frequency for $L1 = 10\text{mH}$, $C1=C2=10\text{nf}$ is _____
2. Out frequency for $L1 = 10\text{mH}$, $C1=C2=100\text{nf}$ is _____
3. Out frequency for $L1 = 20\text{mH}$, $C1=C2=10\text{nf}$ is _____
4. Out frequency for $L1 = 10\text{mH}$, $C1=10\text{nf}$, $C2=100\text{nf}$ _____

APPLICATIONS:

1. It is used for generation of sinusoidal output signals with very high frequencies.


2. The Colpitts oscillator using SAW device can be used as the different type of sensors such as temperature sensor. As the device used in this circuit is highly sensitive to perturbations, it senses directly from its surface.
3. It is frequently used for the applications in which very wide range of frequencies are involved.

EXP NO: 6 B**COLPITTS OSCILLATOR(HARDWARE)****AIM:**

Find practical frequency of Colpitt's oscillator and to compare it with theoretical Frequency for $L = 5\text{mH}$ and $C = 0.001\text{ F}, 0.0022\text{ F}, 0.0033\text{ F}$ respectively.

COMPONENTS & EQUIPMENT REQUIRED: -

S.No	Device	Range/Rating	Quantity
1	a) DC supply voltage	12V	1
	b) Inductors	5mH	1
	c) Capacitor	0.01 F, 0.01 F, 100 F	1
	d) Resistor	1K , 10K , 47K	1
	e) NPN Transistor	BC 107	1
2	Cathode Ray Oscilloscope	(0-20) MHz	1
3.	BNC Connector		1
4	Connecting wires	5A	4

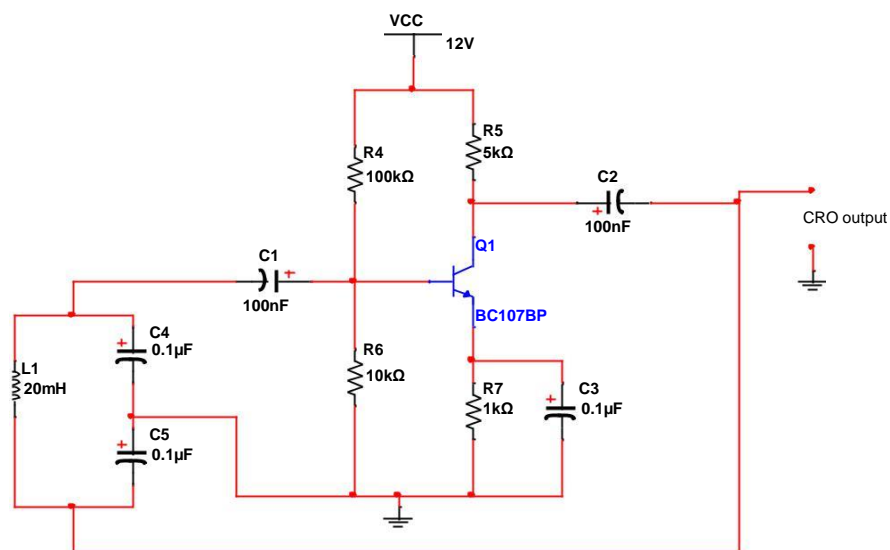CIRCUIT DIAGRAM:**Fig: 6B.C: Colpitts oscillator circuit diagram**

PROCEDURE:-

1. Connect the circuit as shown in the figure
2. Connect $C_2 = 0.001$ F in the circuit and observe the waveform.
3. Time period of the waveform is to be noted and frequency should be calculated by the formula $f = 1/T$
4. Now, fix the capacitance to 0.002 F and then to 0.003 F and calculate the frequency and tabulate the reading as shown.
5. Find the theoretical frequency by using below formula

$$f = \frac{1}{2\pi\sqrt{C_{eq}L}}$$

where $C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$

PRECAUTIONS:-

1. No loose connections at the junctions.

TABULAR COLUMN:

S.NO	L(mH)	C ₁ (F)	C ₂ (F)	C _T (F)	Theoretical Frequency (KHz)	Practical Frequency (KHz)	Vo(V) Peak to peak
1	1mH	.1u	0.1u				
2	1mH	0.01u	0.1u				
3	1mH	0.01	0.0iu				

RESULT:

1. For $C = 0.01$ F, 0.1uf & $L = 1$ mH

Theoretical frequency =

Practical frequency =

2. For $C = 0.1$ F, 0.1uf & $L = 1$ mH

3. For $C = 0.01$ F, 0.01uf & $L = 5$ mH

Theoretical frequency =

Practical frequency =

Frequency of oscillations of Colpitt's oscillator is measured practically and compared with theoretical values .

APPLICATIONS:

- i. The Hartley oscillator is to produce a sine wave with the desired frequency
- ii. Hartley oscillators are mainly used as radio receivers. Also note that due to its wide range of frequencies, it is the most popular oscillator
- iii. The Hartley oscillator is Suitable for oscillations in RF (Radio-Frequency) range, up to 30MHZ

VIVA QUESTIONS:

1. Define an oscillator?
2. Define barkhausen criteria
3. Which type of feedback is employed in oscillators
4. Give applications for oscillators
5. What is the condition for sustained oscillations
6. Draw an oscillator circuit with feedback network given below.
7. What is the principle behind operation of a *HARTLEY* oscillator?
8. What are the advantages and disadvantages of *HARTLEY* oscillators?
9. Mention two essential conditions for a circuit to maintain oscillations[
10. Define an colpits oscillator?
11. Define barkhausen criteria
12. Which type of feedback is employed in oscillators
13. Give applications for oscillators
14. Which feedback used in oscillators?
15. Classify oscillators?
16. Which oscillators are AF oscillators?
17. Draw an oscillator circuit with feedback network given below.
18. What are the applications of LC oscillator?
19. What type of feedback is used in oscillators?
20. What is the loop gain of an oscillator?
21. What is the difference between amplifier and oscillator?
22. Plot the Amplitude response of BC 547 Oscillator with $C_2 = 5 \mu\text{F}$, i/p.
23. Plot the Amplitude response of 2N3904 Oscillator with $R_1 = 4.1 \text{ K}$.
24. Plot the Amplitude response of 2N3904 Oscillator with $R_2 = 9.4 \text{ K}$ i/p.
25. Plot the Amplitude response of 2N3904 Oscillator $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
26. Plot the Amplitude response of 2N3904 Oscillator with $C_1 = 10 \mu\text{F}$.
27. Plot the Amplitude response of CL100 Oscillator with $C_2 = 2 \mu\text{F}$ with i/p.
28. Plot the Amplitude response of CL 100 Oscillator with $R_1 = 2.1 \text{ K}$.
29. Plot the Amplitude response of CK 100 Oscillator with $R_2 = 5.4 \text{ K}$ i/p.
30. Plot the Amplitude response of 2N3904 Oscillator $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.

EXERCISE PROBLEMS:

1. Plot the Amplitude response of 2N3904 Oscillator with $C_1 = 5 \mu\text{F}$.
2. Plot the Amplitude response of 2N2222 Oscillator $C_2 = 5 \mu\text{F}$ with i/p.
3. Plot the Amplitude response of BC107 Oscillator with $R_1 = 4.1 \text{ K}$.
4. Plot the Amplitude response of BC 547 Oscillator with $R_2 = 9.4 \text{ K}$ i/p.
5. Plot the Amplitude response of BC 548 Oscillator $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
6. Plot the Amplitude response of BC 557 Oscillator with $C_1 = 5 \mu\text{F}$.

EXP NO:7**CLASS A POWER AMPLIFIER (Transformer less) (SOFTWARE)**

AIM: To calculate the efficiency of Class A power amplifier.

SOFTWARE TOOL:

Multisim V 13.0

APPARATUS REQUIRED:

- | | |
|--|--------|
| 1. Function generator | |
| 2. Regulated power supply (0 - 30V) | |
| 3. CRO (0-20MHz) | - 1No |
| 4. Transistor (SL - 100) | - 1No. |
| 5. Resistors (20 K Ω , 100 Ω) | - 1No. |
| 6. Capacitor (10 μ F) | - 1No. |

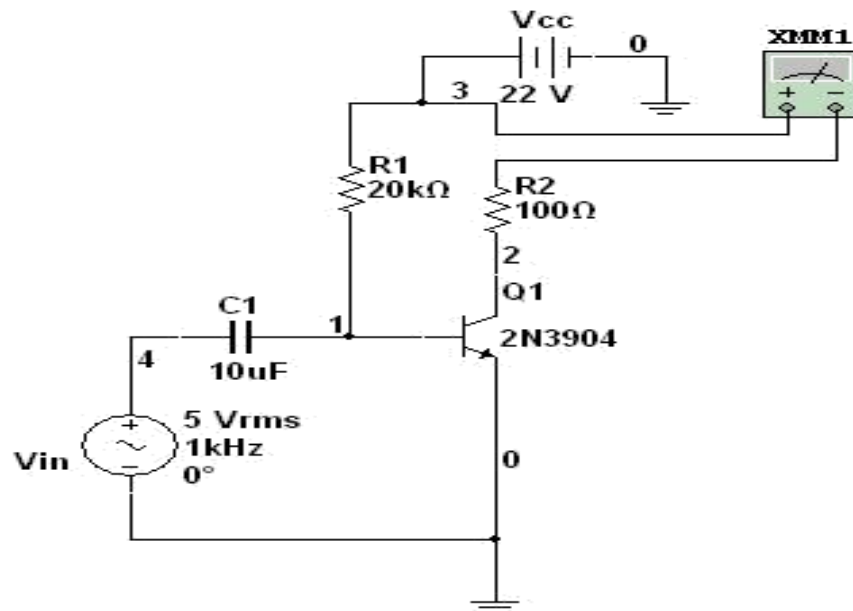
CIRCUIT DIAGRAM:


Fig 7.a: ClassA power amplifier circuit diagram

THEORY:

A Class A power amplifier is a type of amplifier that operates with the output transistor conducting for the entire cycle of the input signal, meaning it is always "on." This mode of operation results in high linearity, making Class A amplifiers ideal for applications where signal fidelity is crucial, such as in high-quality audio amplification. The continuous conduction ensures that the output is a faithful reproduction of the input signal, with minimal distortion. However, this comes at the cost of efficiency; Class A amplifiers are typically only 20-30% efficient, as the transistor dissipates a significant amount of power as heat even when no input signal is present. To manage the heat generated, Class A amplifiers often require large heatsinks. Despite their low efficiency, Class A amplifiers are valued in applications where the quality of the amplified signal is more important than power efficiency, providing a pure, undistorted output with excellent linearity across the entire frequency range.

PROCEDURE:

1. Connect the circuit as per the diagram.
2. Connect the function generator with sine wave of 0.3 V p-p as input at the input terminals of the circuit.
3. Note down the multi meter readings across the RL resistor. (V_{ac} and I_{dc})
4. Calculate the efficiency.

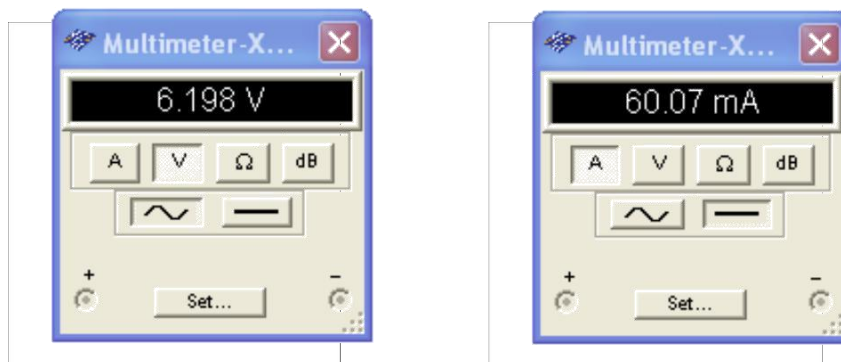OBSERVATIONS:

From multimeter

$$V_{ac} = \underline{\hspace{2cm}} \text{ V}$$

$$I_{ac} = \underline{\hspace{2cm}} \text{ mA}$$

Calculations:

$$P_{dc} = V_{CC} \times I_{dc} =$$

$$P_{ac} = V_{ac}^2 / R_L =$$

$$efficiency \frac{P_{ac}}{P_{dc}} \times 100 =$$

EXP NO -7**CLASS A POWER AMPLIFIER (Transformer less) (Hardware)**

AIM: To calculate the efficiency of Class A power amplifier.

COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	CL100	1
	(c) Capacitors	100 μ F	1
	(d) Resistors	22K Ω , 1K Ω	1
		5.6K Ω	1
		,100 Ω ,50 Ω	1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

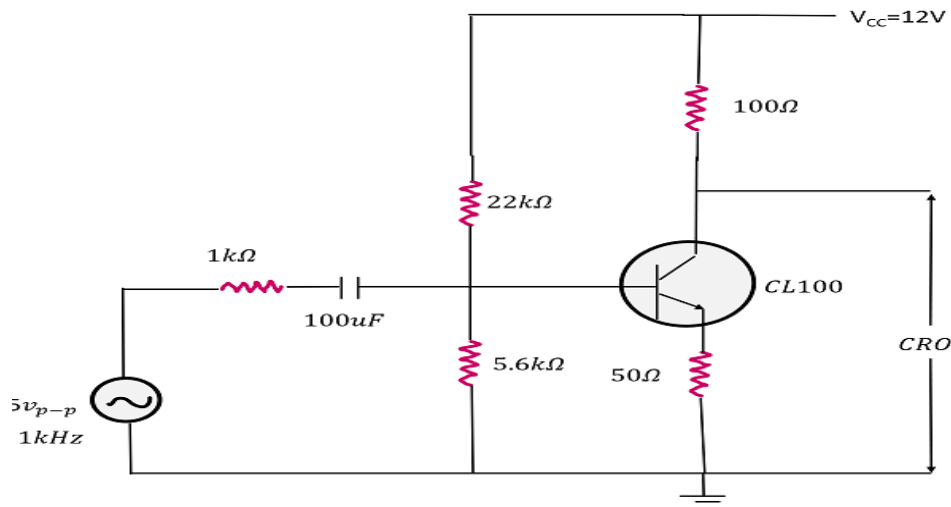
CIRCUIT DIAGRAM:

Fig: 7.B Class A power amplifier circuit diagram

PROCEDURE:

1. Connect the circuit as per the diagram.
2. Connect the function generator with sine wave of 0.3 V p-p as input at the input terminals of the circuit.
3. Note down the multi meter readings across the R_L resistor. (V_{ac} and I_{dc})
4. Calculate the efficiency.

OBSERVATIONS:

From Multimeter

$$V_{ac} = \underline{\hspace{2cm}} \quad V$$

$$I_{dc} = \underline{\hspace{2cm}} \quad mA$$

Calculations:

$$P_{dc} = V_{CC} \times I_{dc} =$$

$$P_{ac} = V_{ac}^2 / R_L =$$

$$\text{Efficiency } \eta = (P_{ac} / P_{dc}) * 100$$

RESULT: The efficiency of Class A power amplifier is calculated.

APPLICATIONS:

- a. The Class A Amplifier more suitable for outdoor musical systems, since the transistor reproduces the entire audio waveform without ever cutting off. As a result, the sound is very clear and more linear, that is, it contains much lower levels of distortion.
- b. They are usually very large, heavy and they produce nearly 4-5 watts of heat energy per a watt of output. Therefore, they run very hot and need lots of ventilation. So they are not at all ideal for a car and rarely acceptable in a home.

VIVA QUESTIONS:

1. Differentiate between voltage amplifier and power amplifier?
2. Why power amplifiers are considered as large signal amplifier?
3. When does maximum power dissipation happen in this circuit?
4. What is the maximum theoretical efficiency?
5. Sketch wave form of output current with respective input signal.
6. What are the different types of class-A power amplifiers available?
7. What is the theoretical efficiency of the transformer coupled class-A power amplifier?
8. What is difference in AC, DC load line?
9. How do you locate the Q-point?
10. What are the applications of class-A power amplifier?
11. Define class A power amplifier?
12. Give the reason why class A power amplifier is called as directly coupled power amplifier?
13. What is the efficiency of class A power amplifier?
14. In class-A power amplifier, when the maximum power dissipation takes place in the transistor?
15. List out the different types of distortions? 6. Define Harmonic distortion?
16. What are Class B, Class C and Class AB amplifiers and which type is used for what application?
17. Differentiate between voltage amplifier and power amplifier
18. Why power amplifiers are considered as large signal amplifier?
19. What is the theoretical efficiency of the transformer coupled class-A power amplifier?
20. Sketch wave form of output current with respective input signal.

21. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
22. Plot the frequency response of BC 107 amplifier with $C_2 = 5 \mu\text{F}$ with triangular i/p.
23. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
24. Plot the amplitude response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
25. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
26. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
27. Plot the frequency response of amplifier with $C_2 = 5 \mu\text{F}$, triangular i/p.
28. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
29. Plot the amplitude response of BC107 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
30. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.

EXERCISE PROBLEMS:

1. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \mu\text{F}$.
2. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \mu\text{F}$ with i/p.
3. Plot the amplitude response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
4. Plot the amplitude response of BC 10 7 amplifier with $R_2 = 5.4 \text{ K}$ i/p.
5. Plot frequency response of BC 107 amplifier $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.

EXP NO: 8**CLASS B COMPLEMENTARY SYMMETRY AMPLIFIER (SOFTWARE)**

AIM: To observe the Cross over distortion of Class B complementary symmetry power amplifier.

SOFTWARE USED:

Multisim V13.0

APPARATUS REQUIRED:

- | | | |
|-----------------------------------|---|------|
| 1. Function generator | - | 1No. |
| 2. Cathode Ray oscilloscope (CRO) | - | 1No. |
| 3. Regulated power supply (0-30V) | - | 1No. |
| 4. Transistor (2N3905, 2N3904) | - | 1No. |
| 5. Resistor (1K Ω) | - | 1No. |

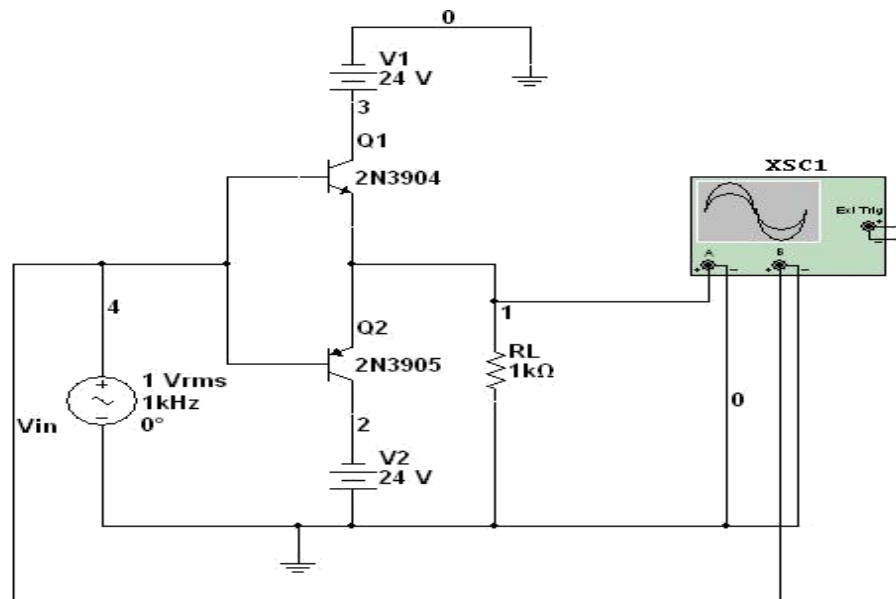
CIRCUIT DIAGRAM:

Fig: 8 a- Circuit diagram of Class B complementary symmetry power amplifier

THEORY:

A Class B complementary symmetry power amplifier is a type of amplifier designed to improve efficiency by using two complementary transistors (one NPN and one PNP) to amplify each half of the input signal. In this configuration, the NPN transistor conducts during the positive half of the input waveform, while the PNP transistor conducts during the negative half, resulting in each transistor being active for only half of the signal cycle. This push-pull arrangement reduces power dissipation, making Class B amplifiers much more efficient (up to 78.5%) compared to Class A amplifiers. However, the transition between the two transistors can introduce a small distortion known as crossover distortion, as there is a brief period when neither transistor is conducting. Despite this, Class B amplifiers are widely used in audio and RF applications where efficiency is important, and the crossover distortion can be minimized or corrected using various techniques, such as adding small biasing currents to the transistors, making them slightly conductive even when there is no input signal (Class AB operation).

PROCEDURE:

1. Switch ON the computer and open the multisim software.
2. Check whether the icons of the instruments are activated and enable.
3. Now connect the circuit using the designed values of each and every component.
4. Connect the function generator with sine wave of 30mV p-p as input at the input of terminals of the circuit.
5. Connect the Cathode Ray Oscilloscope (CRO) to the output terminals of the circuit.
6. Go to simulation button click it for simulation process.
7. Observe the cross over distortion in the CRO.

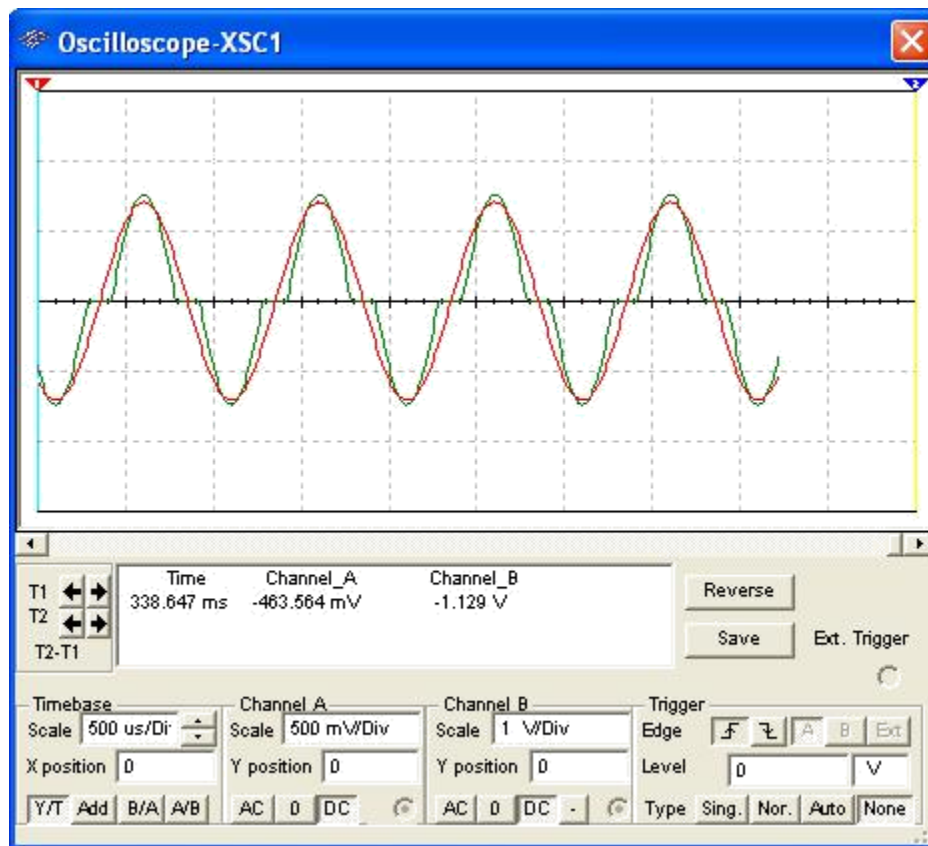
OBSERVATION:

Fig: 8 b- Output waveform of Class B complementary symmetry power amplifier

EXP NO: 8**CLASS B COMPLEMENTARY SYMMETRY AMPLIFIER (HARDWARE)**

AIM: To observe the Cross over distortion of Class B complementary symmetry power amplifier.

APPARATUS REQUIRED:

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	CL100	1
	(c) Capacitors	CK100	1
	(d) Resistors	100 μ F	1
		1K Ω	1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

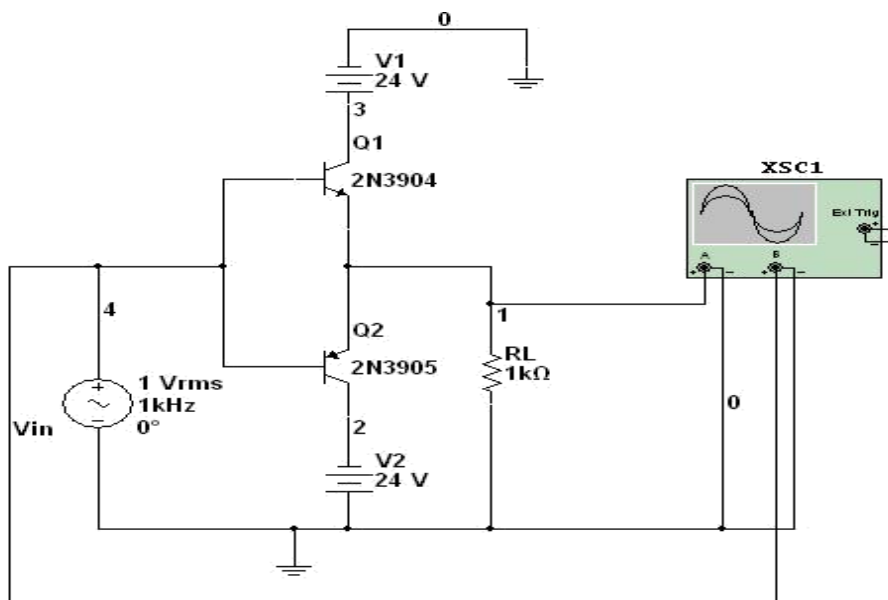
CIRCUIT DIAGRAM:

Fig: 10 c -Class B complementary symmetry power amplifier Circuit diagram

PROCEDURE: -

1. Connect the circuit diagram as shown in figure.
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, vary the input signal frequency from 0 to 1MHz in steps as shown in tabular column and note the corresponding output voltages.

PRECAUTIONS:

Avoid loose connections and give proper input Voltage

TABULAR COLUMN:

Frequency(in Hz)	Output Voltage (V _o)		Gain $A_v = V_o/V_i$		Input = 50mV	
					Gain(in dB)	
20					$=20\log_{10}(V_o/V_i)$	
40						
80						
100						
1K						
10k						
50k, 100K						
1M						

RESULT: The efficiency of Class B power amplifier graph is plotted.

VIVA QUESTIONS:

1. Differentiate between voltage amplifier and power amplifier
2. Why power amplifiers are considered as large signal amplifier?
3. When does maximum power dissipation happen in this circuit?
4. What is the maximum theoretical efficiency?
5. Sketch wave form of output current with respective input signal.
6. What are the different types of class-B power amplifiers available?
7. What is the theoretical efficiency of the transformer coupled class-A power amplifier?
8. What is difference in AC, DC load line?
9. How do you locate the Q-point?
10. What are the applications of class-B power amplifier?
11. Define class –B power amplifier?
12. Give the reason why class -B power amplifier is called as directly coupled power amplifier?
13. What is the efficiency of class –B power amplifier?
14. In class-B power amplifier, when the maximum power dissipation takes place in the transistor?
15. List out the different types of distortions?
16. What are Class B, Class C and Class AB amplifiers and which type is used for what application?
17. Differentiate between voltage amplifier and power amplifier
18. Why power amplifiers are considered as large signal amplifier?
19. What is the theoretical efficiency of the transformer coupled class-B power amplifier?
20. Sketch wave form of output current with respective input signal.
21. How do you locate the Q-point?
22. When does maximum power dissipation happen in this circuit?
23. What are the different types of class-B power amplifiers available?
24. When does maximum power dissipation happen in this circuit?
25. What is the maximum theoretical efficiency?
26. Sketch wave form of output current with respective input signal.
27. What are the applications of class-B power amplifier?
28. Give the reason why class –B power amplifier is called as directly coupled power amplifier?
29. How do you locate the Q-point?
30. When does maximum power dissipation happen in this circuit?

EXERCISE PROBLEMS:

1. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
2. Plot the frequency response of BC547 amplifier with $C_2 = 5 \mu\text{F}$ with triangular i/p.
3. Plot the amplitude response of BC 557 amplifier with $R_1 = 4.1 \text{ K}$.
4. Plot the amplitude response of BC 548 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
5. Plot frequency response of SL 100 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
6. Plot the frequency and amplitude response of CL 100 amplifier with $C_1 = 5 \mu\text{F}$.
7. Plot the frequency response of amplifier with $C_2 = 5 \mu\text{F}$, triangular i/p.
8. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
9. Plot the amplitude response of BC107 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
10. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
11. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \mu\text{F}$.
12. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \mu\text{F}$ with i/p.
13. Plot the amplitude response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
14. Plot the amplitude response of BC 10 7 amplifier with $R_2 = 5.4 \text{ K}$ i/p.
15. Plot frequency response of BC 107 amplifier $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.

EXP NO: 9**SINGLE TUNED AMPLIFIER (SOFTWARE)****PRELAB:**

Study the operation and working principle Tuned amplifier.

OBJECTIVE:

To design single tuned amplifier using Multisim software and calculate the frequency response and bandwidth

Apparatus:

1. Transistor – BC 107
2. Resistors – 2K(2), 4.7K
3. Capacitors – 10nF(2)
4. RPS
5. CRO

SOFTWARE TOOL: Multisim V 13.0

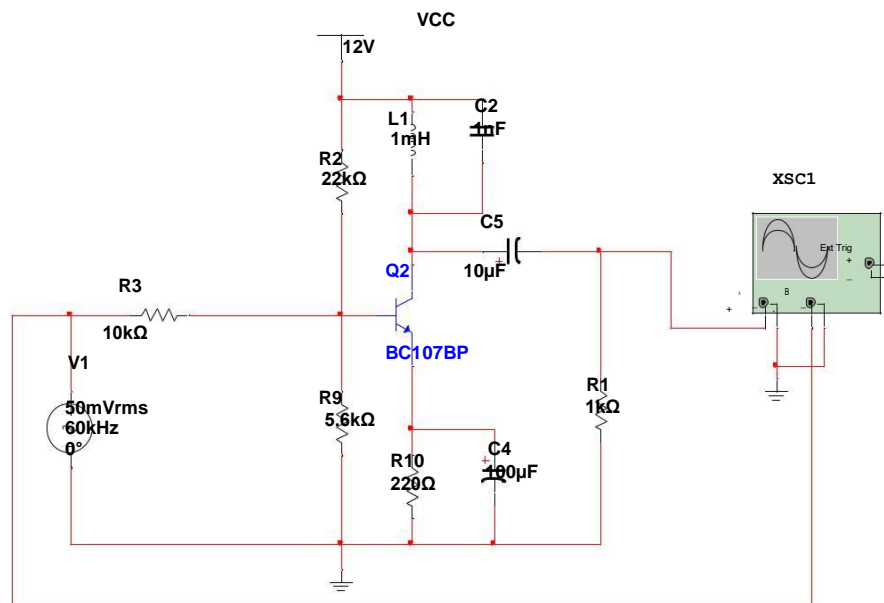
CIRCUIT DIAGRAM:


Fig: 9.a Single Tuned amplifier circuit diagram

THEORY:

A single-tuned amplifier is a type of amplifier that is designed to selectively amplify a specific frequency or a narrow band of frequencies using a resonant circuit, typically consisting of an inductor (L) and a capacitor (C) in parallel. The resonant circuit, also known as a tuned circuit or LC tank, is placed either in the load or in the feedback network of the amplifier. At resonance, the impedance of the tuned circuit is at its maximum, allowing the amplifier to achieve maximum gain at the desired frequency while attenuating frequencies outside the band. Single-tuned amplifiers are commonly used in radio frequency (RF) applications, such as in radio receivers and transmitters, where they help in selecting and amplifying signals of a specific frequency while rejecting unwanted signals. However, the bandwidth of a single-tuned amplifier is relatively narrow, and its gain decreases rapidly as the frequency deviates from the resonant frequency.

PROCEDURE:

1. Open Multisim Software to design circuit
2. Select on New editor window and place the required component on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Indicate the node names and go for AC Analysis with the output node
6. Observe the Ac Analysis and draw the magnitude response curve
7. Calculate the bandwidth of the amplifier

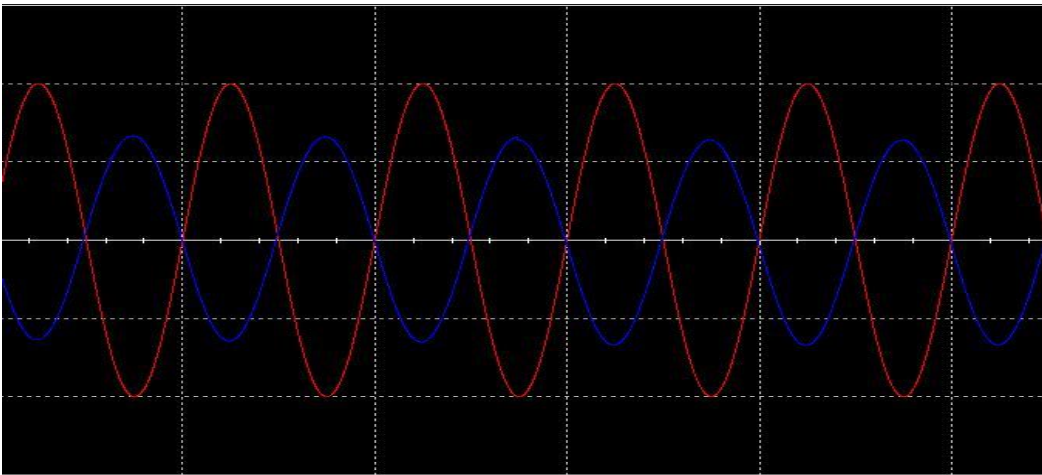OBSERVATIONS/GRAPHS:**RESULT: -**

1. Frequency response of single tuned Amplifier is plotted.
2. Gain = _____dB (maximum).
3. Bandwidth= $f_H - f_L$ = _____Hz.

EXP NO:9**SINGLE TUNED VOLTAGE AMPLIFIER (Hardware)****AIM: -**

Plot the frequency response of a single tuned amplifier.

Calculate gain.

Calculate bandwidth.

COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Device	Range/Rating	Qty
1.	(a) DC supply voltage	12V	1
	(b) BJT	BC107	1
	(c) Capacitors	10 F	2
		100 F	1
	(d) Resistors	220 ,22K ,1k	1
	(e) inductor (1mH)	5.6K ,10k	1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

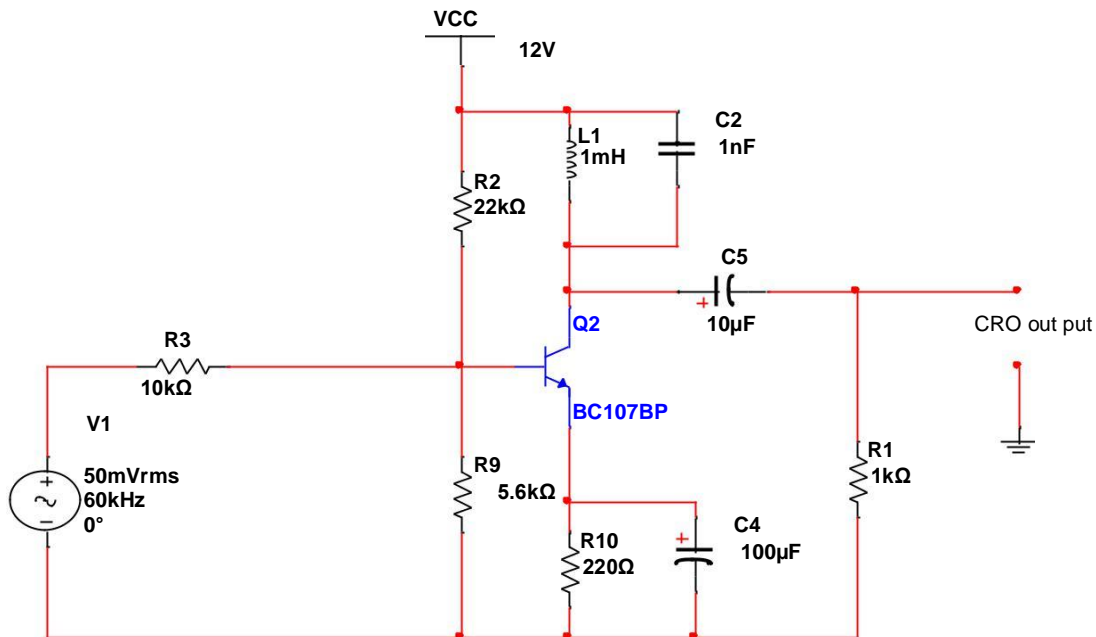
CIRCUIT DIAGRAM:

Fig: 9.c Single Tuned amplifier circuit diagram

PROCEDURE :

1. Connect the circuit diagram as shown in figure.
2. Set the input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, vary the input signal frequency from 0 to 1MHz in steps as shown in tabular column and note the corresponding output voltages.

PRECAUTIONS:

1. Avoid loose connections and give proper input Voltage

TABULAR COLUMN:

Input = 50mV

Frequency (in Hz)	Output Voltage (V _o)	Gain $A_v = V_o/V_i$	Gain (in dB) = $20\log_{10}(V_o/V_i)$
20			
40			
80			
100			
500			
1000			
5000			
10K			

RESULT:

1. Frequency response of single Tuned voltage amplifier is plotted.
2. Gain = _____dB (maximum).
3. Bandwidth= $f_H - f_L$ = _____Hz.

VIVA QUESTIONS:

1. What is a tuned amplifier?
2. Define Q-factor?
3. What is selectivity?
4. Is tuned amplifier a narrow band or wide band amplifier?
5. Give the applications for tuned amplifier?
6. Is tuned amplifier a narrow band or wide band amplifier?
7. What is the type of capacitor used in RC coupled amplifier for a) coupling two stages b) by pass emitter
8. What is signal source used for experiment of an RC coupled amplifier and how much maximum voltage it could give
9. What is the pin configuration on bread board used in the lab
10. How do you determine AC power output in class A amplifier i.e., do you measure current or voltage and how
11. How much current do you pass through reference zener in series regulated power supply experiment
12. In shunt regulator how is the value of resistor between base and emitter of shunt transistor determined
13. How do you determine Q of coil used in tuned amplifier experiment
14. What is a tuned amplifier
15. Define Q-factor
16. What is selectivity?
17. Is tuned amplifier a narrow band or wide band amplifier
18. Give the applications for tuned amplifier
19. Is tuned amplifier a narrow band or wide band amplifier
20. What is the type of capacitor used in RC coupled amplifier for a) coupling two stages b) by pass emitter
21. What is signal source used for experiment of an RC coupled amplifier and how much maximum voltage it could give
22. What is the pin configuration on bread board used in the lab
23. How do you determine AC power output in class A amplifier i.e., do you measure current or voltage and how
24. How much current do you pass through reference zener in series regulated power supply experiment
25. In shunt regulator how is the value of resistor between base and emitter of shunt transistor determined
26. How do you determine Q of coil used in tuned amplifier experiment
27. What is the type of capacitor used in RC coupled amplifier for a) coupling two stages b) by pass emitter
28. What is signal source used for experiment of an RC coupled amplifier and how voltage it could give?
29. What is the pin configuration on bread board used in the lab
30. How do you determine AC power output in class A amplifier i.e., do you measure current or voltage and how?

EXERCISE PROBLEMS:

1. Plot the frequency response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
2. Plot the frequency response of BC 547 amplifier with $C_2 = 5 \mu\text{F}$ with i/p.
3. Plot the frequency response of BC 2N2222 amplifier with $R_1 = 4.1 \text{ K}$.
4. Plot the frequency response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
5. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
6. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
7. Plot the frequency response of amplifier with $C_2 = 5 \mu\text{F}$, i/p.
8. Plot the frequency response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
9. Plot the frequency response of BC107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
10. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
11. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \mu\text{F}$.
12. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \mu\text{F}$ with i/p.
13. Plot the frequency response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
14. Plot the frequency response of BC 107 amplifier with $R_2 = 5.4 \text{ K}$ i/p.
15. Plot frequency response of BC 107 amplifier $R_1 = 2.1 \text{ K}$, $R_2 = 2.4 \text{ K}$ with i/p.
16. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 2 \mu\text{F}$.
17. Plot the frequency response of amplifier with $C_2 = 2 \mu\text{F}$, i/p.
18. Plot the frequency response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.
19. Plot the frequency response of BC 107 amplifier with $R_2 = 2.4 \text{ K}$ i/p.
20. Plot frequency response of $R_1 = 2.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
21. Plot the frequency response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
22. Plot the frequency response of BC 107 amplifier with $C_2 = 5 \mu\text{F}$ with i/p.
23. Plot the frequency response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
24. Plot the frequency response BC 107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
25. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p.
26. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
27. Plot the frequency response of amplifier with $C_2 = 5 \mu\text{F}$, i/p.
28. Plot the frequency response of BC107 amplifier with $R_1 = 4.1 \text{ K}$.
29. Plot the frequency response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ i/p.
30. Plot frequency response of $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with i/p

APPLICATIONS:

- (a) Intermediate frequency (IF) amplifier in a super heterodyne receiver;
- (b) very narrow-band IF amplifier in a spectrum analyzer;
- (c) IF amplifier in a satellite transponder;
- (d) RF amplifiers in receivers;
- (e) wide-band tuned amplifiers for video amplification;

EXPT NO: 10**MONOSTABLE MULTIVIBRATOR (SOFTWARE)**

AIM: To observe the waveforms of Monostable Multivibrator at base and collector of the transistors and find the Gate Width

APPARATUS REQUIRED

1. Transistor (BC107B) - 2No's.
2. Resistor $R_1 = 10k\Omega$, $R = 12.5k\Omega$
3. Capacitor $C = 100nF$
4. CRO probes & CRO
5. Bread Board Trainer
6. Connecting wires.

SOFTWARE TOOL: Multisim 13.0

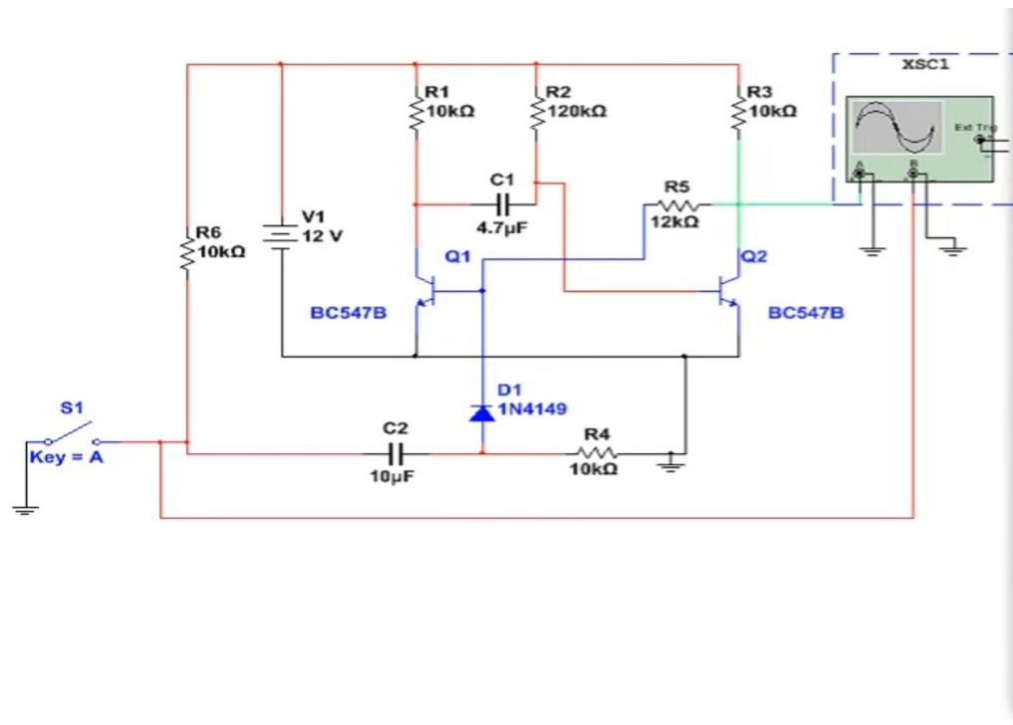
CIRCUIT DIAGRAM :

Fig 10.a: Circuit diagram of monostable multivibrator

THEORY:

A monostable multivibrator, also known as a one-shot pulse generator, is a type of electronic circuit that generates a single output pulse of fixed duration in response to a triggering input pulse. The circuit has one stable state and one quasi-stable state. When the circuit is in its stable state, it remains there indefinitely until a trigger pulse is applied. Upon receiving the trigger, the circuit temporarily switches to its quasi-stable state, where it generates a pulse with a duration determined by external components, typically a resistor and a capacitor. After this period, the circuit automatically returns to its stable state. The pulse width is governed by the RC time constant, allowing for precise timing applications. Monostable multivibrators are widely used in timing applications, pulse width modulation, and digital signal processing where a specific time delay or single pulse generation is required.

PROCEDURE:

1. Open Multisim Software to design Monostable multivibrator circuit
2. Select on New editor window and place the required component Monostable multivibrator on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Indicate the node names and go for AC Analysis with the output node
6. Observe the output waveform .

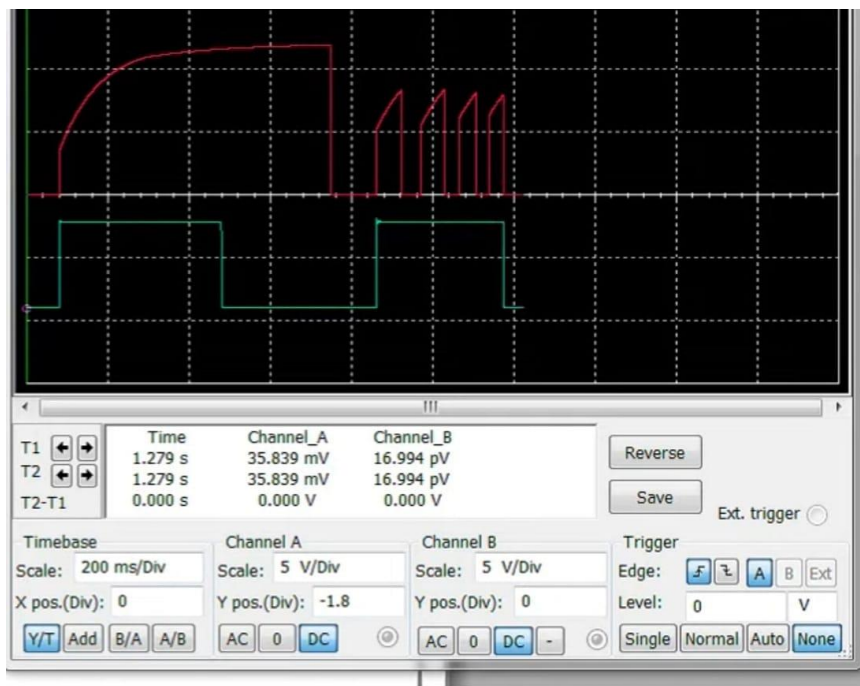
OBSERVATIONS/GRAPHS:

Fig:10b:output waveform of monostable multivibrator

RESULT: -

Output waveform of monostable multivibrator is plotted.

EXP NO: 10**MONOSTABLE MULTIVIBRATOR (HARDWARE)**

AIM: To observe the waveforms of Monostable Multivibrator at base and collector of the transistors and find the Gate Width.

APPARATUS REQUIRED:

7. Transistor (BC107B) - 2No's.
8. Resistor $R_1 = 10k\Omega$, $R = 12.5k\Omega$
9. Capacitor $C = 100nF$
10. CRO probes & CRO
11. Bread Board Trainer
12. Connecting wires.

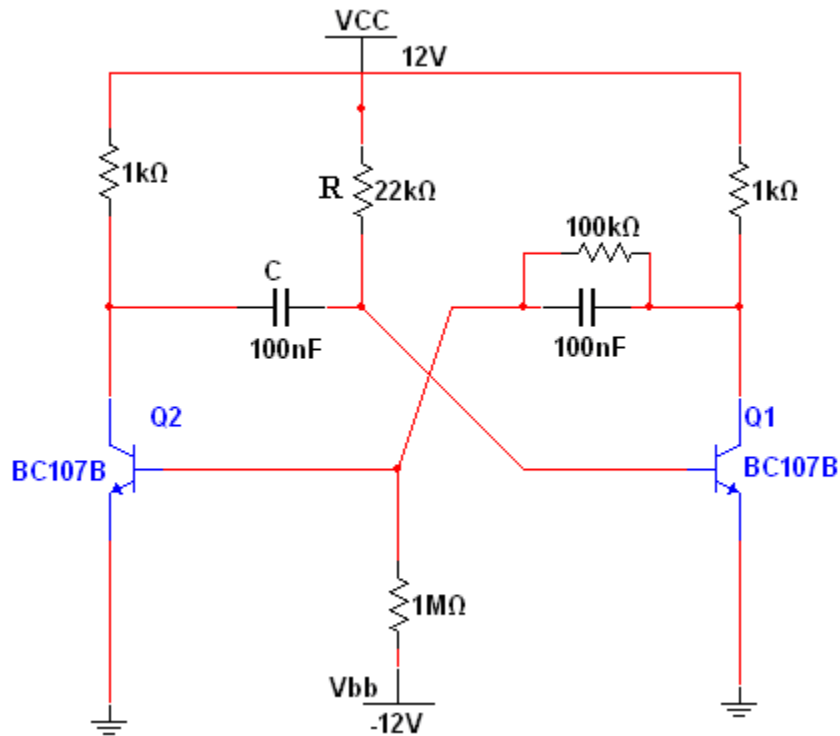
CIRCUIT DIAGRAM:

Fig: 10 a– Monostable multivibrator Circuit diagram

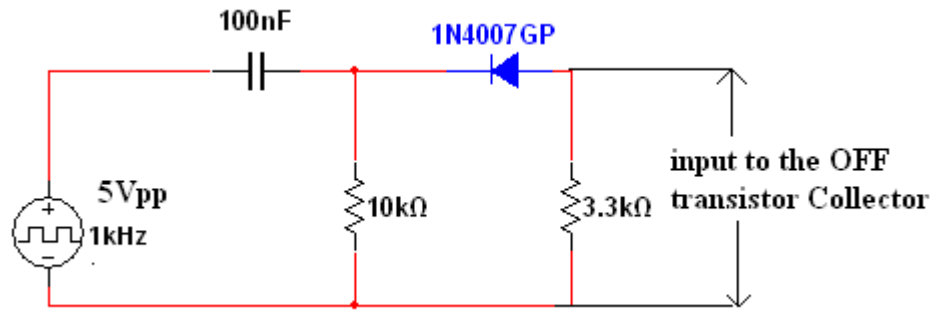
TRIGGER CIRCUIT:


Fig: 10 b– Trigger Circuit diagram

PROCEDURE:

1. Connect the circuit as per circuit diagram.
2. Assume Q_1 – OFF, Q_2 – ON
3. Measure V_{B1} , V_{C1} , V_{B2} , V_{C2} .
4. Measure quasi stable state voltage and current Q_1 – ON & Q_2 – OFF
5. Connect the base of ON transistor and find out the V_{C1} , V_{C2} , V_{B1} , V_{B2} ,
6. Connect the base of OFF transistor and observe the waveform.

CALCULATIONS:

- Gate Width $T = 0.69RC$

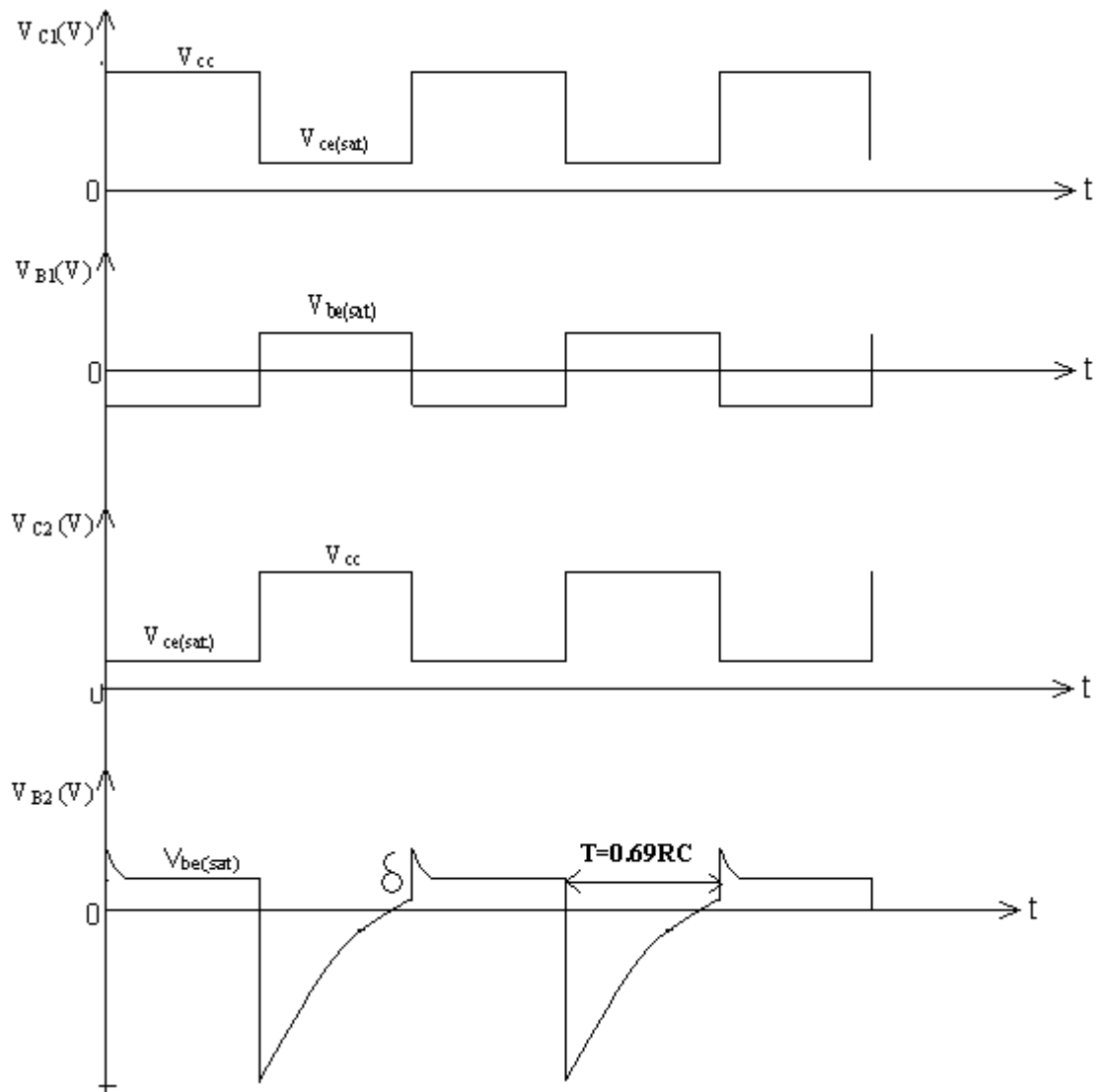EXPECTED WAVEFORMS:**Fig: 10 c– Output waveforms of monostable multivibrator**

RESULT: Monostable multivibrator wave forms are plotted.

VIVA QUESTIONS:

1. Explain the operation of collector coupled Monostable Multivibrator?
2. Derive the expression for the gate width of a transistor Monostable Multivibrator?
3. Give the application of a Monostable Multivibrator.
4. What are applications of Monostable Multivibrator?
5. Why is a Monostable Multivibrator called a gating circuit?
6. Explain the waveform of VB1?
7. Describe the operation of the capacitor C3 in the circuit?
8. Why is the time period T also called Delay time?
9. Justify, Why Monostable Multivibrator is called one-shot circuit?
10. Why is the -ve voltage given at the base of Q1 transistor?
11. What is the no of quasi & stable states of Monostable Multivibrator?
12. What is a multivibrator? What is a quasi state?
13. What are applications of Monostable Multivibrator?
14. The monostable multivibrator is also called __, __, __, __ or __?
15. A Monostable Multivibrator generates __ waveform?
16. Why is the time period T also called Delay time?
17. Justify, Why Monostable Multivibrator is called one-shot circuit?
18. In monostable multivibrator, the coupling elements are __?
19. What is a switching circuit?
20. What are the other names of monostable multivibrator?
21. What are the applications of monostable multivibrator? Design a Monostable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C=0.1\mu F$, For the pulse width of $1\mu sec$
22. Design a One-shot multivibrator with $V_{cc}=12V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C=0.1\mu F$ at $V_{in}=4V$
23. Design a Monostable multivibrator with $V_{cc}=10V$, $R_1=5K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$
24. Design a Monostable multivibrator with $V_{cc}=10V$, $R_1=5K$, $R_2=25K$, $R_{C1}=R_{C2}=2K$, $C=10\mu F$, For the pulse width of $1\mu sec$
25. Design a One-shot multivibrator with $V_{cc}=10V$, $R_1=3K$, $R_2=25K$, $R_{C1}=R_{C2}=2K$, $C=10\mu F$ at $V_{in}=5V$
26. Design a Monostable with BFW10 and $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$ with triggering circuit having the values of $R_T=1k$, $c_T=1\mu F$

27. Design Monostable with BFW10 and $R_1=5K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$
28. Design a One-shot multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=15K$, $R_{C1}=R_{C2}=4K$, $C=0.1\mu F$ at $V_{in}=10V$
29. Design a Monostable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$ with commutating capacitors $C_1=C_2=1\mu F$
30. Monostable multivibrator is also called as _____.

REAL TIME APPLICATIONS OF MONOSTABLE MULTIVIBRATORS :

1. Monostable vibrators are used in analog systems to control an output signal frequency.
2. Synchronize the line and frame rate of television broadcasts.
3. Even moderate the tunes of different octaves with electronic organs.
4. Used to hold output voltages in its unstable state for a certain period of time.
5. The monostable multivibrator is used as delay and timing circuits.
6. It is also used for temporary memories.
7. It is often used to trigger another pulse generator.
8. It is used for regenerating old and worn out pulses.

EXP NO: 11**BISTABLE MULTIVIBRATOR(SOFTWARE)****AIM:**

To design a fixed bias Bistable Multivibrator and to measure the stable state voltages before and after triggering.

APPARATUS REQUIRED :

1. Multisim software version 13.0
2. Operating system windows XP

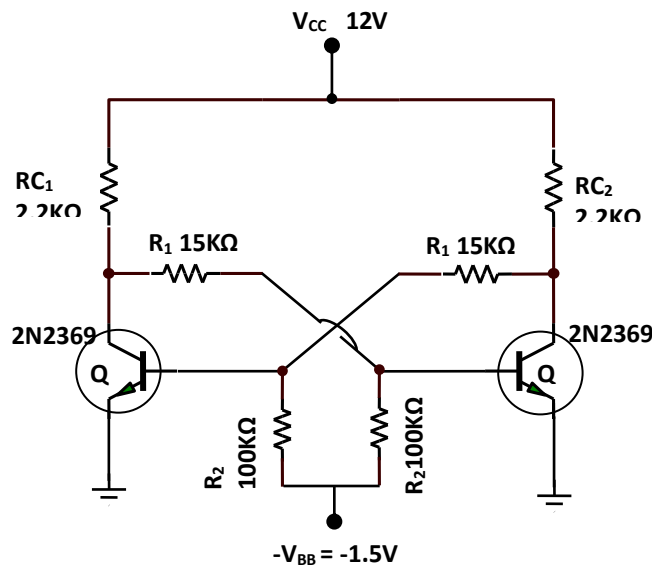
CIRCUIT DIAGRAM:

Fig 11.a circuit diagram of Bistable multivibrator

THEORY:

A bistable multivibrator, also known as a flip-flop, is an electronic circuit that has two stable states and can store a single bit of binary data. Unlike monostable or astable multivibrators, the bistable multivibrator remains in one of its two stable states indefinitely until an external input or trigger causes it to switch to the other state. It operates as a memory element or a digital storage device in various applications. The bistable multivibrator is typically implemented using two cross-coupled logic gates or transistors, where each state represents a different binary value (0 or 1). The transition between states is controlled by input signals, such as clock pulses or control inputs, which determine when the output should switch states. Common examples include the SR (Set-Reset) flip-flop, D (Data) flip-flop, and JK flip-flop.

PROCEDURE:

1. Open Multisim Software to design Bistable multivibrator circuit

2. Select on New editor window and place the required component Bistable multivibrator on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Indicate the node names and go for AC Analysis with the output node
6. Observe the output waveform .

OBSERVATIONS/GRAPHS:

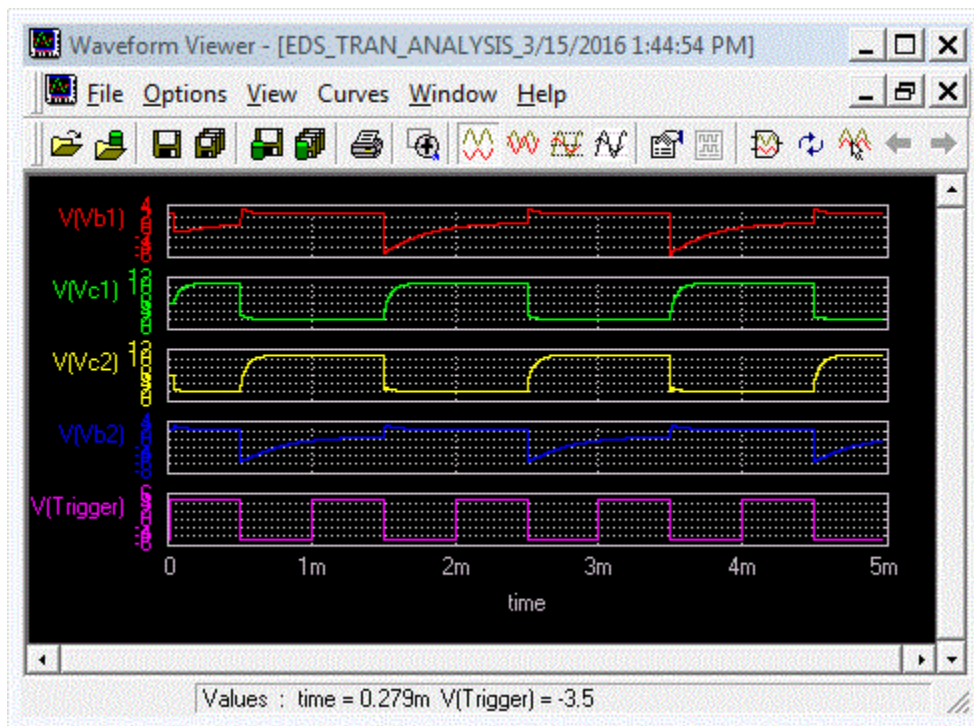


Fig 11.b. Output waveforms of Bistable multivibrator

RESULT: -

Output waveform of Bistable multivibrator is plotted.

EXP NO: 11**BISTABLE MULTIVIBRATOR(HARDWARE)****AIM:**

To design a fixed bias Bistable Multivibrator and to measure the stable state voltages before and after triggering.

COMPONENTS & EQUIPMENTS REQUIRED :

S.No	Device	Range/Rating	Qty
1.	(a) DC supply voltage	12V	1
	(b) BJT	2N2369	2
	(c) Resistors	2.2K Ω ,15K Ω ,100K Ω	Each 2NO
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

THEORY:

A Bistable multivibrator has two stable output states. It can remain indefinitely in any one of the two stable states, and it can be induced to make an abrupt transition to the other stable state by means of suitable external excitation. It would remain indefinitely in this stable state, until it is again induced to switch into the original stable state by external triggering.

Bistable multivibrators are also termed as 'Binary's or Flip-flops'. A binary is sometimes referred to as '*Eccles-Jordan Circuit*'.

Principle of Operation of bistable multivibrator:

Consider the circuit as shown in the figure.1. The transistor Q_1 and Q_2 are n-p-n transistors. They are coupled to each other as shown in figure 1. It is evident that the output of each transistor is coupled to the input of the other transistor. Since the transistors are identical, there quiescent currents would be the same, unless the loop gain is greater than unity. When I_1 increases slightly, the voltage drop across the collector resistance R_{C1} increases. Since V_{CC} is fixed, the voltage of point C decreases. This has the effect of decreasing the base current of Q_2 . This, in turn, decreases the collector current of Q_2 viz. I_2 decreases, the voltage drop $I_2 R_{C2}$ decreases. Hence the voltage of point D increases.

Due to increase of V_D , the base current of Q_1 increases. This increases the collector current of Q_1 viz I_1 . Thus I_1 further increases. $I_1 R_{C1}$ drop further increases, V_C further decreases, the base current of Q_2 further decreases, with the result that I_2 further decreases. Thus it can easily seen that if the collector current I_1 increases even marginally, I_2 would go on progressively decreasing and as a result, I_1 would progressively increase. Eventually I_2 would become practically zero, cutting off the transistor Q_2 , at the same time transistor Q_1 would conduct heavily with the result that it

would be driven into saturation. Thus Q_2 becomes OFF and Q_1 becomes ON. It can similarly be shown that if I_2 increases even marginally similar sequence of operation would result and ultimately Q_2 would be ON and Q_1 OFF. Thus when Q_1 is ON, Q_2 is OFF and when Q_1 is OFF Q_2 is ON

CIRCUIT DIAGRAM:

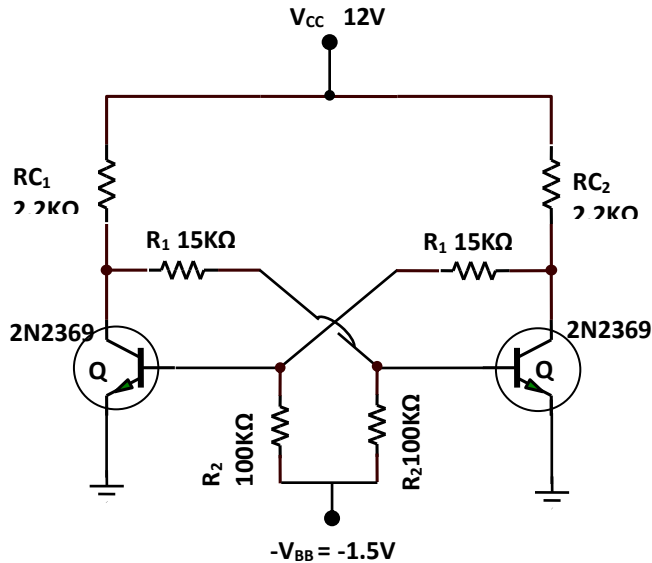


Fig 11.a circuit diagram of Bistable multivibrator

PROCEDURE:

1. Connect the circuit as shown in figure 2.
2. Observe the waveforms at V_{BE1} , V_{BE2} , V_{CE1} , V_{CE2} using CRO & multimeter
3. Observe the voltages at V_{C1} and V_{C2} .
4. If $V_{C1} = V_{CE(Sat)}$ and $V_{C2} = V_{CC}$ (Approximately) then Q_1 is 'ON' and Q_2 is 'OFF'. Otherwise $V_{C1} = V_{CC}$ (Approximately) and $V_{C2} = V_{CE(Sat)}$ then Q_1 is 'OFF' and Q_2 is 'ON'.
5. Observe which transistor is in ON state and which transistor is in OFF state. and observe the voltages V_{C1} , V_{C2} , V_{B1} , and V_{B2} .
6. Apply -ve triggering at the base of the ON transistor and observe the voltages V_{C1} , V_{C2} , V_{B1} , and V_{B2} .

OBSERVATIONS:

Before Triggering : When Q_1 is 'ON' and Q_2 is 'OFF'

	V_{BE1}	V_{BE2}	V_{CE1}	V_{CE2}
Stable state Voltages				

After Triggering: When Q_1 is 'OFF' and Q_2 is 'ON'.

	V_{BE1}	V_{BE2}	V_{CE1}	V_{CE2}
Stable state Voltages				

RESULTS:

Conclusion can be made on which transistor is 'ON' and which transistor is 'OFF' before triggering and after triggering.

DESIGN PROBLEMS:

1. Design a Bistable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{c1}=R_{c2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$
2. Design a Fixed Bias Binary multivibrator with $V_{cc}=12V$, $R_1=2K$, $R_2=20K$, $R_{c1}=R_{c2}=2K$, $C=0.1\mu F$ at $V_{in}=4V$
3. Design a Bistable multivibrator with $V_{cc}=10V$, $R_1=5K$, $R_2=20K$, $R_{c1}=R_{c2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$
4. Design a Bistable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=15K$, $R_{c1}=R_{c2}=4K$, $C=0.1\mu F$ at $V_{in}=10V$
5. Design a Fixed Bias Binary multivibrator with $V_{cc}=10V$, $R_1=3K$, $R_2=25K$, $R_{c1}=R_{c2}=2K$, $C=10\mu F$ at $V_{in}=5V$
6. Design a flip flop or Binary with BFW10 and $R_1=2K$, $R_2=20K$, $R_{c1}=R_{c2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$
7. Design a flip flop or Binary with BFW10 and $R_1=5K$, $R_2=20K$, $R_{c1}=R_{c2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$
8. Design a Bistable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=15K$, $R_{c1}=R_{c2}=4K$, $C=0.1\mu F$ at $V_{in}=10V$
9. Design a Bistable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{c1}=R_{c2}=2K$, $C=0.1\mu F$ at $V_{in}=8V$ with commutating capacitors $C_1=C_2=1\mu F$
10. Design a Bistable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{c1}=R_{c2}=2K$, $C=10\mu F$ at $V_{in}=8V$ with commutating capacitors $C_1=C_2=0.1\mu F$

VIVA QUESTIONS:

1. What is Multivibrator? Explain the principle on which it works? Why is it called a binary?
2. Explain the role of commutating capacitors in a Bistable Multivibrator?
3. Give the Application of a Binary.
4. What are the applications of a Bistable multivibrator?
5. Describe the operation of commutating capacitors?
6. Why is a Binary also called a flip-flop?
7. Mention the name of different kinds of triggering used in the circuit shown?
8. What are the disadvantages of direct coupled Binary?
9. How many types of unsymmetrical triggering are there?
10. What are catching diodes?
11. Which triggering is used in binary counting circuits?
12. What are the applications of a Bistable Multivibrator?
13. Describe the operation of commutating capacitors?
14. Commutating capacitors are also called as ___ or ?
15. What is the meaning of a stable state in a multi-vibrator?
16. Mention the names of different kinds of triggering used in the circuit shown?
17. What are the disadvantages of direct coupled Binary?
18. The diodes used in a bistable multivibrator to maintain a constant output swing are called diodes?
19. The interval during which conduction transfers from one transistor to another is called the?
20. What are the coupling elements of a Bi-stable Multivibrator?
21. What are the other names of Bistable Multivibrator?
22. What is multivibrator?
23. Give the applications of bistable multivibrator?
24. Explain the multivibrator?
25. What are the other names of Bistable Multivibrator?
26. Describe the operation of commutating capacitors?
27. What is the meaning of a stable state in a multi-vibrator?
28. Mention the names of different kinds of triggering used in the circuit shown?
29. What are the disadvantages of direct coupled Binary?
30. The diodes used in a bistable multivibrator to maintain a constant output swing are called ___ diodes?

APPLICATIONS OF BISTABLE MULTIVIBRATORS :

1. The bistable multivibrator or Flip Flop is of great importance in digital operation in computers, digital communications.
2. It is also used for reversing to the supply to a given circuit or change supply to two circuit at regular intervals.

EXP NO: 12**ASTABLE MULTIVIBRATOR (SOFTWARE)****AIM :**

To design and simulate an Astable Multivibrator to generate clock pulse for a give frequency and obtain the wave forms and test its performance.

COMPONENTS REQUIRED:

1. Resistors	1K Ω , 4.7K Ω	2 No.s 2 No.s
2. Capacitors	0.1 μ f	2 No.s
3. Transistors	2N2369	2 No.s

SOFTWARE TOOL :

MULTISIM 13.0

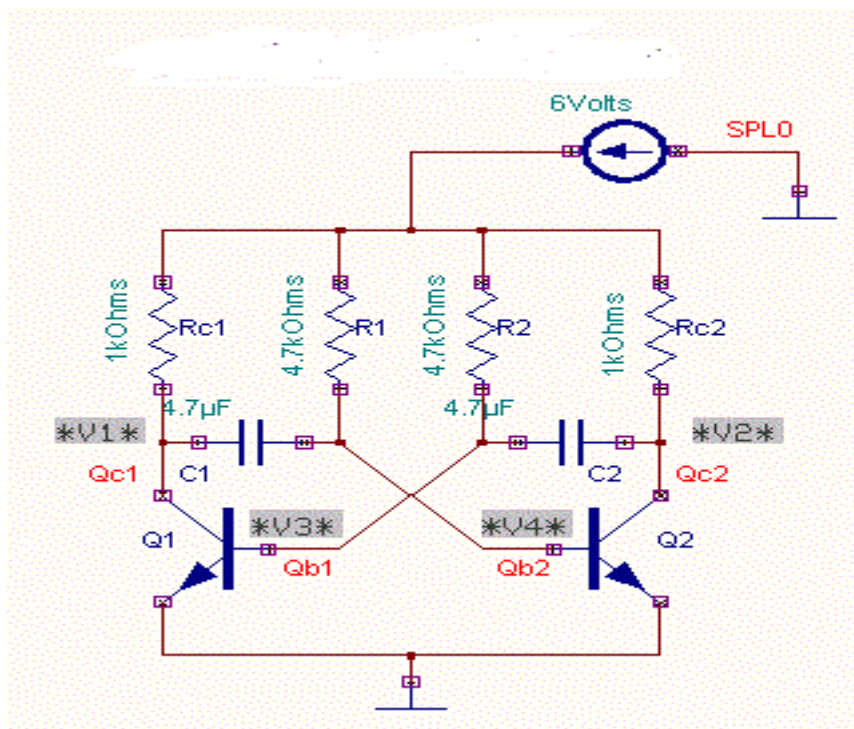
CIRCUIT DIAGRAM :

Fig12.a :circuit diagram of Astable multivibrator

THEORY:

An astable multivibrator is a type of electronic oscillator circuit that continuously switches between its two unstable states, generating a square wave output with a defined frequency and duty cycle. Unlike monostable and bistable multivibrators, which require external triggering, the astable multivibrator oscillates autonomously, producing a periodic waveform without the need for an external input. The circuit typically consists of an amplifier (such as a transistor or operational amplifier) and a feedback network that includes resistors and capacitors.

PROCEDURE:

1. Open Multisim Software to design Astable multivibrator circuit
2. Select on New editor window and place the required component Astable multivibrator on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Indicate the node names and go for AC Analysis with the output node
7. Observe the output waveform .

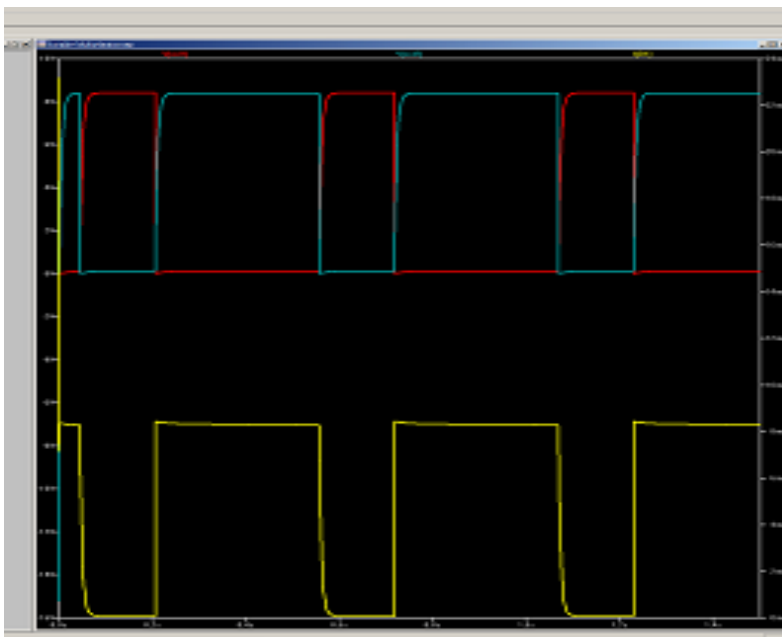
OBSERVATION RESULTS:

Fig12.b : output waveform of Astable multivibrator

RESULTS :

Output Waveforms of Astable multivibrator is plotted.

EXP NO: 12**ASTABLE MULTIVIBRATOR (HARDWARE)****AIM :**

To design an Astable Multivibrator to generate clock pulse for a give frequency and obtain the wave forms and test its performance.

COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	1
	(c) Capacitors	10 μ F	2
	(d) Resistors	15K Ω	2
		4.7K Ω	2
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

THEORY:

An Astable multivibrator has two quasi-stable states, and it keeps on switching between these two states, by itself, No external triggering signal is needed. The astable multivibrator cannot remain indefinitely in any of these two states. The two amplifiers of an astable multivibrator are regeneratively cross-coupled by capacitor.

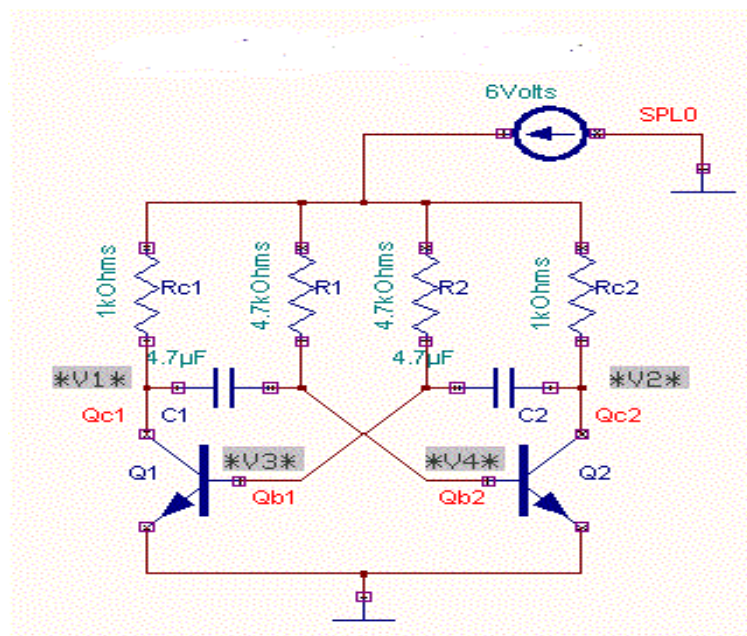
CIRCUIT DIAGRAM :

Fig 12.a circuit diagram of Astable multivibrator

THEORY :

Let it be assumed that the multivibrator is already in action and is oscillating i.e., switching between the two states. Let it be further assumed that at the instant considered, **Q₂ is ON and Q₁ is OFF.**

i) Since Q₂ is ON, capacitor C₂ charges through resistor R_{C1}. The voltage across C₂ is V_{CC}.

ii) Capacitor C₁ discharges through resistor R₁, the voltage across C₁ when it is about to start discharging is V_{CC}. (Capacitor C₁ gets charged to V_{CC} when Q₁ is ON).

As capacitor C₁ discharges more and more, the potential of point A becomes more and more positive (or less and less negative), and eventually V_A becomes equal to V_γ, the cut in voltage of Q₁. For V_A > V_γ, transistor Q₁ starts conducting. When Q₁ is ON Q₂ becomes OFF.

Similar operations repeat when Q₁ becomes ON and Q₂ becomes OFF.

Thus with **Q₁ ON and Q₂ OFF**, capacitor C₁ charges through resistor R_{C2} and capacitor C₂ discharges through resistor R₂. As capacitor C₂ discharges more and more, it is seen that the potential of point B becomes less and less negative (or more and more positive), and eventually V_B becomes equal to V_γ, the cut in voltage of Q₂. when V_B > V_γ, transistor Q₂ starts conducting. When Q₂ becomes On, Q₁ becomes OFF.

It is thus seen that the circuit keeps on switching continuously between the two quasi-stable states and once in operation, no external triggering is needed. Square wave voltage are generated at the collector terminals of Q₁ and Q₂ i.e., at points C and D.

Design:

$$I_C \text{ max} = 5 \text{ mA} ; V_{CC} = 12 \text{ V} ; V_{CE(\text{SAT})} = 0.2 \text{ V}$$

$$R_C = (V_{CC} - V_{CE(\text{SAT})}) / I_{C \text{ MAX}}$$

$$\text{Let } C = 0.1 \text{ } \mu\text{F} \text{ and } R = 10 \text{ K}\Omega$$

$$T = 0.69 (R_1 C_1 + R_2 C_2) = 0.69 (2RC) \quad \because (R_1 = R_2 ; C_1 = C_2)$$

$$= T_{\text{ON}} + T_{\text{OFF}}$$

OBSERVATION TABLE:

S.No	Theoretical Time Period ($T_{(\text{T}_{\text{ON}} + \text{T}_{\text{OFF}})} = 1.38RC$ Calculation	Practical Time Period ($T = T_{\text{ON}} + T_{\text{OFF}}$) Calculation
1		

PROCEDURE:

1. Connect the circuit as shown in figure 1.
2. Observe the waveforms at V_{BE1}, V_{BE2}, V_{CE1}, V_{CE2} and find frequency.
3. Vary C from 0.01 to 0.001 μF and measure the frequency at each step.
4. Keep the DC- AC control of the Oscilloscope in DC mode.

EXPECTED WAVEFORMS

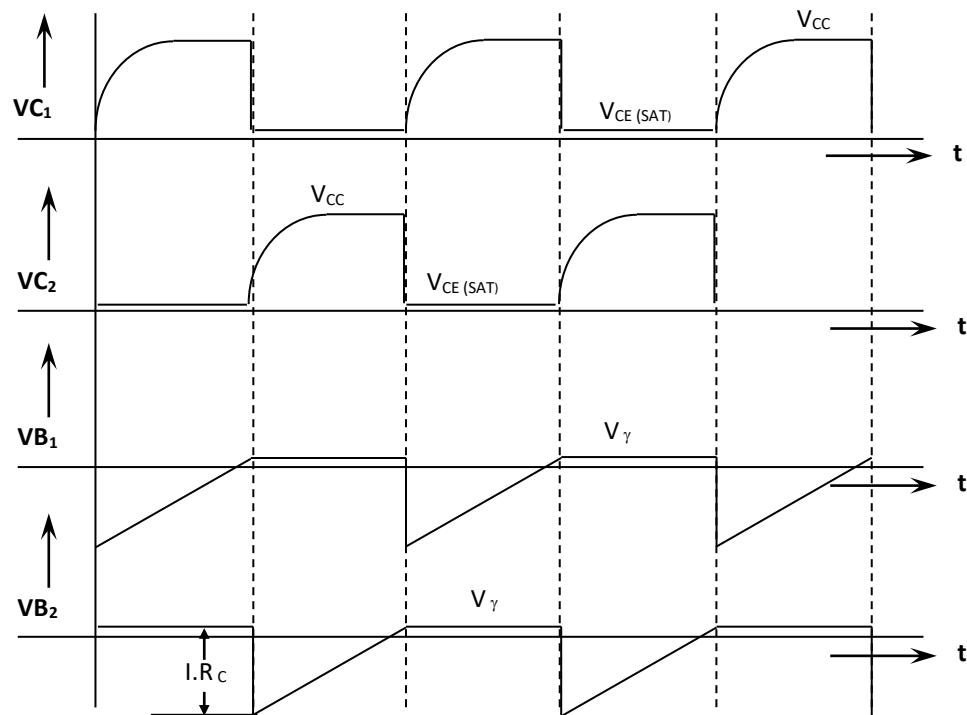


Fig 12.b:Expected waveform of Astable multivibrator

OBSERVATIONS:

T_{ON} (Theoretical) = $0.69RC$ =

T_{OFF} (Theoretical) = $0.69RC$ =

$T(T_{ON} + T_{OFF})$ (Theoretical) = $1.38RC$ =

T_{ON} (practical) =

T_{OFF} (practical) =

$T(T_{ON} + T_{OFF})$ (practical) =

RESULT:

Conclusion can be made on time period of the output waveforms of the Astable multivibrator theoretically and practically and output waveforms of the multi vibrator are identical or not WHEN compared with the theoretical wave forms

DESIGN PROBLEMS:

1. Design a Astable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, , $C_1=C_2=0.1\mu F$,
For the time period of $1\mu sec$
2. .Design a Square wave generator with $V_{cc}=10V$, $R_1=5K$, $R_2=15K$, $R_{C1}=R_{C2}=5K$, $C_1=C_2=10\mu F$,
For the time period of $5\mu sec$
- 3.Design a Astable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=10K$, $R_{C1}=R_{C2}=2K$, $C_1=C_2=0.1\mu F$,
For the time period of $5\mu sec$
- 4.Design a Square wave generator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C_1=C_2=4.7\mu F$,
For the time period of $1\mu sec$
- 5 .Design a Astable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, , $C_1=C_2=0.1\mu F$,
For the time period of $1\mu sec$
- 6.Design a Square wave generator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C_1=C_2=4.7\mu F$,
For the time period of $1\mu sec$
- 7 .Design a Astable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, , $C_1=C_2=0.1\mu F$,
For the time period of $1\mu sec$
- 8 .Design a Square wave generator with $V_{cc}=10V$, $R_1=5K$, $R_2=15K$, $R_{C1}=R_{C2}=5K$, $C_1=C_2=10\mu F$,
For the time period of $5\mu sec$
- 9.Design a Astable multivibrator with $V_{cc}=10V$, $R_1=2K$, $R_2=10K$, $R_{C1}=R_{C2}=2K$, $C_1=C_2=0.1\mu F$,
For the time period of $5\mu sec$
- 10.Design a Square wave generator with $V_{cc}=10V$, $R_1=2K$, $R_2=20K$, $R_{C1}=R_{C2}=2K$, $C_1=C_2=4.7\mu F$,
For the time period of $1\mu sec$.

VIVA QUESTIONS:

1. What is a switching circuit?
2. Justify that the Astable Multivibrator is a two stage RC coupled Amplifier using negative feedback.
3. What is the difference between a switching transistor and an ordinary transistor?
4. What is the effect of slew rate on the working of an Op-amp Multivibrator?
5. Is it possible to change time period of the waveform without changing R & C? Support your answer?
6. Collector waveforms are observed with rounded edges. Explain?
7. Explain charging and discharging of capacitors in an Astable Multivibrator?
8. How can an Astable multivibrator be used as VCO?
9. Why do you get overshoots in the Base waveforms?
10. What are the applications of Astable Multivibrator?
11. How can Astable multivibrator be used as a voltage to frequency converter?
12. What is the formula for frequency of oscillations?
13. What are the other names of Astable multivibrator?
14. What are the other names of Astable multivibrator?
15. The smaller allowable interval between two triggers is called the ___ of the flip-flop?
16. Explain charging and discharging of capacitors in an Astable Multivibrator?
17. How can an Astable multivibrator be used as VCO?
18. What are symmetrical triggering and unsymmetrical triggering?
19. What are the applications of Astable Multivibrator?
20. Which multivibrator has two quasi-stable states? What is duty cycle?
21. What is the formula for frequency of oscillations?
22. An astable multivibrator is used as a ___ generator?
23. Design R and C for a frequency of 2KHz of a symmetric Astable oscillator?
24. Define astable state?
25. Define quasi stable state?
26. Explain about the the astable multivibrator?
27. Explain the wave form the astable multivibrator?
28. Describe the operation of commutating capacitors?
29. What is multivibrator? explain the principle on which it works? why is it called a binary?
30. What are the applications of a astable multivibrator?

REAL TIME APPLICATIONS :

1. Used in amateur radio equipment to receive and transmit radio signals.
2. Used in Morse code generators, timers, and systems that require a square wave, including television broadcasts and analog circuits.
3. Involve in radio gears to transmit and receive radio signals and also in time, morse code generators and some systems which require a square wave like analog integrated circuits and TV broadcasts.
4. The astable or free running multivibrator is used as a square wave frequency generator
5. As a timing oscillator or clock of a computer system.
6. It is also used for flashing lights, switching and power supply circuits.
7. Amateur radio equipment to receive and transmit radio signals.
8. Used in Morse code generators.
9. Timers.
10. Systems that require a square wave, including television broadcasts and analog circuits.

EXP NO: 13

SCHMITT TRIGGER USING TRANSISTOR(SOFTWARE)

AIM:

To design and simulate a Schmitt trigger and to observe the waveforms for a given UTP & LTP Values and test its performance.

COMPONENTS REQUIRED:

1. Resistors 5K Ω , 3.3K Ω , 27K Ω , 14K Ω
25K Ω , 2K Ω
2. Transistors 2N2369 – 2
3. Capacitors - 10 μ F

SOFTWARE TOOL :

Multisim 13.0

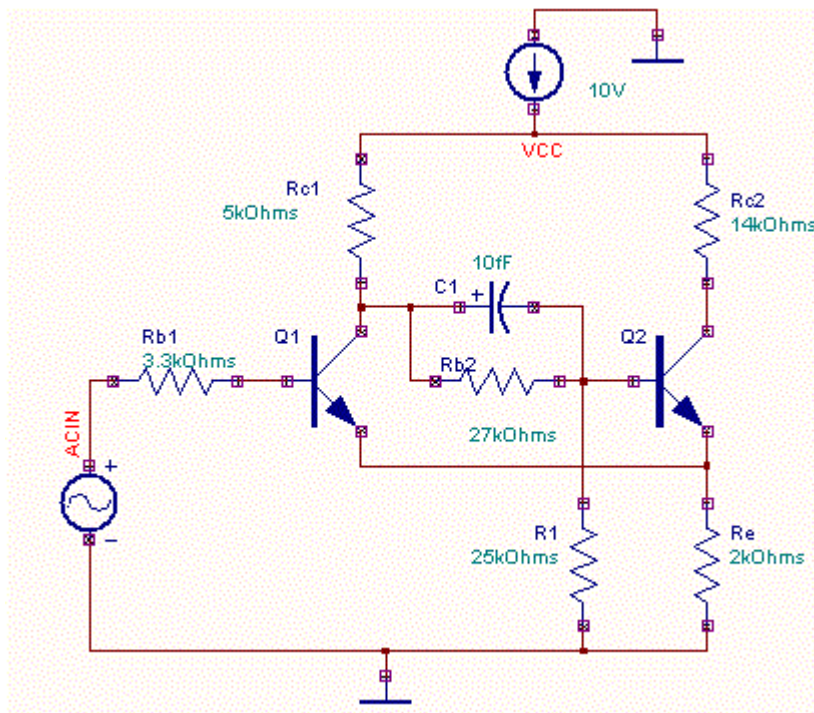
CIRCUIT DIAGRAM :

Fig 13.a: Circuit Diagram of Schmitt trigger

THEORY:

A Schmitt trigger is a type of electronic comparator with hysteresis, designed to provide a stable output when the input signal is noisy or slow-changing. It features two distinct threshold voltage levels: a higher threshold for transitioning from a low to a high output state and a lower threshold for transitioning back to a low state. This hysteresis ensures that the output switches states only when the input signal crosses these predefined thresholds, thus reducing the impact of noise and preventing false triggering due to small fluctuations around the threshold levels. The circuit typically uses positive feedback to achieve these thresholds, creating a more robust and stable switching behavior. Schmitt triggers are commonly implemented using operational amplifiers, logic gates, or dedicated ICs.

PROCEDURE:

1. Open Multisim Software to design Astable multivibrator circuit
2. Select on New editor window and place the required component Astable multivibrator on the circuit window.
3. Make the connections using wire and check the connections and oscillator.
4. Go for simulation and using Run Key observe the output waveforms on CRO
5. Indicate the node names and go for AC Analysis with the output node
6. Observe the output waveform .

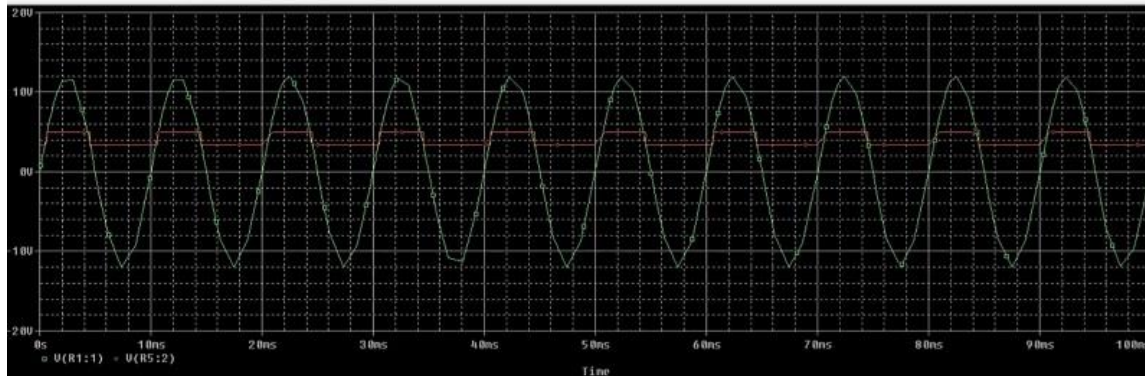
OBSERVATION RESULTS:

Fig 13.b:Output waveform of Schmitt trigger circuit

RESULTS:

Output waveform of Schmitt trigger is plotted.

EXP NO: 13**SCHMITT TRIGGER USING TRANSISTOR (HARDWARE)****AIM:**

To design a Schmitt trigger and to observe the waveforms for a given UTP & LTP Values and test its performance.

COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	1
	(c) Capacitors	10 μ F	1
	(d) Resistors	5K Ω ,14K Ω	1
		3.3K Ω ,27K Ω , 25K Ω ,2K Ω	1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

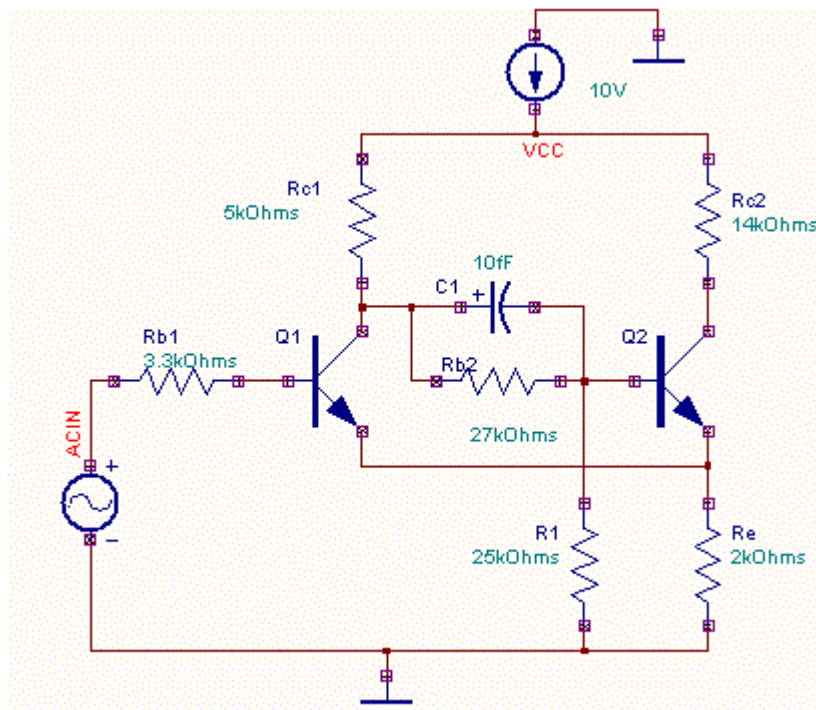
CIRCUIT DIAGRAM:

Fig 13.a: circuit diagram of Schmitt trigger using transistor

THEORY:

The most important application of Schmitt Trigger circuit are amplitude comparator and squaring circuit. The circuit is used to obtain a square waveform from any arbitrary input waveform. The loop gain is to be less than unity.

If Q_2 is conducting there will be voltage drop across R_Z which will elevate the emitter of Q_1 . Consequently if V is small enough in voltage, Q_1 will be cut-off with Q_1 conducting, the circuit amplifies and since the gain is positive, the output to rise, V_2 continues to fall and Z_2 continues to rise. Therefore a value of V will be reached where Q_2 is turned OFF. At the point the output no longer responds to the input.

Here the input signal is arbitrary except that it has large enough excursion to carry input beyond the limits of hysteresis range, $V_H = (V_1 - V_2)$.

The output is a square wave whose amplitude is independent of the amplitude of the input waveform.

DESIGN:

Given $UTP=5V, LTP=3V$

$$I_{C2} = 5mA$$

$$(R_{C2} + R_E) = V_{CC} / I_{C2}$$

$$U.T.P = V_{E2} = 5V$$

$$V_{E2} = (R_E \times V_{CC}) / (R_{C2} + R_E)$$

$$I_2 = 0.1 \times I_{C2}$$

$$L.T.P = V_{E1} = 3V$$

$$R_2 = E_{R2i} / I_2 = V_{E1} / I_2 = L.T.P / I_2$$

$$R_{C1} = \{ (R_E \times V_{CC}) / V_{E1} \} - R_E$$

$$I_{B2} = I_{C2} / h_{fe}(\min)$$

$$(V_{CC} - V_{E2}) / (R_1 + R_{C1})) = (V_{E2}/R_2) + I_{B2}$$

$$R_B = (h_{fe} \times R_E) / 10$$

Find R_1, R_2, R_E, R_{C1} and R_{C2} from the above equations

OBSERVATION TABLE:

S.No	Theoretical Calculation			Practical Calculation
	Upper threshold Point(U.T.P) $= + V_{sat}(+V_{CC}) \frac{R_2}{R_1 + R_2}$	Lower threshold Point(L.T.P) $= - V_{sat}(-V_{CC}) \frac{R_2}{R_1 + R_2}$	Hysistersis(V_H)= $U.T.P - L.T.P$	Hysistersis(V_H)= $U.T.P - L.T.P$
1				

PROCEDURE:

1. Connect the circuit as shown in figure 1 with designed values.
2. Apply V_{CC} of 12V and an input frequency of 1KHz with an amplitude more than the designed UTP.
3. Now note down the output wave forms
4. Observe that the output comes to ON state when input exceeds UTP and it comes to OFF state when input comes below LTP
5. Observe the waveforms at V_{C1} , V_{C2} , V_{B2} and V_E and plot graphs.
6. Keep the DC- AC control of the Oscilloscope in DC mode.

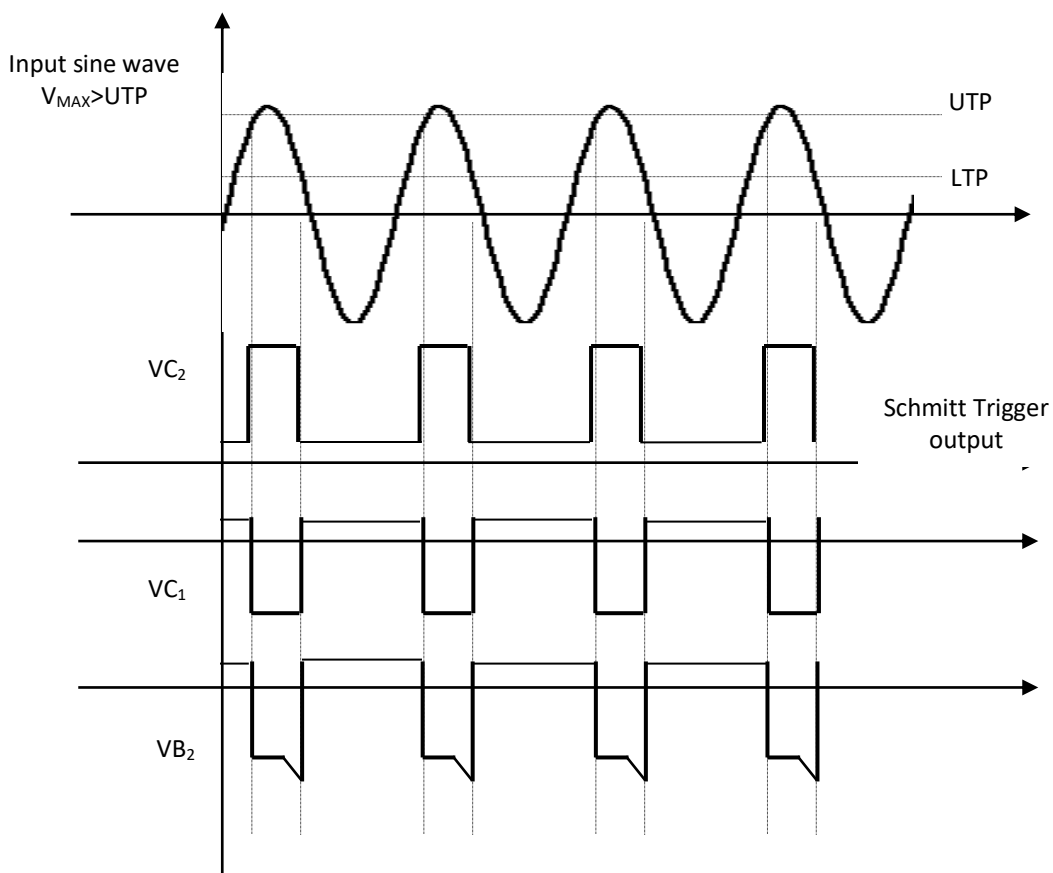
MODEL GRAPHS:

Fig 13.d: expected waveform of Schmitt trigger circuit

RESULTS :

Conclusion can be made on desined and practical values of U.T.P and L.T.P. and also made on output waveform of Schmitt trigger for the given sinusoidal input.

VIVA QUESTIONS:

1. Explain how a Schmitt trigger acts as a comparator?
2. Derive its expressions for UTP & LTP.
3. What are the applications of Schmitt Trigger?
4. Define hysteresis action?
5. Why is Schmitt Trigger called a squaring circuit?
6. What is UTP?
7. What is LTP?
8. What is the difference between a Binary and Schmitt Trigger?
9. Other names of Schmitt trigger.
10. Difference between comparator and Schmitt trigger.
11. Difference between Schmitt trigger and Multivibrator.
12. For good Schmitt trigger the hysteresis value always?
13. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=18K$, $R_{C1}=R_{C2}=2.7K$, $R_E=1.5K$
14. Design a Schmitt Trigger using npn transistor for $V_{cc}=12\text{ V}$, $UTP=3.5V$, $LTP=2.5V$, $h_{fe}=50$, $I_{C2}=2mA$
15. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=10K$, $R_{C1}=R_{C2}=3.3K$, $R_E=4.7K$
16. Design a Schmitt Trigger using npn transistor for $V_{cc}=10\text{ V}$, $UTP=5.5V$, $LTP=2.5V$, $h_{fe}=50$, $I_{C2}=3mA$
17. Design a Schmitt trigger for the Hysteresis of 3V
18. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=18K$, $R_{C1}=R_{C2}=2.7K$, $R_E=1.5K$
19. Design a Schmitt Trigger using npn transistor for $V_{cc}=12\text{ V}$, $UTP=5V$, $LTP=4.5V$, $h_{fe}=50$, $I_{C2}=1.5mA$
20. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=15K$, $R_{C1}=R_{C2}=3K$, $R_E=4K$
21. Design a Schmitt Trigger using npn transistor for $V_{cc}=10\text{ V}$, $UTP=5.5V$, $LTP=2.5V$, $h_{fe}=50$, $I_{C2}=3mA$
22. Design a Schmitt trigger for the Hysteresis of 7V
23. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=20K$, $R_{C1}=R_{C2}=4.7K$, $R_E=1.5K$
24. Design a Schmitt Trigger using npn transistor for $V_{cc}=12\text{ V}$, $UTP=5.5V$, $LTP=3.5V$, $h_{fe}=70$, $I_{C2}=5mA$

25. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=12K$, $R_{C1}=R_{C2}=3.3K$, $R_E=5.7K$
26. Design a Schmitt Trigger using npn transistor for $V_{CC}=12\text{ V}$, $UTP=5.5V$, $LTP=2.5V$, $h_{fe}=50$, $I_{C2}=5mA$
27. Design a Schmitt trigger for the Hysteresis of 5V
28. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=20K$, $R_{C1}=R_{C2}=2.7K$, $R_E=3.5K$
29. Design a Schmitt Trigger using npn transistor for $V_{CC}=12\text{ V}$, $UTP=7V$, $LTP=5.5V$, $h_{fe}=50$, $I_{C2}=3.5mA$
30. Determine UTP and LTP of a Schmitt trigger having the values , $R_1=R_2=20K$, $R_{C1}=R_{C2}=3K$, $R_E=7K$

REAL TIME APPLICATIONS OF SCHMITT TRIGGER:

1. Squaring Circuit.
2. Sine-To-Square Comparator.
3. Amplitude comparator.
4. As Flip Flops.
5. A Comparator Circuit Which Converts Any Arbitrary Signal(Slope!=1) To Square.

EXP NO: 14**MILLER SWEEP CIRCUIT**

AIM: To observe the characteristics of boot strap sweep generator

APPARATUS REQUIRED:

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	1
	(c) Capacitors	10 μ F	1
			1
	(d) Resistors	1K Ω	2
		22K Ω ,2K Ω	1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

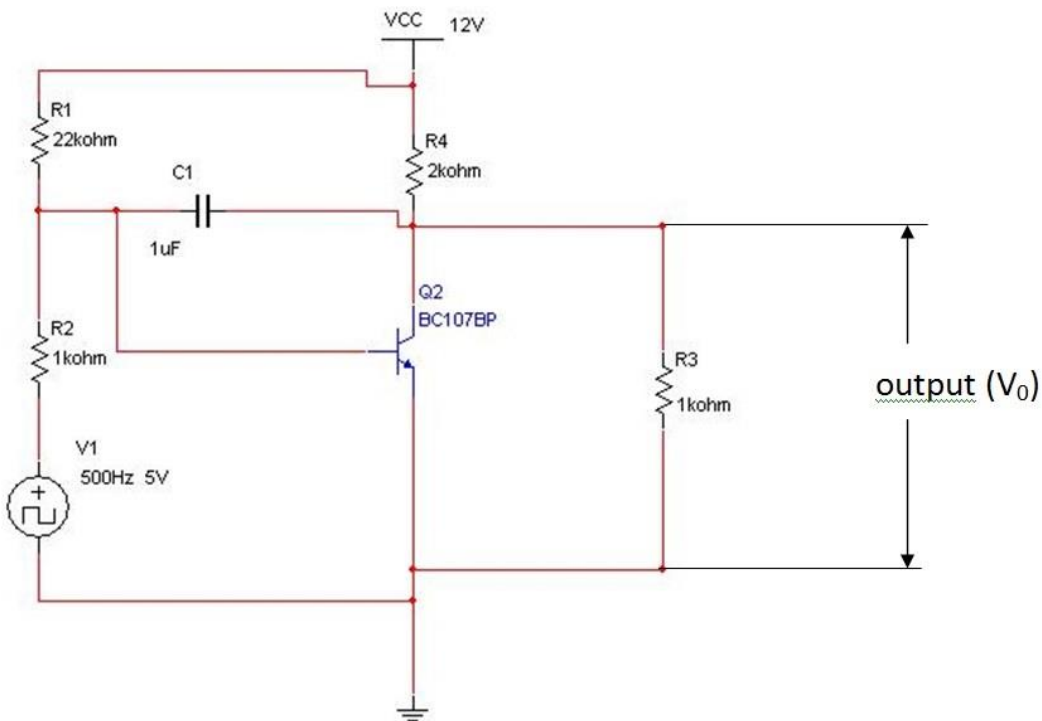
CIRCUIT DIAGRAM:

Fig: 14 a– circuit diagram of Miller sweep circuit

THEORY:

The Miller sweep circuit is an electronic circuit used to analyze the frequency response and characteristics of amplifiers, particularly to measure their bandwidth and gain-frequency relationship. It typically involves an amplifier with a capacitive feedback network that includes a variable capacitor or a capacitor in series with a resistor, which creates a sweeping effect. By varying the capacitance, the circuit effectively sweeps through a range of frequencies, allowing the observation of how the amplifier's gain changes with frequency. This sweeping process can help identify the -3 dB bandwidth of the amplifier, assess its stability, and evaluate its high-frequency performance.

PROCEDURE:

1. Connect the circuit as per the circuit diagram
2. Generate a control square wave amplitude v_c of 5v pp at 500 Hz Frequency and apply into the circuit.
3. Observe the output wave forms

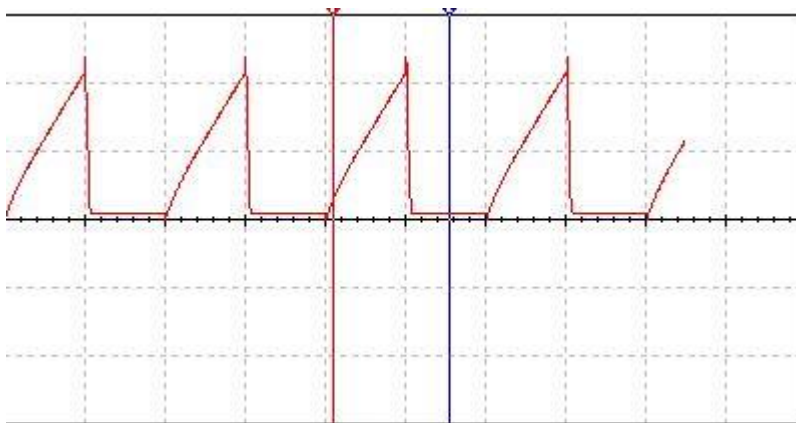
EXPECTED WAVE FORMS:

Fig: 14 b– Output waveform of Miller sweep circuit

Inference:

Conclusions can be made on sweep time T_s and retrace time T_R and sweep voltage V_I of the sweep waveform theoretically and practically and also made on if the output waveform of the Bootstrap are identical with the theoretical wave forms or not.

RESULT:

Miller sweep circuit wave forms are plotted.

VIVA QUESTIONS:

1. What is a Miller Sweep Circuit?
2. Explain the principle behind the Miller Sweep Circuit.
3. What is the role of the Miller effect in this circuit?
4. Describe the components typically used in a Miller Sweep Circuit.
5. How does the capacitor influence the sweep operation in the circuit?
6. What type of waveform is typically generated by the Miller Sweep Circuit?
7. Why is the Miller Sweep Circuit used in oscilloscopes?
8. How do you calculate the sweep rate in a Miller Sweep Circuit?
9. What is the significance of the time constant in the circuit?
10. Explain the working of the transistor in the Miller Sweep Circuit.
11. How does the biasing of the transistor affect the circuit operation?
12. What are the typical applications of the Miller Sweep Circuit?
13. Can the sweep linearity be improved in a Miller Sweep Circuit? If so, how?
14. What is the role of the feedback loop in the Miller Sweep Circuit?
15. How does changing the capacitor value affect the sweep duration?
16. What happens to the sweep signal if the resistor value is increased?
17. Why is it important to have a stable DC operating point in the circuit?
18. How does temperature affect the performance of the Miller Sweep Circuit?
19. Explain the difference between a linear and non-linear sweep in this circuit.
20. What precautions should be taken when setting up the Miller Sweep Circuit?
21. How would you troubleshoot if the circuit fails to generate the desired sweep?
22. What is the impact of parasitic capacitances on the circuit operation?

23. How does the Miller effect contribute to the circuit's high-frequency behavior?
24. What is the role of the load resistor in the Miller Sweep Circuit?
25. Why is the circuit called a "sweep" circuit?
26. How does the Miller Sweep Circuit compare to other types of sweep circuits?
27. What are the limitations of the Miller Sweep Circuit?
28. In what scenarios would you prefer a Miller Sweep Circuit over other types?
29. How does the Miller Sweep Circuit achieve frequency modulation?
30. What are the safety considerations when working with a Miller Sweep Circuit?

EXP NO: 15**BOOTSTRAP TIME BASE GENERATOR****AIM:**

To verify the output characteristics of Bootstrap sweep generator

APPARATUS:

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	1
	(c) Capacitors	1 μ F	2
		10 μ F	1
		220K Ω , 14K Ω ,	
	(d) Resistors	10K Ω	1
			1
2.	Signal generator	0.1Hz-1MHz	1
3.	CRO	0Hz-20MHz	1
4.	Connecting wires	5A	4

CIRCUIT DIAGRAM:

Fig 15.a : Circuit diagram of Bootstrap time base generator

THEORY:

A bootstrap time base generator is a type of electronic circuit used to generate a time base or timing signal, often employed in oscilloscopes and other applications requiring precise timing intervals. The circuit utilizes a bootstrap capacitor in conjunction with a timing resistor and an active device, such as a transistor or operational amplifier. The bootstrap capacitor is charged and discharged to create a periodic timing waveform. The key advantage of the bootstrap approach is its ability to provide a stable and accurate time base signal with minimal drift and variation, as the bootstrap capacitor enhances the linearity of the timing interval. This method also improves the performance of the timing circuit by reducing the impact of variations in component values and power supply fluctuations. By adjusting the resistor and capacitor values, the frequency and duty cycle of the generated time base signal can be precisely controlled, making it ideal for applications requiring reliable and consistent timing signals.

PROCEDURE:

1. Connect the circuit diagram as shown in the figure .(1) Apply +15V (V_{CC}) & -15V ($-V_{EE}$) DC as power supply to the circuit.
2. Apply 1kHz symmetrical square wave signal with the help of signal generator.
3. Observe the input and output wave forms of CRO and plot the waveforms.
4. Calculate the sweep & retrace time from the CRO .
5. Clarify the values with the theoretical calculation

THEORITICAL CALCULATION:

$$T_s = R_{c1} \cdot C_s$$

$$T_r = \left(\frac{C_s V_s}{V_{CC}} \right) / \left[\frac{h_{fe}}{R_B} - \frac{1}{R_{c1}} \right]$$

$$\text{Whose } V_s = \frac{V_{CC} T_g}{R_{c1} C_s}$$

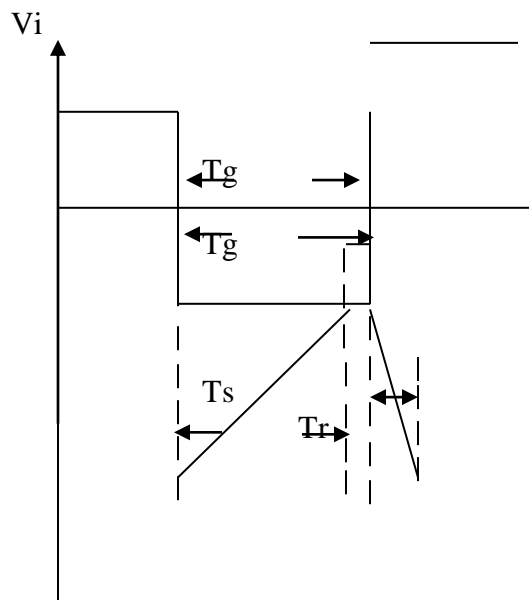
EXPECTED WAVE FORMS :

Fig 15.b:Expected waveform of bootstrap time base generator

OBSERVATION TABLE:

S.No	Theoretical Time Period(T)	Practical Time Period (T) =Ts + Tr
1		

RESULT:

The wave forms shown in figure are observed.

VIVA QUESTIONS:

1. Explain the basic principle involved in Bootstrap Sweep generator.
2. Mention the type of feedback employed in Bootstrap Sweep generator.
3. Mention the characteristics of the amplifier used in Bootstrap sweep generator.
4. What is meant by Bootstrap sweep generator?
5. How much is the amplifier gain for Bootstrap sweep generator.
6. The most important application of time base generator is_____
7. Write the sweep time of a UJT expression.
8. Write the methods of generating time base wave forms.
9. Which oscillator generates the non-sinusoidal wave forms
10. Write the expression for sweep speed error.
11. Define (a) Voltage time base generator, (b) current time base generator (c) linear time base generator.
12. What is the relation between the slope error, displacement error and transmission error?
13. What are the various methods of generating time base wave-form?
14. Which amplifier is used in Boot-strap time base generator?
15. Which amplifier is used in Boot-strap time base generator?
16. Which type of sweep does a bootstrap time-base generator produce?
17. What is the gain of the amplifier used in Bootstrap time base generator?
18. What is retrace time? Write the formula for the same for Bootstrap time base generator.
19. What is the formula for sweep amplitude in Bootstrap time base generator?
20. To have less flatness time of sweep signal, then the gate signal time has to be ____.
21. A Bootstrap sweep circuit employs ____ type of feedback.
22. Which amplifier is used in Boot-strap time base generator?
23. Which type of sweep does a bootstrap time-base generator produce?
24. Design a Bootstrap Sweep generator for $V_{cc}=12V$, $h_{fe}=20$, $R_{c1}=11.2K$, $R_b=150K$, $C_s=0.8\mu F$, $C_b=8.8\mu F$ and $R_e=5.8K$.
25. Find a reasonable value for R_b , where R_b is the collector to base resistor for a 20V sweep in $560\mu sec$. Assume $h_{fe}=50$, $R_{c1}=5K$, $T_g=500msec$
26. Design a Bootstrap Sweep generator for $V_{cc}=12V$, $h_{fe}=20$, $R_{c1}=11.2K$, $R_b=150K$, $C_s=0.8\mu F$, $C_b=5.8\mu F$ and $R_e=5.8K$.

27. Find a reasonable value for R_b , where R_b is the collector to base resistor for a 20V sweep in 400 μ sec. Assume $h_{fe}=50$, $R_{c1}=5K$, $T_g=20msec$
28. Design a Bootstrap Sweep generator for $V_{cc}=12V$, $h_{fe}=20$, $R_{c1}=11.2K$, $R_b=150K$, $C_s=0.8\mu F$, $C_b=8\mu F$ and $R_e=5.8K$.
29. Find a reasonable value for R_b , where R_b is the collector to base resistor for a 20V sweep in 550 μ sec. Assume $h_{fe}=50$, $R_{c1}=5K$, $T_g=560msec$
30. Design a Bootstrap Sweep generator for $V_{cc}=12V$, $h_{fe}=20$, $R_{c1}=11.2K$, $R_b=150K$, $C_s=0.8\mu F$, $C_b=6.8\mu F$ and $R_e=5.8K$.

REAL TIME APPLICATIONS OF A BOOTSTRAP TIME-BASE GENERATOR :

1. A bootstrap time-base generator produces a positive-going sweep.
2. Bootstrap time-base generator, a non inverting amplifier with unity gain is required.

EXP NO 16: CASCODE AMPLIFIER CIRCUIT /DARLINGTON PAIR CIRCUIT**EXPT NO: 16.****CASCODE AMPLIFIER (Software)**

AIM: To study the frequency response of amplifier, calculate voltage gain and bandwidth from the response.

APPARATUS:

1.Regulated power supply	-	1 No.
2.Function generator	-	1 No.
3.CRO	-	3 No.
4.Transistor (BC 107 or 2N2222)	-	2 No.
5.Resistors (57.3K Ω ,3.15K Ω , 300 Ω ,1K Ω)	-	1 No. each
6.Resistor (4.7K Ω)	-	2 Nos.
7.Capacitors (10 μ F, 100 μ F)	-	3,1No. each
8.Bread Board	-	1 No.
9.Connecting wires		

SOFTWARE USED: Multisim V13.0

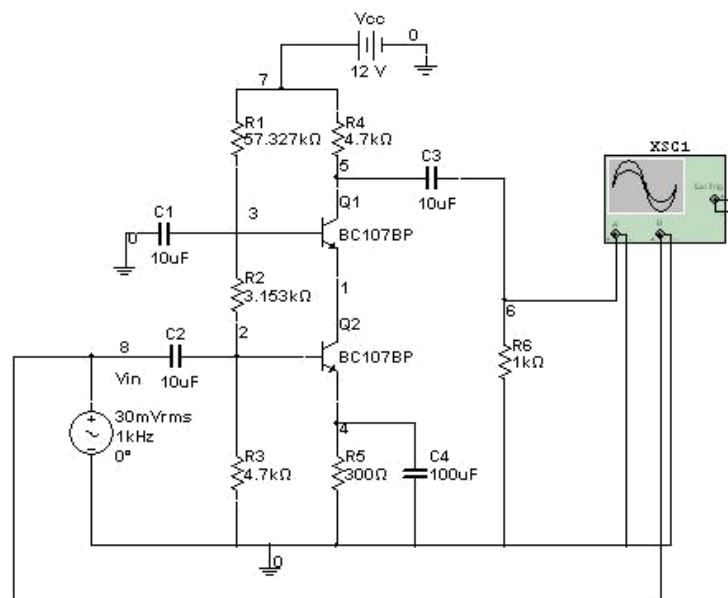
CIRCUIT DIAGRAM:

Fig: 16.a Cascode Amplifier circuit diagram

THEORY:

A cascode amplifier is a type of multi-stage amplifier configuration that enhances performance by stacking two transistor stages in series. In this arrangement, the output of the first transistor stage is connected to the input of the second transistor stage. The primary advantage of a cascode amplifier is its improved gain and bandwidth performance compared to a single transistor stage. The lower transistor, often referred to as the "common-emitter" or "common-source" transistor, provides high voltage gain, while the upper transistor, known as the "common-base" or "common-gate" transistor, improves the overall stability and reduces the Miller effect by minimizing the feedback capacitance between the stages. This configuration effectively increases the amplifier's high-frequency response and reduces distortion. The cascode amplifier is particularly useful in applications requiring high-frequency performance and low noise, such as in RF amplifiers and analog signal processing. Its design enhances input and output impedance matching, making it a valuable circuit for high-performance and high-precision electronic systems.

PROCEDURE:

1. Switch ON the computer and open the multisim software.
2. Check whether the icons of the instruments are activated and enable.
3. Now connect the circuit using the designed values of each and every component.
4. Connect the function generator with sine wave of 50mVp-p as input at the input of terminals of the circuit.
5. Connect the Cathode Ray Oscilloscope (CRO) to the out put terminals of the circuit.
6. Go to simulation button click it for simulation process.
7. From the CRO note the following values
 2. Input voltage $V_i =$
 3. Output voltage $V_0 =$
 4. Voltage gain $A_v = V_0/V_i =$
 5. Phase shift $\theta =$
8. To study the frequency response click the AC analysis, so that a screen displays the following options
9. Start frequency
10. Assign the proper values for start frequency, stop frequency and vertical scale according to the circuit requirements and observe the frequency response.
11. From the frequency response calculate the maximum gain $A_{V_{max}} =$

lower cutoff frequency (f_1) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value

at $A_{V_{\max}}/\sqrt{2}$ (linear scale) =

Higher cutoff frequency (f_2) at $A_{V_{\max}}-3\text{dB}$ (decibel scale) value

at $A_{V_{\max}}/\sqrt{2}$ (linear scale) =

OBSERVATIONS:

From CRO:

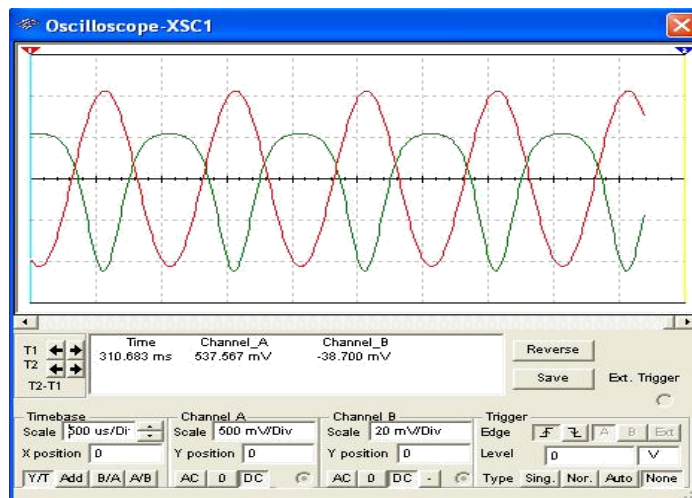


Fig: 16.b Output waveform of cascode amplifier

5. Input voltage V_i =
6. Output voltage V_0 =
7. Voltage gain $A_v = V_0/V_i$ =
8. Phase shift θ =

From Frequency response:

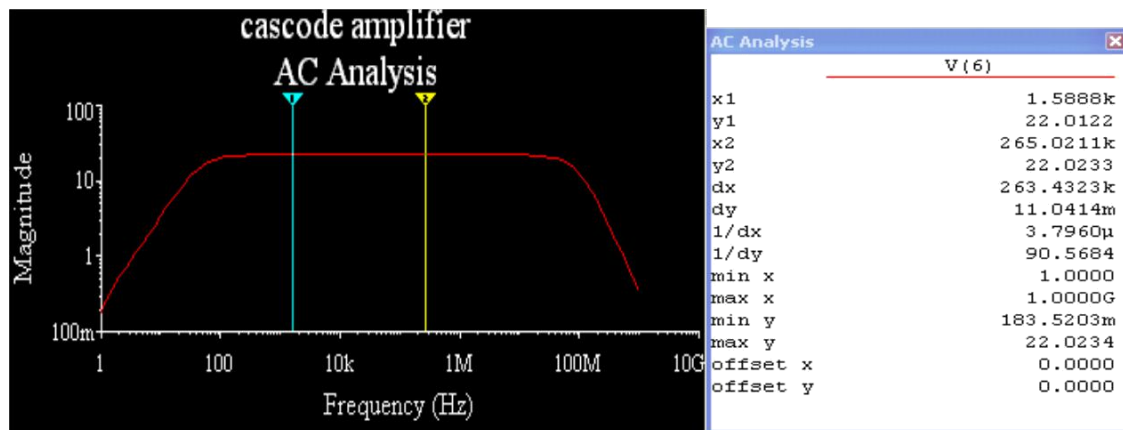


Fig: 16.c Frequency response of cascode amplifier

4. Maximum gain $A_{V_{\max}}$ =

5. Lower cutoff frequency(f_1) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value
at $A_{V_{max}}/\sqrt{2}$ (linear scale) =

6. Higher cutoff frequency(f_2) at $A_{V_{max}}-3\text{dB}$ (decibel scale) value
at $A_{V_{max}}/\sqrt{2}$ (linear scale) =

CALCULATIONS:

$$\text{Band width (BW)} = f_2 - f_1$$

RESULT: Cascode amplifier is design with the given specifications and from observed frequency response, gain and band width are calculated.

APPLICATION:

3. It is used in RF tunner.
4. Used in Amplitude Modulation.

EXP NO: 16**CASCODE AMPLIFIER (HARDWARE)**

AIM: to study the frequency response of amplifier, calculate voltage gain and bandwidth from the response.

COMPONENTS & EQUIPMENTS REQUIRED: -

S.No	Device	Range/Rating	QTY
1.	(a) DC supply voltage	12V	1
	(b) Transistor	BC107	2
	(c) Capacitors	10 μ F	3
		100 μ F	1
	(d) Resistors	56K Ω , 3.3K Ω , 330 Ω , 1K Ω	1
		4.7K Ω	2

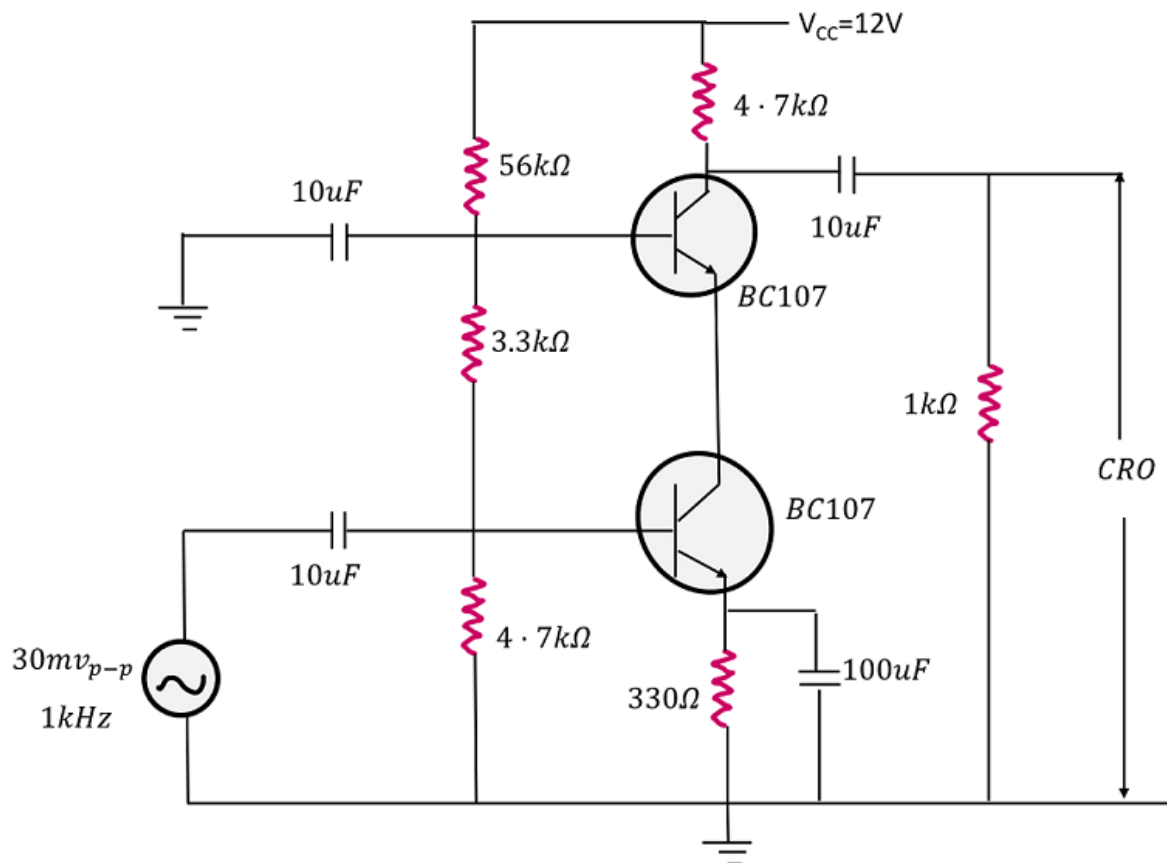


Fig: 16.d Cascode Amplifier circuit diagram

PROCEDURE: -

1. Connect the circuit diagram as shown in figure.
2. Adjust input signal amplitude in the function generator and observe an amplified voltage at the output without distortion.
3. By keeping input signal voltage, say at 50mV, vary the input signal frequency from 0 to 1MHz in steps as shown in tabular column and note the corresponding output voltages.

PRECAUTIONS:

Avoid loose connections and give proper input Voltage

TABULAR COLUMN :

Input $V_i = 50\text{mV}$

Frequency(Hz)	Output voltage V_o	Gain $= V_o / V_i$	Gain in dB $= 20\log(V_o / V_i)$
50Hz			
100Hz			
1KHz			
10KHz			
50KHz			
100KHz			
500KHz			
1MHz			

RESULT:

4. Frequency response of Cascode amplifier graph is plotted.
5. Gain = _____dB (maximum).
6. Bandwidth= $f_H - f_L =$ _____Hz.

VIVA QUESTIONS:

1. Why the case code amplifier provides a phase reversal?
2. In the dc equivalent circuit of an amplifier, how are capacitors treated?
3. What is the effect of bypass capacitor on frequency response?
4. Define lower and upper cutoff frequencies for an amplifier.
5. State the reason for fall in gain at low and high frequencies.
6. What is meant by unity gain frequency?
7. Define Bel and Decibel.
8. What do we represent gain in decibels?
9. Why do you plot the frequency response curve on a semi-log paper?
10. Explain the function of emitter bypass capacitor C_E ?
11. What is the equation for voltage gain?
12. What is cut off frequency? What is lower 3dB and upper 3dB cut off frequency?
13. What are the applications of Case code amplifier?
14. What is active region?
15. What is Bandwidth of an amplifier?
16. What is the importance of gain bandwidth product?
17. Draw h parameter equivalent circuit of Case code amplifier.
18. What is the importance of coupling capacitors in Case code amplifier?
19. What is the importance of emitter by pass capacitor?
20. What type of feedback is used in case code amplifier?
21. What are the various types of biasing a Transistor?
22. What is Q point of operation of the transistor? What is the region of operation of the transistor when it is working as an amplifier?
23. Why frequency response of the amplifier is drawn on semi-log scale graph?
24. If Q point is not properly selected, then what will be the effect on the output waveform?
25. What are the typical values of the input impedance and output impedance of case code amplifier?
26. What is meant by unity gain frequency?
27. In the dc equivalent circuit of an amplifier, how are capacitors treated?
28. What is the effect of bypass capacitor on frequency response?
29. Define lower and upper cutoff frequencies for an amplifier.
30. State the reason for fall in gain at low and high frequencies.

EXERCISE PROBLEMS:

1. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
2. Plot the frequency response of BC 107 amplifier with $C_2 = 5 \mu\text{F}$ with triangular i/p.
3. Plot the amplitude response of BC 107 amplifier with $R_1 = 4.1 \text{ K}$.
4. Plot the amplitude response of BC 107 amplifier with $R_2 = 9.4 \text{ K}$ triangular i/p.
5. Plot frequency response of BC 107 amplifier $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
6. Plot the frequency and amplitude response of BC 107 amplifier with $C_1 = 5 \mu\text{F}$.
7. Plot frequency response of BC107 $R_1 = 4.1 \text{ K}$, $R_2 = 9.4 \text{ K}$ with square i/p.
8. Plot the frequency and amplitude response of BC107 amplifier with $C_1 = 10 \mu\text{F}$.
9. Plot the frequency response of BC 107 amplifier with $C_2 = 2 \mu\text{F}$ with i/p.
10. Plot the amplitude response of BC 107 amplifier with $R_1 = 2.1 \text{ K}$.