



Department of Electronics & Communication Engineering

III Year B.Tech. ECE - I Sem

L T/P/D C

0 /3/- 2

IC APPLICATIONS AND HDL SIMULATION LAB

Note: Minimum of 16 experiments have to be conducted (at least Seven from each part):

Part-I

Linear IC Experiments

1. Op-amp Applications-Adder, Subtractor, Comparator
2. Integrator and Differentiator using IC741 Op-Amp.
3. Active Filter Applications-LPF,HPF(First Order)
4. IC 741 waveform Generators- Sine, Square wave and Triangular waves
5. IC 555 Mono Stable and Astable Multivibrator Circuits
6. Schmitt Trigger Circuits-using IC741
7. IC 565 – PLL applications
8. Voltage regulator IC 723, three terminal voltage regulators- 7805, 7809, 7912.

Part-II

HDL Simulation Programmes


1. HDL Code to Realize the all logic gates
2. Design of 2 to 4 Decoder
3. Design of 8-to-3 encoder(without and with priority)
4. Design of 8-to-1 multiplexer and 1-to-8 demultiplexer
5. Design of 4 bit binary to gray code converter
6. Design of 4 bit comparator
7. Design of Full adder using 3 modeling Styles
8. Design of Flip-Flops: SR,D,JK,T
9. Design of 4-bit binary, BCD Counters (Synchronous/Asynchronous reset)
10. Finite State Machine Design

Part-I**INTRODUCTION TO IC APPLICATIONS LAB**

The operational amplifier forms the basic building block for most of the linear IC's. It is a direct coupled high gain amplifier usually consisting of one or more differential amplifiers and followed by a level translator and an output stage. A few applications of an Op-amp are, instrumentation, voltage to current or current to voltage converter, integrator, Differentiator, oscillators, Filters, clippers and Clampers, sample and hold, analog to digital converter, adder, sub tractor, scale changer, comparator etc.,

Now-a-days, the op-amp has become a basic analog building block common to a number of electronic functions performed in instrumentation, computation and control. Op-amp is basically a differential amplifier whose basic function is to amplify the difference between two input signals. Therefore it is also called as "difference amplifier". The bias levels and the gain characteristic of a differential stage depend on the symmetry, between two branches of the circuit. The balanced nature of the differential amplifiers makes it ideal as a gain block for monolithic op-amp, since the close matching and the temperature tracking properties of monolithic components are far better than their discrete counter parts.

 The ideal operational amplifier is shown in fig. below



A signal appearing at the negative terminal (V_1) is inverted at the output, a signal at the positive terminal (V_2) appears at the output with no change in sign. Hence the negative terminal is called the "inverting" the positive terminal the "non-inverting" terminal, In general, the output voltage is directly proportional to $V_d = (V_1 - V_2)$. The constant of proportionality $-A$, is the voltage gain of the amplifier.

The operational amplifier is a direct-coupled high gain amplifier to which feedback

is added to control its overall response characteristics. It is often referred to as the basic linear integrated circuit.


The ideal OP-amp has the following characteristics:

Properties	Ideal	Typical
Open loop gain	∞	Very high ($\geq 10^4$)
Open loop bandwidth	∞	Very high
Common-mode rejection ratio	∞	High ($> 70\text{dB}$)
Input resistance	∞	High ($\geq 10\text{M}\Omega$)
Output resistance	0	Low ($< 500\ \Omega$)
Off-set voltage and current	0	Low ($< 10\text{mV}, < 0.2\text{nA}$)

General Description:

The LM 741series is general purpose operational amplifiers which feature improved performance over industry standards like the LM 709. They are direct, plug-in replacements for the 709C, LM 201, MC 1439 and 748 in most applications.

 The amplifiers offer many features which make their application nearly fool proof: Overload protection on the input and output, no latch-up when the common mode range is exceeded, as well as freedom from oscillations.



EXPERIMENT-1**OP-AMP Applications-ADDER, SUBTRACTOR&COMPARATOR**

Aim: To study the applications of operational amplifier.

Equipment required:

- | | |
|------------------------------------|--------|
| 1. Bread Board | - 1no. |
| 2. Function Generator (0-30V dual) | - 1no. |
| 3. Digital multimeter | - 1no. |
| 4. CRO(20 MHz) | - 1no. |
| 5. IC 741 | - 1no. |
| 6. Connecting wires. | |

 
Circuit Diagram:**1.Summing Amplifier**

Fig 1a) Inverting Configuration

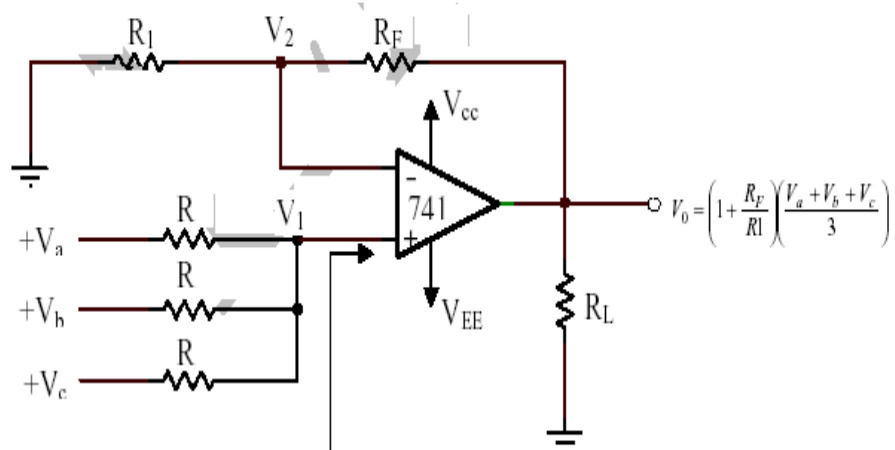


Fig 1b) Non Inverting Configuration

2. Subtractor


 


Fig 2: Subtractor

3. Basic Comparator

 

MODEL GRAPH:

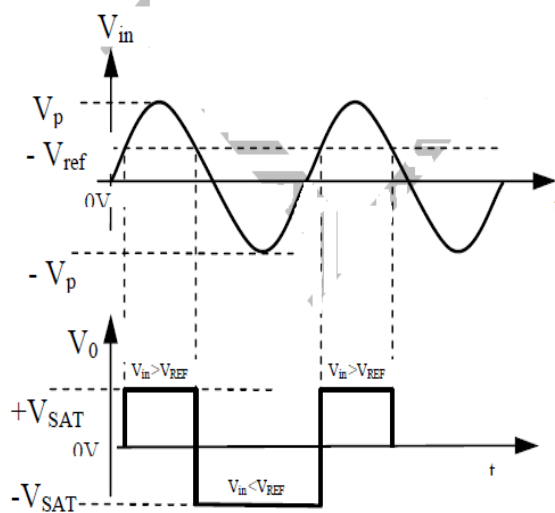


Fig.3(b) if V_{ref} is positive

 


Fig.3(c) if V_{ref} is negative

THEORY:

1. Summing amplifiers

Fig. shows a summing amplifier or adder circuit. Here, the output is a linear summation of a number of input signals. Here, the feedback force virtual ground to exist at the inverting

input to the ideal amplifier. Furthermore the input current to the ideal amplifier is zero.

Hence, the current i is given as

$$i = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n}$$

and $V_o = -R_f i$.

$$V_{out} = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$

Thus the output voltage is equal to the negative weighted Sum of the input voltages. The summing operation depends exclusively on the sum of the resistance ratios. The circuit is also known as Scaling or weighted amplifier.

If $R_1 = R_2 = \dots = R_n$ then

$$V_o = -\frac{R_f}{R_1} (V_1 + V_2 + \dots + V_n)$$

and the output is proportional to the sum of the inputs.

The circuit is widely used to form linear combinations of various signals. in analog computers. The virtual ground at the summing node prevents any interaction between the various signal sources connected to the input terminals. The output impedance of the summing amplifier is zero. The input impedance is different for each input signal. Because of the virtual ground at the summing node, the input impedance seen by each signal source is simply the resistance connecting that source to the summing node.

2. Subtractor

A basic differential amplifier can be used as a subtractor as shown in figure 2. In this figure, input signals can be scaled to the desired values by selecting appropriate values for the external resistors; when this is done, the circuit is referred to as scaling amplifier. However, in figure 3 all external resistors are equal in value, so the gain of the amplifier is equal to 1. From the figure, the output voltage of the differential amplifier with a gain of 1 is

$$I_1 = \frac{V_1 - V_a}{R_1}, \quad I_2 = \frac{V_2 - V_b}{R_2}, \quad I_f = \frac{V_a - (V_{out})}{R_3}$$

$$\text{Summing point } V_a = V_b$$

$$\text{and } V_b = V_2 \left(\frac{R_4}{R_2 + R_4} \right)$$

$$\text{If } V_2 = 0, \text{ then: } V_{out(a)} = -V_1 \left(\frac{R_3}{R_1} \right)$$

$$\text{If } V_1 = 0, \text{ then: } V_{out(b)} = V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$$

$$V_{out} = -V_{out(a)} + V_{out(b)}$$

$$\therefore V_{out} = -V_1 \left(\frac{R_3}{R_1} \right) + V_2 \left(\frac{R_4}{R_2 + R_4} \right) \left(\frac{R_1 + R_3}{R_1} \right)$$

When resistors, $R_1 = R_2$ and $R_3 = R_4$ the above transfer function for the differential amplifier can be simplified to the following expression:

Differential Amplifier Equation

$$V_{OUT} = \frac{R_3}{R_1} (V_2 - V_1)$$

Thus the output voltage V_0 is equal to the voltage applied to the non inverting terminal (V_b) minus the voltage applied to the inverting terminal (V_a); hence the circuit is called a subtractor.

3. Basic comparator:

Figure (3) shows an op-amp used as a comparator. A fixed reference voltage V_{ref} of 1V is applied to the (-) input, and the other time-varying signal voltage V_{in} is applied to the (+) input. Because of this arrangement, the circuit is called the non inverting comparator. When V_{in} is less than V_{ref} , the output voltage V_0 is at $-V_{sat}(-V_{EE})$ because the voltage at the (-) input is higher than that at the (+) input. On the other hand, when V_{in} is greater than V_{ref} , the (+) input becomes positive with respect to the (-) input, and V_0 goes to $+V_{sat}(+V_{CC})$. Thus V_0 changes from one saturation level to another whenever $V_{in} < \text{or} >$

V_{ref} , as shown in figure 3(b). In short, the comparator is a type of analog-to-digital converter. At any given time the V_o waveform shows whether V_{in} is greater or less than V_{ref} . The comparator is sometimes also called a voltage-level detector because, for a desired value of the voltage level of V_{in} can be detected.

PROCEDURE:**Part 1: ADDER:**

1. Connect the circuit as shown in figure(1).
2. Apply different DC input voltages at V_a, V_b , and V_c and measure the output voltage V_o using a multi meter It should be $V_o = V_a + V_b + V_c$.

Part 2: SUBTRACTOR:

1. Connect the circuit as shown in figure(2).
2. Apply different DC input voltages at V_a , and V_b and measure the output voltage V_o using a multi meter. It should be $V_o = V_b - V_a$.

Part 3: COMPARATOR:

1. Connect the circuit as shown in figure(3a).
2. Apply a reference voltage of (say 1V), to inverting terminal of op-amp.
3. Apply a sinusoidal wave with a peak voltage more than V_{ref} to OP-AMPs Non-inverting terminal.
4. Observe the output at pin number 6, which will be a square wave with peak to peak voltage of (V_{sat} to $-V_{sat}$).
5. Observe that when V_{ref} is less than V_{in} , then the output goes to $+V_{sat}$,
When V_{ref} is greater than V_{in} then output goes to $-V_{sat}$.
6. Now set another reference voltage and repeat the steps 4 and 5.
7. Draw the observed waveforms on graph sheet and obtain the practical reference voltage.

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the continuity of the connecting wires.

INFERENCE:

- i. The working of summing amplifier is observed & the output is calculated theoretically and practically.

- ii. The working of subtractor is verified and the output is obtained, the output is calculated theoretically and practically.
- iii. The working of comparator is observed and the output is plotted, the time period & Frequency of the output wave form is calculated.

Applications:

1. Summing amplifiers are used in amplifiers are used in an audio mixer to add different signals with equal gains.
2. Differential amplifiers are used in Instrumentation amplifiers.
3. Comparators used in
 - i. Zero crossing detector
 - ii. Window detector
 - iii. Time marker generator
 - iv. Phase meter.

Result:

Hence the operation of Adder, Subtractor, and comparator (using 741 op amp) is verified.

Review Questions:

1. What is an operational Amplifier?
2. Characteristics of ideal op-amp?
3. Define CMRR?
4. Why op-amp s called as 741 ?
5. Name three important specifications of IC op-amp?
6. Define slew rate of op-amp
7. What is the input offset voltage of 741c op-amp
8. Define power supply sensitivity.
9. Which pins of 741 IC are called null set pins.
10. What is the bandwidth of practical op-amp.

Exercise Problems:

1. Design an adder circuit using 741 op-amp to add 2V and 4V signal.
2. Design 3 input adder circuit using 741 op-amp to add 3V and 4V and 1V signal.
3. Design a subtractor circuit using 741 op-amp to subtract 4V and 2V signal.
4. Design a comparator circuit to generate square wave output with reference voltage 2V DC.
5. Generate a square wave by using zero cross detector.
6. Design a false triggering circuit with $v_{ref}=2V$ and input 5v sinusoidal signal
7. Design an adder circuit using 741 op-amp to add 2v and 4v signal .
8. Design 3 input adder circuit using 741 op-amp to add 1v and 2v and 3v signal.
9. Design a comparator circuit to generate square wave output with reference voltage 4v DC
10. Design a subtractor circuit using 741 op-amp to subtract 3v and 1v signal.
11. Design a adder circuit to add $V_0=V_a+V_b+V_c$.
12. Design a subtractor circuit to give $V_0=V_a-V_b$
13. Generate a square wave by using zero cross detector and what are the applications of comparator
14. Design an amplifier with a gain of +5V using one op-amp
15. Design a adder circuit to add $V_0=V_a+V_b+V_c+V_d$

EXPERIMENT-2

INTEGRATOR AND DIFFERENTIATOR USING IC 741

AIM: Design and verify the functionality of Differentiator and Integrator using IC 741 Op-Amp.

EQUIPMENT REQUIRED:

1. Operational Amplifier uA 741 IC – 2No.
2. Resistors

1K Ω	1No.
1.5 K Ω	1No.
10 K Ω	1No.
15 K Ω	1No.

3. DC Power supply (0-30V) - 1No.
4. Bread board - 1No.
5. CRO (20MHz/30MHz) - 1No.
6. Capacitor(0.1 μ F) -1No.

CIRCUIT DIAGRAM:

Fig 1: Integrator


 


Fig 2: Differentiator

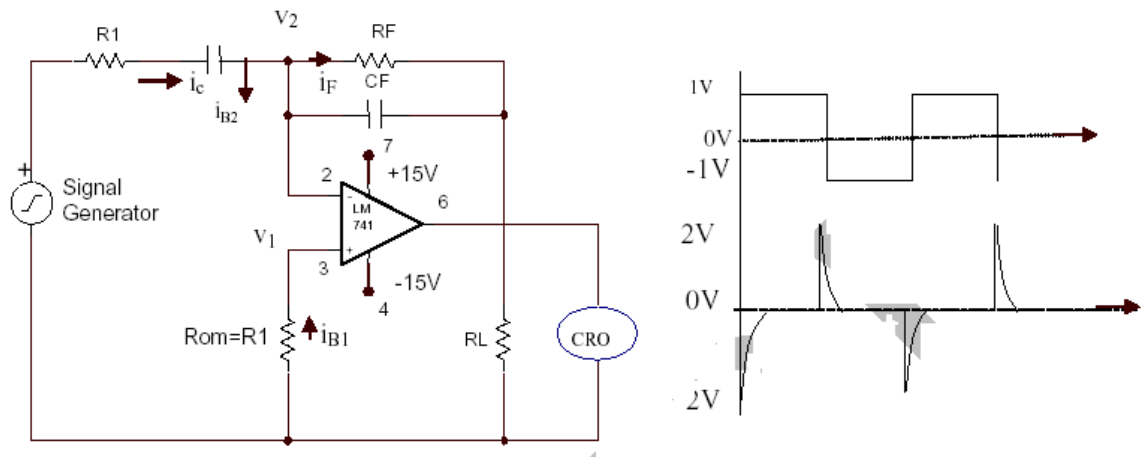

THEORY:

A) INTEGRATOR:

A circuit in which “the output voltage waveform is the integral of the input voltage waveform” is the integrator or the integration amplifier. Such a circuit is obtained by using a basic inverting amplifier configuration, if the feedback resistor R_F is replaced by a capacitor C_F .

Analysis of Integrator Circuit:

We know from first principals that the voltage on the plates of a capacitor is equal to the charge on the capacitor divided by its capacitance giving Q/C . Then the voltage across the capacitor is output V_{out} therefore: $-V_{out} = Q/C$. If the capacitor is charging and discharging, the rate of change of voltage across the capacitor is given as:

$$V_c = \frac{Q}{C}, \quad V_c = V_x - V_{out} = 0 - V_{out}$$

$$\therefore -\frac{dV_{out}}{dt} = \frac{dQ}{C dt} = \frac{1}{C} \frac{dQ}{dt}$$

But dQ/dt is electric current and since the node voltage of the integrating op-amp at its inverting input terminal is zero, $X = 0$, the input current I_{in} flowing through the input resistor, R_{in} is given as:

$$I_{in} = \frac{V_{in} - 0}{R_{in}} = \frac{V_{in}}{R_{in}}$$

The current flowing through the feedback capacitor C is given as:

$$I_f = C \frac{dV_{out}}{dt} = C \frac{dQ}{Cdt} = \frac{dQ}{dt} = \frac{dV_{out} \cdot C}{dt}$$

Assuming that the input impedance of the op-amp is infinite (ideal op-amp), no current flows into the op-amp terminal. Therefore, the nodal equation at the inverting input terminal is given as:

$$I_{in} = I_f = \frac{V_{in}}{R_{in}} = \frac{dV_{out} \cdot C}{dt}$$

$$\therefore \frac{V_{in}}{V_{out}} \times \frac{dt}{R_{in} C} = 1$$

From which we derive an ideal voltage output for the **Op-amp Integrator** as:

$$V_{out} = -\frac{1}{R_{in} C} \int_0^t V_{in} dt = -\int_0^t V_{in} \frac{dt}{R_{in} \cdot C}$$

To simplify the math's a little, this can also be re-written as:

$$V_{out} = -\frac{1}{j\omega RC} V_{in}$$

Where $\omega = 2\pi f$ and the output voltage V_{out} is a constant $1/RC$ times the integral of the input voltage V_{in} with respect to time. The minus sign (-) indicates a 180° phase shift because the input signal is connected directly to the inverting input terminal of the op-amp.

B) Differentiator:

The input signal to the differentiator is applied to the capacitor. The capacitor blocks any DC content so there is no current flow to the amplifier summing point, X resulting in zero output voltage. The capacitor only allows AC type input voltage changes to pass through and whose frequency is dependant on the rate of change of the input signal.

At low frequencies the reactance of the capacitor is “High” resulting in a low gain (R_f/X_c) and low output voltage from the op-amp. At higher frequencies the reactance of

the capacitor is much lower resulting in a higher gain and higher output voltage from the differentiator amplifier.

However, at high frequencies an op-amp differentiator circuit becomes unstable and will start to oscillate. This is due mainly to the first-order effect, which determines the frequency response of the op-amp circuit causing a second-order response which, at high frequencies gives an output voltage far higher than what would be expected. To avoid this the high frequency gain of the circuit needs to be reduced by adding an additional small value capacitor across the feedback resistor R_f .

Ok, some math's to explain what's going on!. Since the node voltage of the operational amplifier at its inverting input terminal is zero, the current, i flowing through the capacitor will be given as:

$$I_{IN} = I_F \text{ and } I_F = -\frac{V_{OUT}}{R_F}$$

The charge on the capacitor equals Capacitance x Voltage across the capacitor

$$Q = C \times V_{IN}$$

The rate of change of this charge is:

$$\frac{dQ}{dt} = C \frac{dV_{IN}}{dt}$$

but dQ/dt is the capacitor current, i

$$I_{IN} = C \frac{dV_{IN}}{dt} = I_F$$

$$\therefore -\frac{V_{OUT}}{R_F} = C \frac{dV_{IN}}{dt}$$

from which we have an ideal voltage output for the op-amp differentiator is given as:

$$V_{OUT} = -R_F C \frac{dV_{IN}}{dt}$$

Therefore, the output voltage V_{out} is a constant $-R_f.C$ times the derivative of the input

voltage V_{in} with respect to time. The minus sign indicates a 180° phase shift because the input signal is connected to the inverting input terminal of the operational amplifier.

PROCEDURE:

1. By using the component values as per the above specified design, Connect the circuit as shown in the figure.
2. Apply the $1V_{P-P}$, 1 KHz Sine wave or Square wave as input
3. Observe the output on CRO.
4. Draw the input and output Signals on the Graph paper.

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the continuity of the connecting wires.

INFERENCE:

- i. The working of differentiator and integrator is observed and the output is plotted.
- ii. The time period of the output waveform is calculated.
- iii. The maximum frequency of differentiation and integration is observed.

Applications:

- i. In Electronic Analog computation.
- ii. In generation of step, ramp, square waveforms.
- iii. In ADC's.

Result:

Hence the output of an active integrator and differentiator using op-amp 741 for a given input signal is observed .

Review Questions:

1. Integration of step function
2. Draw the output waveform for the non inverting integrator for square wave.
3. Draw the output waveform for the inverting differentiator for square wave.
4. Difference between integrator and differentiator circuit.
5. Write the equation for integrator and differentiator inverting and non-inverting amplifier.
6. What are the drawbacks of ideal differentiator?
7. What are the drawbacks of ideal integrator?
8. What is the differentiation of Ramp function
9. What are the applications of Integrator?
10. What are the applications of Differentiator.

Exercise Problems:


1. For an op-amp integrator with $R=100\text{M}\Omega$ and $C=1\mu\text{F}$ Determine the value of V_0
2. Design a differentiator to differentiate an input signal that varies in frequency from 10Hz to about 1kHz
3. Design a differentiator to differentiate an input signal with $f_{\text{max}}=100\text{Hz}$
4. Design a practical integrator circuit to properly process input sinusoidal waveforms up to 1KHz
5. In the differentiator circuit with $R_1=82\Omega$, $R_{\text{om}}=R_f=1.5\text{k}\Omega$ and $C_1=0.1\mu\text{f}$, $C_f=0.05\mu\text{f}$
6. In the integrator circuit with $R_1=82\Omega$, $R_{\text{om}}=R_f=1.5\text{k}\Omega$ and $C_1=0.1\mu\text{f}$, $C_f=0.05\mu\text{f}$ the input is a sine wave with peak to peak amplitude of 3V at 200Hz. Sketch the output waveform
7. Design a differentiator to differentiate an input signal with $F_{\text{max}}=500\text{Hz}$
8. Design a differentiator to differentiate an input signal that varies in frequency from 10Hz to about 1.5 KHz.
9. In the integrator circuit with $R_1=82\Omega$, $R_{\text{om}}=R_f=1.5\text{k}\Omega$ and $C_1=0.1\mu\text{f}$, $C_f=0.05\mu\text{f}$ the input is a sine wave with peak to peak amplitude of 3V at 2KHz. Sketch the output waveform
10. Design a practical integrator circuit to properly process input sinusoidal waveforms up to 2KHz.

EXPERIMENT-3**ACTIVE FILTER APPLICATIONS – LPF, HPF (First Order)**

AIM: To Plot the frequency responses of Second order low pass and high pass filters using 741 OP-AMP and to find Higher and Lower Cut-off frequencies.

EQUIPMENT REQUIRED:

1. Signal generator (0-1MHz)
2. Oscilloscope (20/30MHz)
3. Bread board
4. Dc Power supply (0-30V)
5. Resistors 10K Ω (2 No.s),
100K Ω (1 No).
6. Capacitors 0.01 μ F -1No.
7. Op-amp 741 IC – 1No.

 CIRCUIT DIAGRAM:**Low Pass Filter**


R1=10 K Ω

R2=100 K Ω


R3=10 K Ω

C1=0.01 μ F

Vin=1p-p, 100HZ.

 

High Pass Filter

 


$R1=10\text{ K}\Omega$

$R2=100\text{ K}\Omega$

$R3=10\text{ K}\Omega$

$C1=0.01\text{ }\mu\text{F}$

$V_{in}=1\text{p-p, }100\text{Hz.}$

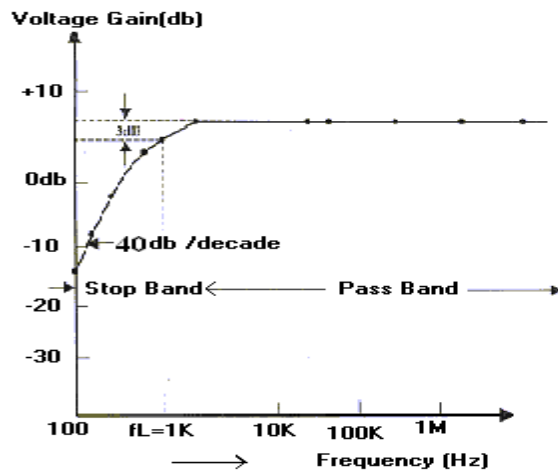

THEORY:

Low Pass Filter:

A frequency selective electric circuit that passes electric signals of specified band of frequencies and attenuates the signals of frequencies outside the band is called an electric filter. The first order low pass filter consists of a single RC network connected to the non-inverting input terminal of the operational amplifier.

Resistors R_1 and R_F determine the gain of the filter in the pass band. The low pass filter has maximum gain at $f = 0\text{Hz}$. The frequency range from 0 to f_H is called the pass band the frequency range $f > f_H$ is called the stop band.

High Pass Filter

A frequency selective electric circuit that passes electric signals of specified band of frequencies and attenuates the signals of frequencies outside the band is called an electric filter. The first order high pass filter consists of a single RC network connected to the non-inverting input terminal of the operational amplifier.

Resistors R_1 and R_F determine the gain of the filter in the pass band. The high pass filter has maximum gain at $f = f_L\text{Hz}$. The frequency range from 0 to f_L is called the stop band the frequency range $f > f_L$ is called the pass band.

PROCEDURE:**LOW PASS FILTER& HIGH PASS FILTER FREQUENCY RESPONSE**

1. Connect the circuit as shown in figure.
2. Take a signal generator and observe its output (sinusoidal signal) on CRO. Adjust the Amplitude of the sinusoidal signal (V_i) as $1V_{p-p}$. Keep its frequency as 100Hz.
3. Connect the signal generator to the input of the LPF. Using CRO observe the input and output waveforms simultaneously.
4. Vary the frequency of input signal from 100Hz to 100 KHz.
5. Measure the output voltage Amplitude (V_o) for every input frequency signal in oscilloscope.
6. Calculate the Gain of the Filter Also Calculate its dB Value.
7. Draw the graph between frequency (Hz) on X-Axis and the Gain on Y –axis on semi - log sheet.
8. Calculate the cut off frequency from the graph. This is the Practical value of Cut off frequency. [from the graph find the value of Cut off frequency, at which the Gain is 0.707 times that of Pass band gain (A_F)].
9. Compare the Practical values with Theoretical values.

OBSERVATIONS:Input Signal Amplitude(V_{in}) = $1V_{p-p}$

Frequency (Hz)	Output voltage(V_o)	Gain = V_o/V_{in}	Gain(in dB) = $20\log (V_o/V_{in})$
100Hz			
200Hz			
400Hz			
600Hz			
800Hz			
900Hz			
950Hz			
980Hz			
1KHz			
1.1KHz			
1.2KHz			
1.4KHz			
2KHz			
.			
.			
.			
.			
100KHz			

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the continuity of the connecting wires

INFERENCE:**Low Pass Filter:**

- i. The working of active low pass filter is observed and the output is plotted.
- ii. The frequency response of the low pass filter is plotted on a semi-log graph paper.
- iii. It is observed that the gain rolls off at the rate of 40dB per decade at the cut off frequency.

High Pass Filter

- i. The working of active high pass filter is observed and the output is plotted
- ii. The frequency response of the high pass filter is plotted on a semi-log graph.
- iii. It is observed that the gain increases at the rate of 40dB per decade at the cut off frequency.

Applications:**Low pass filter:**

- i. To remove high frequency noise.
- ii. To generate sweep
- iii. To generate saw-tooth waveform.

High pass filter:

- i. To remove low ripple.
- ii. To generate sweep.
- iii. To generate spike waveform.

Result:

The cut-off frequency of the low pass filter = kHz

The pass band gain of low pass filter =

The lower cutoff frequency of the high-pass filter = ----- KHz.

The pass band gain = -----

Review Questions:

1. Limitations of passive filters.
2. What are advantages of active filter over passive filter?
3. What are disadvantages of active filter over passive filter?
4. write the voltage gain equation of n^{th} order active LPF.
5. write the voltage gain equation of n^{th} order active HPF.
6. What are the applications of all pass filters?
7. Write the equation to determine the phase shift of all pass filters
8. Define quality factor.
9. What is the relation between q factor, center frequency and Bandwidth
10. What is the other name of Butterworth filter.

Exercise Problems:

1. Design a first order low pass filter with cut off frequency 2KHz
2. Design a first order high pass filter with cut off frequency 3KHz
3. Design a first order high pass filter with cut off frequency 2KHz
4. Design a first order low pass filter with cut off frequency 3KHz
5. Design a first order low pass filter with cut off frequency 2KHz and convert to a low pass filter with cut off frequency of 3.5KHz.
6. Design a first order high pass filter with cut off frequency 2KHz and convert to a low pass filter with cut off frequency of 3.5KHz.
7. Design a first order low pass filter with cut off frequency 3KHz and convert to a low pass filter with cut off frequency of 1.6KHz.
8. Design a first order high pass filter with cut off frequency 3KHz and convert to a low pass filter with cut off frequency of 1.6 KHz.
9. Using frequency scaling method find the new value of resistor in first order HPF with changed value of cut-off frequency 1.6KHz and $R_1=1K\Omega$
10. Using frequency scaling method find the new value of resistor in first order LPF with changed value of cut-off frequency 1.6KHz and $R_1=1K\Omega$

EXPERIMENT-4

IC 741 waveform Generators- Sine, Square wave and Triangular waves


AIM: To generate the Sine, Square wave and Triangular waveforms using IC 741

EQUIPMENT REQUIRED:


1. Op-Amp IC 741 - 2No.
2. Bread board
3. Capacitor $0.1\mu\text{F}$ - 3No.
4. RPS (0 - 30V) - 1No.
5. Resistors - $10\text{K}\Omega$ - 2No., $470\text{K}\Omega$ - 1No., $1\text{K}\Omega$ - 3No.
6. Connecting wires
7. CRO(20MHz)

CIRCUIT DIAGRAM:

Sine Wave Genarator:

 


Square Wave & Triangular Wave Generator:

 

THEORY:

Triangular wave is a periodic, non-sinusoidal waveform with a triangular shape. People often get confused between triangle and sawtooth waves. The most important feature of a triangular wave is that it has equal rise and fall times while a [sawtooth wave](#) has un-equal rise and fall times. The applications of triangular wave include sampling circuits, thyristor firing circuits, frequency generator circuits, tone generator circuits etc. There are many methods for generating triangular waves but here we focus on method using opamps. This circuit is based on the fact that a square wave on integration gives a triangular wave.

 

Procedure:

For Sine Wave Generation:

1. Connect the circuit as per the circuit diagram shown in Fig 1.

2. Give +12V, -12V and ground to circuit from power supply.
3. Observe the output on the CRO.
4. Calculate theoretical and practical output signal frequency and compare them.

For Square and Triangular Wave Generation:

1. Connect the circuit as per the circuit diagram shown in Fig 2.
2. Observe square wave at Vo' and Triangular wave at Vo'' as shown in figure 3.
3. Plot the waveforms on the graph sheet.
4. Calculate the frequency theoretically and compare them with the practical one.

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the continuity of the connecting wires.

INFERENCE:

- i. The working of oscillators is observed and the output is plotted.
- ii. The frequency response of oscillator is plotted.

Applications:

1. Used in sine wave oscillators for audio frequencies.
2. Used in the application of function generators.

RESULT:

By using IC 741 the sine wave, Square wave and triangular wave forms are generated.

Review Questions:

1. What are the different ways of generating Sinusoidal waves?
2. What are different ways of generating square wave voltage waveforms?
3. What is phase-shift oscillator?
4. What is formula for frequency of oscillations for RC phase shift oscillator?
5. How a triangular wave can be generated?

6. What is formula for frequency of oscillations for Astable square wave generator?
7. What is the frequency of oscillations of triangular wave when it is generated by integrating the square wave?
8. For a circuit to act as an integrator, how the time constant has to be?
9. What is barkhausen criterion for oscillations?
10. Why three RC sections are used in the feedback for RC phase shift oscillator?

Exercise Problems:

1. Design an op-amp circuit to generate a sinusoidal waveform using $33\text{K}\Omega$, and $0.01\mu\text{f}$ capacitor and $3.3\text{K}\Omega$ resistor.
2. Design an op-amp circuit to generate a square waveform.
3. Generate sinusoidal wave form by designing wein bridge oscillator using 741 op-amp.
4. Generate sinusoidal wave form by designing RC Phase shift oscillator using 741 op-amp.
5. Generate a triangular wave form from square wave using 741 op-amps.
6. Generate a Saw tooth wave form from square wave using 741 op-amps.
7. Generate a Saw tooth wave form using 741 op-amps.
8. Design a single op-amp circuit to generate square, triangular and saw tooth wave forms.
9. Design a square wave and triangular wave from a single circuit
10. Design a square wave by using 555 IC

EXPERIMENT-5

MONOSTABLE AND ASTABLE MULTIVIBRATOR CIRCUITS

- AIM:** 1. To design a monostable multivibrator for a required pulse width using 555 timer.
2. To design astable multivibrator for a given frequency using 555 timer.

EQUIPMENT REQUIRED:

Bread board	1
CRO (20MHz)	1
IC 555	1
Resistors	
47K Ω	2
2.2K Ω	1
10K Ω	1
100K Ω	1
Capacitors	
0.01 μ F	2
0.1 μ F	2
PN Diode 1N4007	1
RPS	1
Function generator (10 Hz-20MHz)	1

Design:

Monostable Multivibrator:

$$T = 1.1R_1C_1$$

Let $C_1 = 0.01\mu\text{F}$ & $R_1 = 47\text{K}\Omega$ then $T = 0.3\text{ms}(\text{approx})$

Astable Multivibrator:

For 55% duty cycle choose $R_B = 10\text{K}\Omega$

$$T_{\text{HIGH}} = T_c = 0.693 (R_A + R_B)C$$

$$T_{\text{LOW}} = T_d = 0.693 R_B C$$

$$T = T_{\text{HIGH}} + T_{\text{LOW}} = 0.693 (R_A + 2R_B)C$$

$$f = 1/T = 1.44 / (R_A + 2R_B)C$$

$$\% \text{ duty cycle, } D = T_c / T * 100 = (R_A + R_B) / (R_A + 2R_B) * 100$$

 
Circuit diagrams:**Monostable Multivibrator:****Triggering Circuit**

Fig 1. Monostable Multivibrator

Astable Multivibrator:

 



Fig 2. Astable Multivibrator

Procedure:**Monostable Multivibrator:**


1. Connect the circuit as shown in the circuit diagram Fig 1.
2. Apply Negative triggering pulses of frequency 1 KHz at pin 2.
3. Observe the output waveform at pin 3 and measure capacitor voltage across it at pin 6.
4. Theoretically calculate the pulse duration as $T = 1.1R_1C_1$
5. Compare it with experimental values.
6. Plot the graph for the input and output waveforms.

Astable Multivibrator:

1. Connect the circuit as shown in the circuit diagram Fig 2.
2. Observe the output waveform at pin 3 and measure capacitor voltage across it at pin 6.
3. Theoretically calculate the Time period as $T = 0.69 R_B C + 0.69 (R_A + R_B) C$.
4. Compare it with experimental values.
5. Plot the graph for the input and output waveforms.

 Model Wave Forms:**Monostable Multivibrator:**

Waveforms at Capacitor and monostable output

 Astable Multivibrator:

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the diode connection between pin 2 and 8
- iii. Check the connections between pin no.1 and pin no.5
- iv. Check the continuity of the connecting wires.

INFERENCE:

- i. The working of 555 timer monostable multivibrator is observed and the output is plotted.
- ii. The time period of the output waveform is calculated.
- iii. Frequency of the output wave form is calculated.

Applications:

- i. To construct missing pulse detector circuit.
- ii. To construct linear ramp generator circuit.
- iii. To construct Frequency divider circuit.

RESULT: Designed and verified the waveforms of monostable multivibrator and Astable multivibrator using 555 Timer.

.

REVIEW QUESTIONS:

1. Define duty cycle?
2. Draw the pin diagram of 555 timers?
3. What are the applications of 555 timers in monostable mode?
4. Explain capacitor output waveform in monostable mode?
5. Write down the expression for output pulse width in monostable mode?
6. Why the number has come for 555 IC as 555?

7. Write down the expression for output pulse width in Astable mode?
8. What are the applications of 555 timers in Astable mode?
9. What is a quasi stable state and what is a steady state?.
10. What are the other names for the Monostable Multivibrator and Astable Multivibrator?

Exercise Problems:

1. Design a astable multivibrator using 555 IC.
2. Design a monostable multivibrator using 555 IC.
3. Generate a square wave with 60% duty cycle using 555 IC.
4. Generate a square wave with variable duty cycle between 30% to 70%.
5. Design a multivibrator circuit using 555 IC to make the ON time of a bulb is 2sec and OFF time is 1sec
6. Design a free running Oscillator using 555 IC.
7. Design a one shot multivibrator using 555 IC.
8. Design a multivibrator circuit using 555 IC to make the ON time of a bulb is 1sec and OFF time is 500msec.
9. Design a traffic signal controller with time delay of 30sec using 555IC.
10. Design a traffic signal Controller with time delay of 30sec and 45sec using 555 IC.

EXPERIMENT-6

SCMITT TRIGGER CIRCUITS-USING IC741

AIM: To Design a Schmitt trigger circuit using IC 741 and verify the output wave forms.

EQUIPMENT REQUIRED:

Bread board	1 No.
Regulated power supply	1 No.
Function generator	1 No.
CRO	1 No.
IC 741	1 No.
Resistors	
100K Ω	2 No.s
100 Ω	2 No.s
1K Ω	1 No.
10K Ω	1 No.
5.1K Ω	1 No.
Capacitor	
0.01 μ F	2 No.s

Design: To design a Schmitt trigger for a given value of $+V_{sat}$, $-V_{sat}$, UTP and LTP.

$$+V_{sat} = V_{cc} - 3V \text{ (approx)}$$

$$-V_{sat} = V_{ee} + 3V \text{ (approx)}$$

Select V_{cc} and V_{ee} as per the design requirements.

UTP and LTP depends on β i.e. $R_2 / (R_1 + R_2)$. Select the resistors as per the UTP and LTP requirements.

Design a Schmitt Trigger for $+V_{sat} = 9V$ and $-V_{sat} = -6V$ and UTP and LTP as 3V and –

2V. For this requirement, $V_{cc} = +12V$ and $V_{ee} = -9V$ and the $\beta = 1/3$ (R_1 can be selected

as 1K which gives R_2 as 2K)

Circuit diagrams:


 


Fig 1. Schmitt trigger using IC 741

 


Procedure:

Using IC 741:

1. Connect the circuit as shown in fig 1(a) as Schmitt trigger using IC 741.
2. Give a 5 V_{p-p} sine wave of 1 kHz as input.
3. Observe the wave form on CRO and measure UTP and LTP, V_{sat} and - V_{sat}.
4. Use X-Y mode in CRO and observe hysteresis curve.

5. Repeat the above experiment for $R_1 = 5.1\text{Kohms}$ and 15 Kohms and observe the effect.

Expected waveforms:

 

(a) Input wave form (b) output wave form

Observations:

Parameter	Input	Output
Voltage(V_{p-p}), V		
Time period - Positive Half cycle(ms)		
Time period - Negative Half cycle(ms)		

	Theoretical	Observed
UTP		
LTP		

PRECAUTIONS:

- Check the circuit connections before switching on the power supply.
- Pin No.1 and Pin No.8 should be left free.
- Check the continuity of the connecting wires.

INFERENCE:

- i. The working of Schmitt Trigger is observed and the output is plotted.
- ii. The upper and lower Threshold voltages are measured.

Applications:

- i. This can be used as frequency divider, pulse width modulator, burglar alarm, FSK generator, ramp generator, pulse position modulator, waveform generator, etc.
- ii. This can be used as square wave converter.

Result: Designed and verified Schmitt trigger circuit using IC 741.

VIVA Questions:

1. What are the circuits used to generate square wave?
2. Short notes on zero crossing detector?
3. Define hysteresis width?
4. What are the other names for Schmitt Trigger?
5. What is the duty cycle of the output square wave of the Schmitt Trigger?
6. What is a Schmitt Trigger?
7. For what requirements, Schmitt Trigger is used?
8. define utp and ltp. what are the values of utp and ltp for the above circuit?
9. what is the basic difference between the comparator and schmitt trigger?
10. which type of feedback is used in schmitt trigger?

Viva Questions:

1. Schmitt trigger is also known as?
2. What is the disadvantage of comparator and how it is overcome?
3. Define hysteresis.
4. What are the Applications of schmitt trigger?
5. Define UTP.
6. Define LTP.

7. Which type of feedback is used in Schmitt trigger?
8. What is the other name of hysteresis?
9. Write the formula for hysteresis
10. Draw the schematic diagram of 555 as Schmitt trigger.

Exercise Problems:

1. Design single supply Schmitt trigger circuit.
2. Design Schmitt trigger with $V_{CC}=5V$, $V_{Low}=0V$, $V_{High}=5V$, $V_{TL}=3.5V$, $V_{Th}=5V$.
3. Design Schmitt trigger with $V_{TL}=2V$, $V_{Th}=5V$.
4. In Schmitt trigger circuit if V_{in} exceeds V_{sat} what will happen.
5. In Schmitt trigger when $V_{in} > V_{sat}$ output is distorted or not if distorted why?
6. Design Schmitt trigger with $V_{CC}=5V$, $V_{Low}=0V$, $V_{High}=5V$, $V_{TL}=2.25V$, $V_{Th}=5V$.
7. Design Schmitt trigger with $V_{TL}=1.5v$, $V_{Th}=4V$.
8. Design Schmitt trigger with $V_{CC}=5V$, $V_{Low}=0v$, $V_{High}=6v$, $V_{th}=6V$.

EXPERIMENT-7

IC 565 – PLL APPLICATIONS

AIM:

To study the operation of NE565 PLL – with a given free running frequency.

EQUIPMENT REQUIRED:


- DC power supply
- CRO
- Bread Board
- Function Generator
- Resistors 2.2k Ω , 10K Ω , 18K Ω – 1No. each
- Capacitor 10 μ F – 1No
- Capacitor 0.001 μ F – 2Nos
- IC565 - 1No.

THEORY:


The 565 IC is available as a 14-pin DIP package. The output frequency of the V_{CO} is $f_o = 1.2 / 4 R_T C_T$, where R_T and C_T are the external Resistor and Capacitor connected to pin 8 and pin 9. A value between 2k and 20k is recommended for R_T . The V_{CO} free running frequency is adjusted with R_T and C_T , so that it is at the centre of the input frequency range.

$$f_o \simeq \frac{1.2}{4R_1C_1}$$

Circuit diagram:

 



PLL Block Diagram

 **Procedure:**

1. Connect the circuit as shown in the figure.
2. Measure the free running frequency of V_{CO} at pin 4 with the input signal $V_{in} =$ zero. Compare it with the calculated value $= 1.2/4R_T C_T$
3. Now apply the input signal of $1V_{pp}$ square wave of 100Hz to pin 2. Connect channel 1 of the CRO to pin 2 and display this signal on the scope.
4. Gradually increase the input frequency till the PLL is locked to the input frequency.
5. This frequency f_{CL} gives the lower end of the capture range.
6. Go on increase the input frequency, till PLL stops tracking the input signal. This frequency f_{LH} gives the upper end of the lock range.
7. If the input frequency is increased further the loop will be in unlocked condition only.
8. Now gradually decrease the input frequency till the PLL is again get locked. This is the frequency f_{CH} , the upper end of the capture range. Keep on decreasing the

input frequency until the loop is unlocked. This frequency f_{LL} gives the lower end of the lock range.

Expected Wave Forms:

  

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the connection between pin 7 and 8
- iii. Check the connections at the input.
- iv. Check the continuity of the connecting wires

INFERENCE:

- i. The working of 565 PLL is observed and the output is plotted.
- ii. The time period of the output waveform is calculated
- iii. Frequency of the output wave form is calculated
- iv. The Lock range and Capture range of the PLL are calculated.

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the connection between pin 7 and 8
- iii. Check the connections at the input.
- iv. Check the continuity of the connecting wires.

Applications:

- i. To construct missing frequency multiplier circuit
- ii. To construct AM demodulator circuit
- iii. To construct FSK demodulator circuit

RESULT:

- f_O Free running frequency: _____
- f_{LL} Lower Locking frequency: _____
- f_{CL} Lower capture frequency: _____
- f_{CH} Higher capture frequency: _____
- f_{LH} Higher Locking frequency: _____

VIVA Questions:

1. What are the basic blocks of a PLL?
2. Define V_{CO} ?
3. What is the formula for the free running frequency F_o of 565 PLL?
4. What is PLL?
5. Define lock range?.
6. Define pull-in time?
7. Define capture range?
8. What is the function of the LPF in PLL?
9. What are the applications of PLL?
10. Which is greater – lock in range or capture range?

EXPERIMENT-8


VOLTAGE REGULATOR USING IC723

AIM: To study the voltage regulation characteristics and plot the response curve for line regulation and load regulation using 723 IC.

APPARATUS:

1. Bread board
2. IC LM723 - 1No.
3. Resistors(1K Ω , 2.7K Ω , 4.7K Ω , 6.8K Ω) - 1No. each
4. RPS
5. DRB / Potentiometer 10K - 1No.
6. Capacitors 100pF - 1No.
7. Connecting wires
8. Ammeter 0-20 mA - 1No.
9. Voltmeter 0-20V - 1No.

Circuit Diagrams:

 

a. To get output voltage > 7V

 


Fig1: Voltage Regulator

b. To get output voltage < 7V

PROCEDURE:

I. LINE REGULATION

1. Connections are made as per the circuit diagram.
2. RPS is connected as V_i .
3. A fixed load of 1K is kept at the output.
4. Input V_i is varied from 15V to 25V in steps of 2V and Output voltage is measured.
5. Graph is drawn between the input voltage and output voltage.

II. LOAD REGULATION

1. Connections are made as per the circuit diagram.
2. RPS is connected as V_i .
3. Output voltage is measured by varying the load (Potentiometer), in steps of 1mA
4. Graph is drawn between the output voltage and output current (load).

Observations:

$$\text{Line regulation} = (\Delta V_{out} / \Delta V_{in}) / 100\%$$

$$V_{nl} =$$


Line Voltage (V)	Output Voltage (V)

Load regulation

Regulated Output (V)	Load Current(mA)	Load Resistance(K Ω)	Load Regulation

$$\text{Regulation} = [(V_{nl} - V_{fl}) / V_{fl}] * 100\%$$

Model Graph:

 

INFERENCE:

- i. The working of 723 regulator is observed and the output is plotted.
- ii. The load regulation is calculated.
- iii. The line regulation is calculated.

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the continuity of the connecting wires.

Result: The load regulations and line regulations are observed by the IC 723.

Experiment 8B

AIM: To study the voltage regulation characteristics and plot the response curve for line regulation and load regulation using 7805, 7809, 7912 ICs.

Apparatus:

1. Bread board
2. ICs 7805, 7809, 7912 ICs - 1No. each
3. RPS
4. DRB / potentiometer 10K Ω - 1No.
5. Capacitors 1000 μ F, 22 μ F - 1No. each
6. Voltmeter - 0-20V
7. Connecting wires

Circuit Diagrams:

 


Figure.1 Fixed Positive Voltage regulator

 


Figure.2 Fixed Negative Voltage Regulator

Theory: A regulated power supply has to provide constant output voltage irrespective of variation in the load connected to the power supply or variation in the input unregulated power given to the power supply. This is achieved by taking the feedback from the output voltage and compared with a fixed reference voltage. Based on the error, the output voltage is adjusted.

Procedure:

For fixed positive voltage regulator (7805 and 7809):

1. Connect the circuit diagram as shown in figure.1.
2. Apply the unregulated voltage to the IC 7805 and note down the regulator output voltage. Vary input voltage from 7V to 20V and record the output voltages.
3. Calculate the line regulation of the regulator using the formula.
4. $\text{Line Regulation} = \Delta V_O / \Delta V_i$.
5. Now, fix the input voltage as 15V and vary the load resistance R_L , from 1K to 10 K ohms. Note down the regulator output voltage.
6. Calculate the Load regulation of the regulator using the formula.
7. $\text{Load Regulation} = \Delta V_O / \Delta I_L$.
8. Repeat the above procedure for 7809.

For fixed negative voltage regulator (7912):

1. Connect the circuit diagram as shown in figure.2.
2. Apply the unregulated voltage to the IC 7912 and note down the regulator output voltage.
3. Vary input voltage from 7V to 20V and record the output voltages.
4. Calculate the line regulation of the regulator using the formula.
5. $\text{Line Regulation} = \Delta V_O / \Delta V_i$.
6. Now, fix the input voltage as 15V and vary the load resistance R_L , from 1K to 10 K ohms. Note down the regulator output voltage.
7. Calculate the Load regulation of the regulator using the formula.
8. $\text{Load Regulation} = \Delta V_O / \Delta I_L$.

Observations:

1). For +Ve Voltage Regulator 7805

Line Regulation: (R_L is constant)

S.No.	Unregulated DC Input, V_i in Volts	Regulated DC Output, V_o in Volts

Load Regulation: (V_i is constant)

S.No.	Load Resistance, R_L in Ohms	Regulated DC output, V_o in Volts

2). For +Ve Voltage Regulator 7809

Line Regulation: (R_L is constant)

S.No.	Unregulated DC Input, V_i in Volts	Regulated DC Output, V_o in Volts

Load Regulation: (V_i is constant)

S.No.	Load Resistance, R_L in Ohms	Regulated DC output, V_O in Volts

3). For -Ve Voltage Regulator 7912

Line Regulation: (R_L is constant)

S.No.	Unregulated DC Input, V_i in Volts	Regulated DC Output, V_O in Volts

Load Regulation: (V_i is constant)

S.No.	Load Resistance, R_L in Ohms	Regulated DC output, V_O in Volts

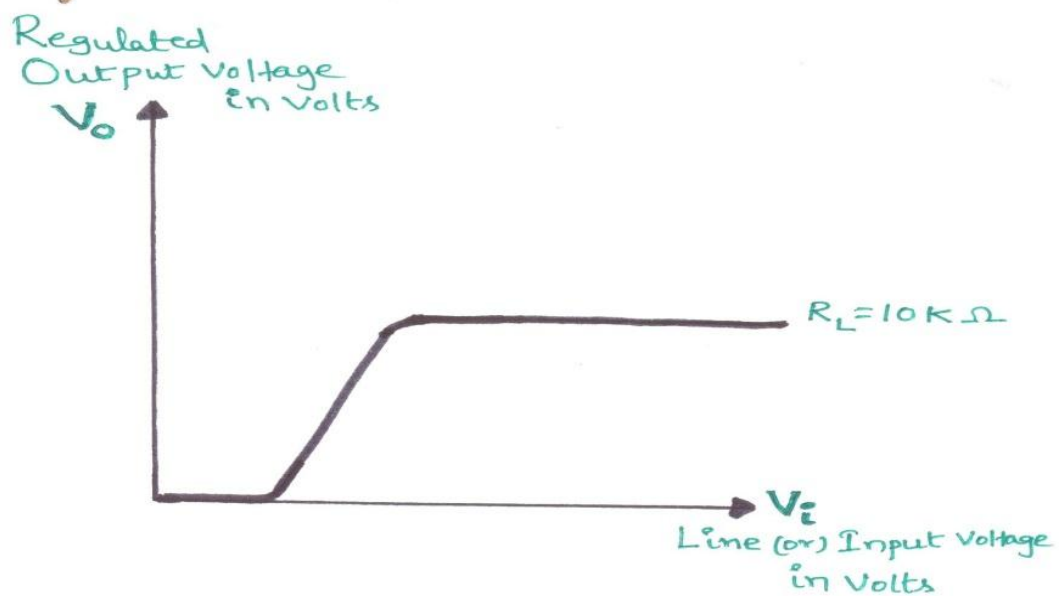
Model Graphs(for +Ve Voltage Regulators):

Fig 3. Line Regulation

 


Fig 4. Load Regulation

Model Graphs(for -Ve Voltage Regulator):

 


Figure 5. Line Regulation for 79XX

 


Figure 6. Load Regulation for 79XX

PRECAUTIONS:

- i. Check the circuit connections before switching on the power supply.
- ii. Check the continuity of the connecting wires.

INFERENCE:

- i. The working of 78XX regulator is observed and the output is plotted.
- ii. The load regulation is calculated.
- iii. The line regulation is calculated.

Applications:

- i. Used as an fixed voltage regulator.
- ii. Used as an current source.

Result:

Studied the 3-terminal fixed voltage regulator using IC 78XX and 79XX series &also the line regulation and load regulation of them are verified.

VIVA Questions:

1. What is meant by line regulation?
2. What is meant by load regulation?
3. What is the function of a series pass transistor in Linear regulated power supply?
4. What is a voltage regulator?
5. What are the advantages of IC voltage regulators?
6. What is meant by current limiting?
7. Give the drawbacks of linear regulators.
8. What is thermal shut down?
9. What are the limitations of 3 pin fixed voltage regulators?
10. How current boosting is achieved in 723 IC?

Part-II**LIST OF EXPERIMENTS**

1. HDL code to realize all the logic gates
 - 1.1. Logic Gates (Data Flow Model)
 - 1.2. Logic Gates (Behavioral Model)
 - 1.3. Nand Logic Gate (Structural Model)
 - 1.4. Nor Logic Gate (Structural Model)
 - 1.5. XNor Logic Gate (Structural Model)
2. Design of 2-to-4 decoder
3. Design of 8-to-3 encoder
 - 3.1. Without parity
 - 3.2. With parity
4. Design of 8-to-1 multiplexer
5. Design of 4 bit binary to gray converter
6. Design of 4-bit Comparator
7. Design of full adder using 3 modeling styles
 - 7.1. Full adder (dataflow Model)
 - 7.2. Full adder (Behavioral Model)
 - 7.3. Full adder (Behavioral Model with Select)
 - 7.4. Full adder (Structural Model)
8. Design of flip flops: SR,D,JK,T
 - 8.1. SR flip flop
 - 8.2. D flip flop
 - 8.3. JK flip flop
 - 8.4. T flip flop
9. Design of 4-bit binary, BCD counters (synchronous/ asynchronous reset)
 - 9.1. 4-bit synchronous counter
 - 9.2. 4-bit asynchronous counter
 - 9.3. BCD up counter
 - 9.4. BCD down counter
10. Finite state machine design

1.1 Logic Gates (Data Flow Model)

Aim: To design all types the logic gates using HDL Programming and verify their simulation and synthesis reports.

Apparatus:

Personal Computer: 1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Theory:

A logic gate performs a logical operation on one or more logic inputs and produces a single logic output. The logic is normally performed as Boolean logic and is most commonly found in digital circuits.


The different types of logic gates are:

i. AND gate

 


The AND gate is an electronic circuit that gives a high output (1) only if all its inputs are high. A dot (.) is used to show the AND operation i.e. A.B. Bear in mind that this dot is sometimes omitted i.e. AB

ii. OR gate

 


The OR gate is an electronic circuit that gives a high output (1) if one or more of its inputs are high. A plus (+) is used to show the OR operation.

iii. NOT gate

 

NOT gate	
A	$\bar{A}$
0	1
1	0

The NOT gate is an electronic circuit that produces an inverted version of the input at its output. It is also known as an inverter. If the input variable is A, the inverted output is known as NOT A. This is also shown as A', or A with a bar over the top, as shown at the outputs. The diagrams below show two ways that the NAND logic gate can be configured to produce a NOT gate. It can also be done using NOR logic gates in the same way.

 

iv. NAND gate




2 Input NAND gate		
A	B	$\bar{A}\bar{B}$
0	0	1
0	1	1
1	0	1
1	1	0

This is a NOT-AND gate which is equal to an AND gate followed by a NOT gate.

The outputs of all NAND gates are high if any of the inputs are low. The symbol is an AND gate with a small circle on the output. The small circle represents inversion.

v. NOR gate

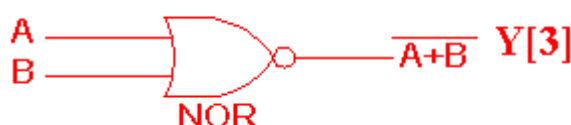

2 Input NOR gate		
A	B	$\bar{A} + \bar{B}$
0	0	1
0	1	0
1	0	0
1	1	0

This is a NOT-OR gate which is equal to an OR gate followed by a NOT gate. The outputs of all NOR gates are low if any of the inputs are high.

The symbol is an OR gate with a small circle on the output. The small circle represents inversion.

vi. EXOR gate



2 Input EXOR gate		
A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

The 'Exclusive-OR' gate is a circuit which will give a high output if either, but not both, of its two inputs are high. An encircled plus sign ($\oplus$) is used to show the EOR operation.


vii. EXNOR gate



2 Input EXNOR gate		
A	B	$\overline{A \oplus B}$
0	0	1
0	1	0
1	0	0
1	1	1

The 'Exclusive-NOR' gate circuit does the opposite to the EOR gate. It will give a low output if either, but not both, of its two inputs are high. The symbol is an EXOR gate with a small circle on the output. The small circle represents inversion.

Block Diagram:

 

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
```

```

use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity allall is
  Port ( a : in  STD_LOGIC;
        b : in  STD_LOGIC;
        c : out STD_LOGIC;
        d : out STD_LOGIC;
        e : out STD_LOGIC;
        f : out STD_LOGIC;
        g : out STD_LOGIC;
        h : out STD_LOGIC;
        i : out STD_LOGIC);

```


```
end allall;
```

```

architecture dataflow of allall is
begin
  c<= a and b;
  d<= a or b;
  e<= not a;
  f<= a nand b;
  g<= a nor b;
  h<= a xor b;
  i<= a xnor b;
end dataflow;

```

Simulation Waveform:

 

Synthesis Report:

```

=====
=====

```

* Final Report *

```

=====
=====

```

Cell Usage :


```

# BELS : 7
# AND2 : 1
# INV : 4
# OR2 : 1
# XOR2 : 1
# IO Buffers : 9

```

```
# IBUF : 2
# OBUF : 7
```

```
=====
=====
```

 RTL Schematic:

1.2 Logic Gates (Behavioral Model)

Aim: To simulate and verify the **All Logic Gates** with **Behavioral Model**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.1i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity allbeh is
    Port ( a : in  STD_LOGIC;
          b : in  STD_LOGIC;
          c,d,e,f,g,h,i : out  STD_LOGIC);
end allbeh;
architecture Behavioral of allbeh is
begin
    process (a,b)
    begin
        if a='1' and b='1' then c<='1';
        else c<='0';
        end if;
        if a='0' and b='0' then d<='0';
        else d<='1';
        end if;
        if a='1' and b='1' then e<='0';
        else e<='1';
        end if;
        if a='0' and b='0' then f<='1';
        else f<='0';
        end if;
        if a=b then g<='0';
        else g<='1';
        end if;
        if a=b then h<='1';
        else h<='0';
        end if;
        if a='0' then i<='1';
        else i<='0';
        end if;
    end process;
end Behavioral;
```

Simulation Waveform:

 


Synthesis Report:

```

=====
=====
*                               *
                               Final Report
=====
=====
Cell Usage :
# BELS                               : 9
# AND2                               : 2
# INV                                : 6
# XOR2                               : 1
# IO Buffers                         : 9
# IBUF                               : 2
# OBUF                               : 7
=====
=====

```

RTL Schematic:

 

1.3 Nand Logic Gate (Structural Model)

Aim: To simulate and verify the **Nand Gate** with **Structural Model**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.1i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity nandstruct is
  Port ( x : in STD_LOGIC;
        y : in STD_LOGIC;
        z : out STD_LOGIC);
end nandstruct;
```

```
architecture structural of nandstruct is
  component and12 is
    port(a,b:in std_logic;
         c:out std_logic);
  end component;
  component not12 is
    port(d:in std_logic;
         e:out std_logic);
  end component;
  signal w:std_logic;
begin
  a1:and12 port map(x,y,w);
  a2:not12 port map(w,z);
end structural;
```

-- program for and12

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity and12 is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end and12;
```

```
architecture dataflow of and12 is
begin
  c<=a and b;
end dataflow;
```

-- program for not12


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

entity not12 is
    Port ( d : in  STD_LOGIC;
          e : out STD_LOGIC);

```

```

end not12;

```

```

architecture dataflow of not12 is
begin
    e<= not d;
end dataflow;

```

Simulation Waveform:



Synthesis Report:

```

=====
=====

```

* Final Report *

```

=====
=====

```

Cell Usage :

```


# BELS : 3
# INV : 2
# OR2 : 1
# IO Buffers : 3
# IBUF : 2
# OBUF : 1

```

```

=====
=====

```

 RTL Schematic:

1.4 Nor Logic Gate (Structural Model)

Aim: To simulate and verify the **Nor Gate** with **Structural Model**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.1i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity norstruct is
Port ( x : in STD_LOGIC;
      y : in STD_LOGIC;
      z : out STD_LOGIC);
end norstruct;
```

```
architecture structural of norstruct is
component or12 is
port(a,b:in std_logic;
     c:out std_logic);
end component;
component not12 is
port(d:in std_logic;
     e:out std_logic);
end component;
```

```
signal w:std_logic;
begin
a1:or12 port map(x,y,w);
a2:not12 port map(w,z);
end structural;
```

-- program for or12

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity or12 is
Port ( a : in STD_LOGIC;
      b : in STD_LOGIC;
      c : out STD_LOGIC);
```

```
end or12;
```

```
architecture dataflow of or12 is
begin
c<=a or b;
end dataflow;
```

-- program for not12

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity not12 is
```

```
    Port ( d : in  STD_LOGIC;
          e : out STD_LOGIC);
```


```
end not12;
```

```
architecture dataflow of not12 is
```

```
begin
```

```
e<= not d;
```

```
end dataflow;
```

 Simulation Waveform:**Synthesis Report:**

```
=====
=====
```

```
          *                      Final Report                      *
```



```
=====
=====
```

Cell Usage :

```
# BELS                      : 3
# AND2                      : 1
# INV                      : 2
# IO Buffers                : 3
# IBUF                      : 2
# OBUF                      : 1
```

```
=====
=====
```

RTL Schematic:

  

1.5 XNor Logic Gate (Structural Model)

Aim: To simulate and verify the XNor Gate with Structural Model

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.1i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity xnors is
  Port ( x : in STD_LOGIC;
        y : in STD_LOGIC;
        z : out STD_LOGIC);
end xnors;
```

```
architecture struct of xnors is
  component xor12 is
    port(a,b:in std_logic;
         c:out std_logic);
  end component;
```

```
  component not12 is
    port ( d : in STD_LOGIC;
           e : out STD_LOGIC);
  end component;
  signal w:std_logic;
begin
  a1:xor12 port map (x,y,w);
  a2:not12 port map (w,z);
end struct;
```

-- program for xor12

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity xor12 is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : out STD_LOGIC);
end xor12;
```

```
architecture dataflow of xor12 is
begin
  x<=p xor q;
end dataflow;
```

-- program for not12

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

```

```

entity not12 is

```

```

    Port ( d : in  STD_LOGIC;
          e : out STD_LOGIC);

```

```

end not12;

```

```

architecture dataflow of not12 is

```

```

begin

```

```


    e<= not d;

```

```

end dataflow;

```

 Simulation Waveform:**Synthesis Report:**

```

=====
*                               *
Final Report
=====
=====

```

Cell Usage :

```


# BELS                : 2
#   INV                : 1
#   XOR2               : 1
# IO Buffers           : 3
#   IBUF               : 2
#   OBUF               : 1


```

```

=====
=====

```

 RTL Schematic:

 

Result: Designed and verified logic gates using HDL.

Viva Questions

1. How many N AND gates are required to design XOR logic?
2. How many NOR gates are required to design XOR logic?
3. How many N AND gates are required to design XNOR logic?
4. How many NOR gates are required to design XNOR logic?
5. Draw the circuit of AND gate using Transistors.
6. Draw the circuit of OR gate using Transistors.
7. Draw the circuit of NOT gate using Transistors.
8. Define Fan-in Fan Out.
9. Define Noise Margin.
10. Define Figure of merit.

EXERCISE PROBLEMS

1. To simulate and verify 3-input AND gate with dataflow model.
2. Write a VHDL code for 2-input NOR gate in structural model and verify it.
3. To simulate and verify 3-input OR gate with dataflow model.
4. Write a VHDL code for 3-input NAND gate in structural model and verify it.
5. To simulate and verify 2-input NAND gate with behavioral model.
6. To simulate and verify 2-input NOR gate with behavioral model.
7. Write VHDL code for 3-input NAND gate in dataflow model and verify it.
8. Write VHDL code for 3-input NOR gate in dataflow model and verify it.
9. To simulate and verify 3-input AND gate with behavioral model.
- 10 To simulate and verify 3-input OR gate with behavioral model.
- 11 Write a VHDL code for 3-input NAND gate in behavioral model and verify it.
- 12 To simulate and verify 2input NAND gate with data flow model
- 13 Write a VHDL code for 2-input NAND gate in Structural model and verify it.
- 14 To simulate and verify 2input NOR gate with data flow model
- 15 Write a VHDL code for 3-input NOR gate in behavioral model and verify it
- 16 Write a VHDL code for 2-input XOR gate in data flow model and verify it
- 17 Write a VHDL code for 2-input XOR gate in behavioral model and verify it
- 18 Write a VHDL code for 2-input XNOR gate in data flow model and verify it
- 19 Write a VHDL code for 2-input XNOR gate in behavioral model and verify it
- 20 Write a VHDL code for 2-input XNOR gate in Structural model and verify it

2. Design of 2-to-4 decoder

Aim: To design 2 to 4 line decoder using HDL, obtain the simulation and synthesis.

Apparatus:

Personal Computer: 1 No.

Operating System : Windows XP.

Software : Xilinx 9.2i.

Theory:

Decoders are circuits with two or more inputs and 2^n outputs. Based on the input code, only one of the output is selected.

The truth table of 2-to-4 line decoder is

E_n	INPUTS		OUTPUTS			
	D_{in1}	D_{in0}	D_{03}	D_{02}	D_{01}	D_{00}
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Developed into a circuit it looks like

 
 
 


Figure: Gate Level Representation of 2 to 4 Line Decoder (Logic Diagram)

Block Diagram:**Program:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```


```
entity dec24 is
port(a,b,e:in std_logic;
      z:out std_logic_vector(0 to 3));
end dec24;
architecture data of dec24 is
begin
z(0)<= (not a) and (not b) and e;
z(1)<= b and (not a) and e;
z(2)<= a and (not b) and e;
z(3)<= a and b and e;
end data;
```

Simulation Waveform:**Synthesis Report:**

```

=====
*                               *
                               Final Report                               *
=====
=====
Cell Usage :
# BELS                               : 10
# AND2                               : 4
# AND3                               : 2
# INV                                : 4
# IO Buffers                         : 7
# IBUF                              : 3
# OBUF                              : 4
=====
=====

```

 RTL Schematic:

Result: Designed 2x4 decoder and verified by synthesizing and simulating the code.

Viva Questions

1. Define Decoder ?
2. What are the applications of decoder?
3. What is the difference between decoder and encoder?
4. What is the difference between encoder and priority encoder ?
5. How many 2 to 4 decoders are required to construct 4 to 16 decoder ?
6. What is the IC no of dual 2 to 4 decoder ?
7. What is the IC no of 3 to 8 decoder ?
8. What are the advantages of decoder ?
9. What is the IC no of dual 2 to 4 decoder ?
10. What is the IC no of 3 to 8 decoder ?

EXERCISE PROBLEMS

1. Design 4 to 16 decoder using 2 to 4 decoder
2. Write VHDL code for 2 to 4 decoder in structural model and verify it.
3. To simulate and verify the 3 to 8 line decoder with dataflow model.
4. To simulate and verify the 4 to 16 line decoder with dataflow model.
5. Write a VHDL code for 3 to 8 line decoder in behavioral model and verify it.
6. Write a VHDL code for 3 to 8 line decoder in data flow model and verify it.
7. Write a VHDL code for 2 to 4 line decoder in behavioral model and verify it.
8. Write a VHDL code for 2 to 4 line decoder in data flow model and verify it.
9. Write a VHDL code for 4 to 16 line decoder in data flow model and verify it.
10. Write a VHDL code for 4 to 16 line decoder in behavioral model and verify it.
11. Write a VHDL code for 4 to 16 line decoder in structural model and verify it.
12. Write a VHDL code for 5 to 32 line decoder in data flow model and verify it.
13. Write a VHDL code for 5 to 32 line decoder in behavioral model and verify it.
14. Write a VHDL code for 5 to 32 line decoder in structural model and verify it.
15. Design 5 to 32 decoder using 2 to 4 decoder

3.1 Design of 8-to-3 Encoder (Without Priority)

Aim: To Design and verify the functionality of 8 to 3 Encoder.

Apparatus:

Personal Computer: 1 No

Operating System : Windows XP,

Software : Xilinx 9.2i.

Theory:

An Encoder is a device, circuit, transducer, software program, algorithm or person that converts information from one format or code to another. The purpose of encoder is standardization, speed, secrecy, security, or saving space by shrinking size.

Encoders are combinational logic circuits and they are exactly opposite of decoders.

They accept one or more inputs and generate a multibit output code.

Encoders perform exactly reverse operation than Decoder. An Encoder has M input and N output lines. Out of M input lines only one is activated at a time and produces equivalent code on output N lines. If a device output code has fewer bits than the input code has, the device is usually called an encoder.

Octal to binary encoder

Octal-to-Binary take 8 inputs and provides 3 outputs, thus doing the opposite of what the 3-to-8 decoder does. At any one time, only one input line has a value of 1. The figure below shows the truth table of an Octal-to-binary encoder.

Inputs								Outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	E ₂	E ₁	E ₀
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Table: Truth Table of octal to binary encoder

For an 8-to-3 binary encoder with inputs I0-I7 the logic expressions of the outputs Y0-Y2 are:

$$E0 = I1 + I3 + I5 + I7$$

$$E1 = I2 + I3 + I6 + I7$$

$$E2 = I4 + I5 + I6 + I7$$


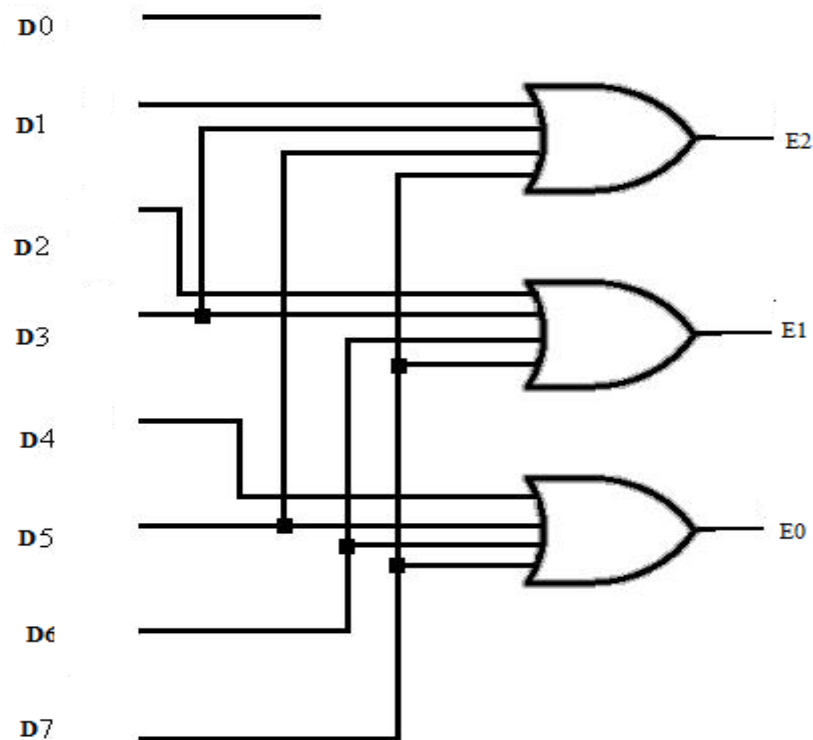


Fig. Logic Diagram of octal to binary encoder


Block Diagram:

 

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
--without Priority
entity encode83 is
port(e:in std_logic;
     d_in:in std_logic_vector(7 downto 0);
     d_out:out std_logic_vector(2 downto 0));
end encode83;

architecture beh of encode83 is
begin
process(e,d_in)
begin
if(e='1')then
d_out<="000";
else
case d_in is
when "00000001" => d_out <= "000";
when "00000010" => d_out <= "001";
when "00000100" => d_out <= "010";
when "00001000" => d_out <= "011";
when "00010000" => d_out <= "100";
when "00100000" => d_out <= "101";
when "01000000" => d_out <= "110";
when "10000000" => d_out <= "111";
when others => null;
end case;
end if;
end process;
end beh;
```

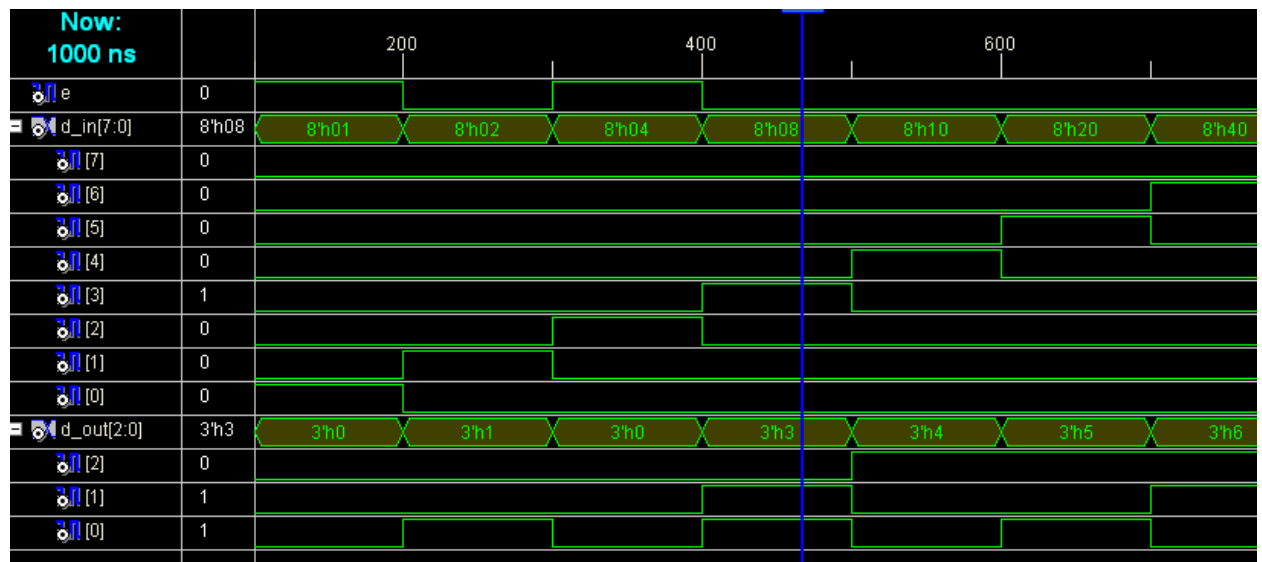
Simulation Waveform:**Synthesis Report:**

```
=====
=====
*                               *
Final Report
=====
=====
```

Cell Usage :

```
# BELS : 87
# AND2 : 13
# AND3 : 15
# INV : 43
# OR2 : 5
# OR3 : 1
# XOR2 : 10
# FlipFlops/Latches : 3
# LD : 3
# IO Buffers : 12
# IBUF : 9
# OBUF : 3
```

```
=====
=====
```

 RTL Schematic:

3.2 Design of 8-to-3 Encoder (With Priority)

Aim: To Design and verify the functionality of 8 to 3 priority Encoder.

Apparatus:

Personal Computer:1 No

Operating System : Windows XP.

Software : Xilinx 9.2i.

Program:


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

--with priority:

```
entity encode83wp is
port(e:in std_logic;
     d_in:in std_logic_vector(7 downto 0);
     d_out:out std_logic_vector(2 downto 0));
end encode83wp;
```

architecture beh of encode83wp is

```
begin
process(e,d_in)
begin
if(e='1')then
d_out<="000";
else
case d_in is
when "00000111" => d_out <= "000";
when "00000110" => d_out <= "001";
when "00000101" => d_out <= "010";
when "00000100" => d_out <= "011";
when "00000011" => d_out <= "100";
when "00000010" => d_out <= "101";
when "00000001" => d_out <= "110";
when "00000000" => d_out <= "111";
when others => null;
end case;
end if;
end process;
end beh;
```

 Simulation Waveform:

Result: Designed and verified 8 to 3 priority encoder is by synthesizing and simulating the code.

Viva questions

1. Define encoder ?
2. Define priority encoder ?
3. Difference between encoder and priority encoder ?
4. What are the advantages of encoder ?
5. What are the applications of encoder ?
6. Explain the difference between encoder and decoder ?
7. How many 4 to 2 encoders are required to construct 8 to 3 encoder ?
8. Draw the logic diagram of 4 to 2 encoder ?
9. Draw the logic diagram of 8 to 3 encoder ?
10. What is the IC no of 8 to 3 encoder ?

EXERCISE PROBLEMS

1. To simulate and verify the 4 to 2 encoder (without priority) with dataflow model.
2. To simulate and verify the 8 to 3 encoder (without priority) with dataflow model.
3. Write a VHDL code for 4 to 2 encoder (without priority) with behavioral model.
4. To simulate and verify the decimal to BCD encoder (without priority) with dataflow model.
5. To simulate and verify the decimal to BCD encoder (without priority) with behavioral model.
6. To simulate and verify the octal to binary encoder (without priority) with dataflow model.
7. To simulate and verify the octal to binary encoder (without priority) with behavioral model.
8. Write a VHDL code for 4 to 2 encoder (with priority) with dataflow model.
9. Write a VHDL code for 4 to 2 encoder (with priority) with behavioral model.
10. To simulate and verify the 8 to 3 encoder (with priority) with dataflow model.
11. To simulate and verify the 4 to 2 encoder (with priority) with structural model
12. To simulate and verify the 4 to 2 encoder (with out priority) with structural model
13. To simulate and verify the 8 to 3 encoder (with out priority) with behavioral model
14. To simulate and verify the 8 to 3 encoder (with out priority) with data flow model
15. To simulate and verify the 8 to 3 encoder (with out priority) with structural model.
16. To simulate and verify the 8 to 3 encoder (with priority) with behavioral model
17. To simulate and verify the 8 to 3 encoder (with priority) with data flow model
18. To simulate and verify the 8 to 3 encoder (with priority) with structural model
19. To simulate and verify the 16 to 4 encoder (with priority) with behavioral model
20. To simulate and verify the 16 to 4 encoder (without priority) with behavioral model

4. Design of 8-to-1 Multiplexer

Aim: To simulate and verify the **8 to 1 Multiplexer** with **Behavioral Model**

Apparatus:

Personal Computer:1 No


Operating System : Windows XP,

Software : Xilinx 9.2i.

Program:

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;


entity mux_81 is
    port (en: in std_logic;
          a: in std_logic_vector (2 downto 0);
          xin: in std_logic_vector (7 downto 0);
          xout1: out std_logic;
          xout2: out std_logic);
end mux_81;
architecture behavioral of mux_81 is
    begin
        process(en, a, xin)
        begin
            if (en = '0') then
                xout1 <= '0'; xout2 <= '1';
            else
                case a is
                    when "000" => xout1 <= xin (0); xout2 <= not xin(0);
                    when "001" => xout1 <= xin (1); xout2 <= not xin(1);
                    when "010" => xout1 <= xin (2); xout2 <= not xin(2);
                    when "011" => xout1 <= xin (3); xout2 <= not xin(3);
                    when "100" => xout1 <= xin (4); xout2 <= not xin(4);
                    when "101" => xout1 <= xin (5); xout2 <= not xin(5);
                    when "110" => xout1 <= xin (6); xout2 <= not xin(6);
                    when "111" => xout1 <= xin (7); xout2 <= not xin(7);
                    when others => null;
                end case;
            end if;
        end process;
    end behavioral;
```

 
Simulation Waveform:**Synthesis Report:**

```

=====
=====
*                               *
                        Final Report
*                               *
=====
=====
Cell Usage :
# BELS                               : 47
# AND2                               : 18
# INV                                : 15
# OR2                                : 14
# IO Buffers                          : 14
# IBUF                               : 12
# OBUF                               : 2
=====
=====

```

 RTL Schematic:

Result: Designed and Verified 8 to 1 Multiplexer.

Viva questions

1. Define multiplexer ?
2. Define demultiplexer ?
3. Explain the difference between multiplexer and demultiplexer ?
4. Explain the applications of multiplexers ?
5. Explain the applications of demultiplexers ?
6. How many 4: 1 multiplexers are required to design one 8:1 multiplexer ?
7. What is the use of selection lines in MUX?
8. what are the other names of multiplexers ?
9. What is the difference between MUX and decoder ?
10. why multiplexer is called as data selector ?

EXERCISE PROBLEMS

1. To simulate and verify the 4 to 1 MUX with dataflow model.
2. To simulate and verify the 4 to 1 MUX with behavioral model.
3. To simulate and verify the 8 to 1 MUX with dataflow model.
4. To simulate and verify the 8 to 1 MUX with behavioral model.
5. To simulate and verify the 16 to 1 MUX with dataflow model.
6. To simulate and verify the 16 to 1 MUX with behavioral model.
7. To simulate and verify the 4 to 1 MUX with structural model.
8. To simulate and verify the 8 to 1 MUX with structural model.
9. To simulate and verify the 2 to 1 MUX with structural model
10. To simulate and verify the 2 to 1 MUX with behavioral model
11. To simulate and verify the 2 to 1 MUX with data flow model
12. To simulate and verify the 16 to 1 MUX with structural model
13. To simulate and verify the 32 to 1 MUX with data flow model
14. To simulate and verify the 32 to 1 MUX with behavioral model
15. To simulate and verify the 32 to 1 MUX with Structural model
16. To simulate and verify the 64 to 1 MUX with data flow model
17. To simulate and verify the 64 to 1 MUX with behavioral model
18. To simulate and verify the 64 to 1 MUX with Structural model

5. Design of 4 bit binary to gray converter

Aim: To simulate and verify the 4 bit binary to gray converter

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity bi_to_g is
port(b:in std_logic_vector(3 downto 0);
     g:out std_logic_vector(3 downto 0));
end bi_to_g;
```


```
architecture df of bi_to_g is
begin
g(3)<=b(3);
g(2)<=b(3) xor b(2);
g(1)<=b(2) xor b(1);
g(0)<=b(1) xor b(0);
end df;
```

 Simulation Waveform:**Synthesis Report:**

```

=====
*                               *
Final Report
*                               *
=====
=====
Cell Usage :
# BELS                : 3
# XOR2                : 3
# IO Buffers          : 8
# IBUF                : 4
# OBUF                : 4
=====
=====

```

 RTL Schematic:

Viva questions

1. What is the difference between binary and BCD code ?
2. Convert 1010 into gray code ?
3. Convert the gray code 1010011 into binary code ?
4. Convert 101010 binary code into bcd code ?
5. Convert 10100101 bcd code into binary code ?
6. Convert 8547.A5D into decimal code?
7. Convert 58A.52 into octal code?
8. Convert 854.124 into hexa decimal code?
9. Define ASCII.
10. Define EBCDIC.

EXERCISE PROBLEMS

1. To simulate and verify the 4-bit gray to binary code converter.
2. To simulate and verify the 3-bit binary to BCD code converter.
3. To simulate and verify the 3-bit binary to gray code converter.
4. To simulate and verify the 4-bit gray to binary code converter.
5. To simulate and verify the 4-bit BCD to binary code converter using data flow model
6. To simulate and verify the 4-bit BCD to binary code converter using behavioural model
7. To simulate and verify the 3-bit BCD to Excess-3 code converter using behavioural model
8. To simulate and verify the 3-bit BCD to Excess-3 code converter using data flow model
9. To simulate and verify the 3-bit Excess-3 to BCD code converter using behavioural model
10. To simulate and verify the 3-bit Excess-3 to BCD code converter using data flow model
11. To simulate and verify the 3-bit binary to Excess-3 code converter
12. To simulate and verify the 4-bit binary to Excess-3 code converter
13. To simulate and verify the 3-bit BCD to Excess-3 code converter
14. To simulate and verify the 4-bit BCD to Excess-3 code converter
15. To simulate and verify the 3-bit Gray code to Excess-3 code converter
16. To simulate and verify the 3-bit Gray code to BCD code converter
17. To simulate and verify the 4-bit Gray code to Excess-3 code converter
18. To simulate and verify the 4-bit Gray code to BCD code converter
19. To simulate and verify the 2-bit Gray code to Excess-3 code converter
20. To simulate and verify the 2-bit Gray code to BCD code converter

6 Design of 4 bit Comparator

Aim: To simulate and verify the **Comparator**.

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity comparator4 is
  Port ( a,b : in  STD_LOGIC_vector(3 downto 0);
        x,y,z: out STD_LOGIC
        );
end comparator4;

architecture Behavioral of comparator4 is
begin
  process(a,b)
  begin
    if (a>b) then x<='1';else x<='0';
    end if;
    if (a<b) then y<='1'; else y<='0';
    end if;
    if (a=b) then z<='1'; else  z<='0';
    end if;
  end process;
end Behavioral;
```

 
Simulation Waveform:**Synthesis Report:**

```

=====
=====
*                               *
Final Report
=====
=====


```

Cell Usage :

```

# BELS                               : 51
# AND2                               : 8
# AND3                               : 4
# AND4                               : 1
# INV                                : 20
# OR2                                : 14
# XOR2                               : 4
# IO Buffers                         : 11
# IBUF                              : 8
# OBUF                              : 3

```

 RTL Schematic:

Viva Questions

1. Which IC is used as magnitude comparator?
2. What is the drawback of comparator?
3. What is false triggering?
4. What is zero crossing detector?
5. What are the applications of comparator?
6. What are applications of Schmitt trigger?
7. Define UTP.
8. Define LTP.
9. What is hysteresis?
10. What is the other name of Hysteresis?

EXERCISE PROBLEMS

1. To simulate and verify the 1 to 4 DEMUX with behavioral model.
2. To simulate and verify the 1 to 4 DEMUX with dataflow model.
3. To simulate and verify the 1 to 8 DEMUX with behavioral model.
4. To simulate and verify the 1 to 8 DEMUX with dataflow model.
5. Implement full subtractor using 1 to 8 DEMUX and verify it.
6. Implement full subtractor using 1 to 4 DEMUX and verify it.
7. To simulate and verify the 2-bit comparator with behavioral model.
8. To simulate and verify the 1 to 2 DEMUX with behavioral model
9. To simulate and verify the 1 to 2 DEMUX with data flow model
10. To simulate and verify the 1 to 2 DEMUX with structural model
11. To simulate and verify the 1 to 4 DEMUX with behavioral model
12. To simulate and verify the 1 to 4 DEMUX with data flow model
13. To simulate and verify the 1 to 4 DEMUX with structural model
14. To simulate and verify the 1 to 8 DEMUX with behavioral model
15. To simulate and verify the 1 to 8 DEMUX with data flow model
16. To simulate and verify the 1 to 8 DEMUX with structural model
17. Implement Half-Subtractor using 1 to 8 DEMUX and verify
18. Implement Half-Subtractor using 1 to 4 DEMUX and verify
19. To simulate and verify 2 bit comparator with data flow model
20. To simulate and verify 3 bit comparator with data flow model

7.1 Design of Full adder (data flow)

Aim: To simulate and verify the **full adder** with **Dataflow Model**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.2i.

Program:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity fa1 is

port(a,b,c:in std_logic;s,cout:out std_logic);

end fa1;

architecture df of fa1 is


begin

s<=a xor b xor c;

cout<=(a and b)or(a and c)or (b and c);

end df;

Simulation Waveform:

 

Synthesis Report:

=====

*

Final Report


*

=====
=====
Cell Usage:

# BELS	: 8
# AND2	: 3
# INV	: 1
# OR2	: 2
# XOR2	: 2
# IO Buffers	: 5
# IBUF	: 3
# OBUF	: 2

=====

=====
RTL Schematic:

 

7.2 Design of Full adder (Behavioral Model)

Aim: To simulate and verify the **full adder** with **Behavioral Model**

Apparatus:

Personal Computer:1 No


Operating System : Windows XP,

Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity fulladder1 is
port(a:in std_logic_vector(2 downto 0);
s,ca:out std_logic);
end fulladder1;
architecture behavioral of fulladder1 is
begin
process(a)
begin
if a="000" then s<='0';ca<='0';
elsif a="001" then s<='1';ca<='0';
elsif a="010" then s<='1';ca<='0';
elsif a="011" then s<='0';ca<='1';
elsif a="100" then s<='1';ca<='0';
elsif a="101" then s<='0';ca<='1';
elsif a="110" then s<='0';ca<='1';
else s<='1';ca<='1';
end if;
end process;
end behavioral;
```

 Simulation Waveform:**Synthesis Report:**

```

=====
*                               *
Final Report
=====
=====


```

Cell Usage:

```

# BELS : 19
# AND2 : 8
# INV : 6
# OR2 : 5
# IO Buffers : 5
# IBUF : 3
# OBUF : 2

```

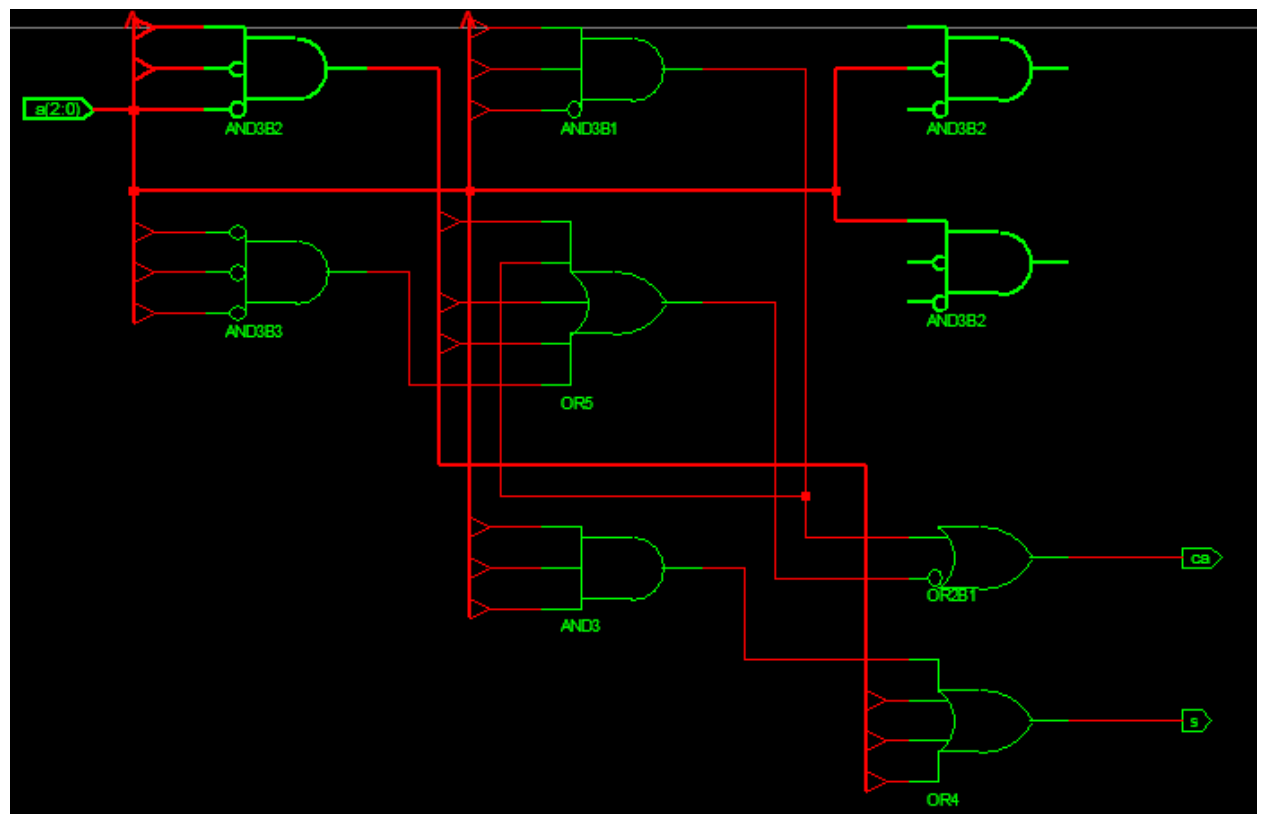RTL Schematic:

7.3 Design of Full adder (with select)

Aim: To simulate and verify the **full adder** with 'with select'

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity fa_select is
port(a:in bit_vector(2 downto 0);
     s:out bit_vector(1 downto 0));
end fa_select ;
```

```
architecture df of fa_select is
begin
with a select
s<=("00")when"000",
  ("10")when"001",
  ("10")when"010",
  ("01")when"011",
  ("10")when"100",
  ("01")when"101",
  ("01")when"110",
  ("11")when"111";
end df;
```

 
Simulation Waveform:**Synthesis Report:**

```

=====
=====
*                               *
                        Final Report
*                               *
=====
=====
Cell Usage:
# BELS                      : 19
# AND2                      : 8
# INV                      : 6
# OR2                      : 5
# IO Buffers                : 5
# IBUF                     : 3
# OBUF                     : 2
=====
=====

```


RTL Schematic:

 

7.4 Design of Full adder (Structural Model)

Aim: To simulate and verify the **full adder** with **Dataflow Model**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity fa2 is
port(a1,b1,c1:in std_logic;sum,cout1:out std_logic);
end fa2;

architecture struc of fa2 is
component xor12 is
port(p,q:in std_logic; x:out std_logic);
end component;
component and12 is
port(c,d:in std_logic;y:out std_logic);
end component;
component or12 is
port(e,f:in std_logic;z:out std_logic);
end component;
signal s1,s2,s3,s4,s5:std_logic;
begin
d1:xor12 port map(a1,b1,s1);
d2:xor12 port map(s1,c1,sum);
d3:and12 port map(a1,b1,s2);
d4:and12 port map(a1,c1,s3);
d5:and12 port map(b1,c1,s4);
d6:or12 port map(s2,s3,s5);
d7:or12 port map(s4,s5,cout1);
end struc;
```

Now: 1000 ns		200	400	600
a1	0			
b1	1			
c1	1			
sum	0			
cout1	1			

=====

=====

* Final Report *

=====

=====

```
# BELS                                : 6
#   AND2                              : 2
#   OR2                               : 2
#   XOR2                              : 2
# IO Buffers                          : 5
#   IBUF                              : 3
#   OBUF                              : 2
```

Viva Questions

1. What is the sum expression of full adder?
2. What is the carry expression of full adder?
3. What is the difference expression of full subtractor?
4. What is the borrow expression of full subtractor?
5. How many half adders are required to construct full adder?
6. How many half subtractors are required to construct full subtractor?
7. To implement 4 bit parallel adder how many full adders are required?
8. To implement 4 bit parallel adder how many full adders and half adders are required?
9. What is the drawback of serial adder?
10. What is the advantage of carry look ahead adder?

EXERCISE PROBLEMS

1. To simulate and verify the full adder by using two half adders.
2. Design 3-bit full adder of the inputs $a=0, b=0, c=1$ with dataflow model and verify it.
3. Design 3-bit full adder of the inputs $a=0, b=1, c=0$ with dataflow model and verify it.
4. Design 3-bit full adder of the inputs $a=0, b=1, c=1$ with dataflow model and verify it.
5. Design 3-bit full adder of the inputs $a=1, b=0, c=0$ with dataflow model and verify it.
6. Design 3-bit full adder of the inputs $a=1, b=0, c=1$ with dataflow model and verify it.
7. Design 3-bit full adder of the inputs $a=1, b=1, c=0$ with behavioral model and verify it.
8. Design 3-bit full adder of the inputs $a=1, b=1, c=1$ with behavioral model and verify it.
9. Design 3-bit full adder of the inputs $a=1, b=0, c=1$ with behavioral model and verify it.

10. Design 3-bit full adder of the inputs $a=1$, $b=1$, $c=0$ with dataflow model and verify it.
11. Design 3 bit full adder with the inputs $a=0$; $b=1$; $c=0$ with behavioral model and verify
12. Design 3 bit full adder with the inputs $a=0$; $b=1$; $c=1$ with behavioral model and verify
13. Design 3 bit full adder with the inputs $a=0$; $b=0$; $c=1$ with behavioral model and verify
14. Design 3 bit full adder with the inputs $a=1$; $b=1$; $c=0$ with behavioral model and verify
15. Design 3 bit full adder with the inputs $a=1$; $b=0$; $c=0$ with behavioral model and verify
16. Design 3 bit full adder with the inputs $a=1$; $b=0$; $c=1$ with behavioral model and verify
17. Design 3 bit full adder with the inputs $a=1$; $b=1$; $c=1$ with behavioral model and verify
18. Design 3 bit full adder with the inputs $a=0$; $b=1$; $c=1$ with behavioral model and verify
19. Design 3 bit full adder with the inputs $a=1$; $b=1$; $c=1$ with data flow model and verify
20. Design 3 bit full adder with the inputs $a=0$; $b=1$; $c=1$ with data flow model and verify

8.1 Design of SR Flip Flop

Aim: To simulate and verify the **SR flip flop** with Behavioral model

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity sr_ff is
port(s,r,clk,clr : in std_logic;
      q:inout std_logic:= '0';
      qbar : out std_logic);
end sr_ff;
```


```
architecture beh of sr_ff is
begin
  process(clk)
  begin
    if(clk'event and clk='1') then
      if(clr='1') then
        q<='0';qbar<='1';
      elsif(clr='0' and s='0' and r='0')then
        q<=q;qbar<=not q;
      elsif(s='0' and r='1')then
        q<='0';qbar<='1';
      elsif(s='1' and r='0')then
        q<='1';qbar<='0';
      else
        q<='Z';qbar<='Z';
      end if;
    end if;
  end process;
end beh;
```

 Simulation Waveform:**Synthesis Report:**

```
=====
=====
*                               *
Final Report
=====
=====
```

Cell Usage:

```
# BELS : 24
# AND2 : 8
# GND : 1
# INV : 11
# OR2 : 2
# OR3 : 2
# FlipFlops/Latches : 4
# FD : 2
# FDCE : 2
# IO Buffers : 6
# IBUF : 4
# IOBUFE : 1
# OBUFE : 1
```

 RTL Schematic:

8.2 Design of D Flip Flop

Aim: To simulate and verify the **D flip flop** with Behavioral model

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```


entity dff is

```
    Port ( d : in  STD_LOGIC;
          clk : in  STD_LOGIC;
          clr: in  STD_LOGIC;
          q : inout STD_LOGIC:= '0'
          qbar:out std_logic);
```

end dff;

architecture Behavioral of dff is


```
begin
process(clk,clr)
begin
if(clk'event and clk='1') then
if clr='1' then q<='0';
else q<=d; qbar<= not d;
end if;
end if;
end process;
end Behavioral;
```

 
Simulation Waveform:**Synthesis Report:**

```
=====
*                               *
Final Report
=====
```

Cell Usage:

```
# BELS                      : 4
# AND2                      : 1
# INV                       : 1
# OR2                       : 1
# FlipFlops/Latches        : 2
# FD                       : 2
# IO Buffers                : 5
# IBUF                     : 3
# OBUF                     : 2
```

 RTL Schematic:

8.3 Design of JK Flip Flop

Aim: To simulate and verify the **JK flip flop** with Behavioral model

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity jkff is
    Port ( jk : in  STD_LOGIC_VECTOR(1 downto 0);
          Clk,clr : in  STD_LOGIC;
          q : inout STD_LOGIC:= '0');
end jkff;

architecture Behavioral of jkff is
begin
    process(clk,jk)
    begin
        if(clk'event and clk='1') then
            if(clr='1')then q<='0';
            else
                case jk is
                    when "00"=>q<=q;
                    when "01"=>q<='0';
                    when "10"=>q<='1';
                    when "11"=>q<= not q;
                    when others=>null;
                end case;
            end if;
        end if;
    end process;
end Behavioral;
```

Current Simulation Time: 1000 ns

Signal	Value / State
jk[1:0]	2'h2, 2'h0, 2'h1, 2'h2, 2'h3, 2'h0, 2'h2
jk[1]	1, 0, 1, 0, 1, 0, 1
jk[0]	0, 1, 0, 1, 0, 1, 0
clk	Periodic clock signal
clr	Active-low pulse at 0
q	1, 0, 1, 0, 1, 0, 1
qbar	0, 1, 0, 1, 0, 1, 0

* Final Report *

```
# BELS                                     : 8
#   AND2                                  : 3
#   INV                                    : 3
#   OR2                                    : 1
#   VCC                                    : 1
# FlipFlops/Latches                       : 1
#   FD                                     : 1
# IO Buffers                              : 6
#   IBUF                                  : 4
#   OBUF                                  : 2
```

The logic diagram illustrates a 4-bit counter implemented with a 4-to-1 multiplexer (a_mux0002) and D flip-flops. The counter is composed of four D flip-flops, each with inputs for clock (Clk), data (D), and set/reset (Sclr). The output of each flip-flop is connected to the input of the next flip-flop in a chain. The multiplexer selects between four data inputs (a_cmp_eq0000, a_cmp_eq0001, a_cmp_eq0002, a_cmp_eq0003) based on a 2-bit select signal (Sclr). The output of the multiplexer is connected to the D input of the first flip-flop. The clock signal (clk) is connected to the clock inputs of all flip-flops. The reset signal (clr) is connected to the Sclr inputs of all flip-flops. The output of the counter is shown as a 4-bit bus (q) and its complement (qbar).

8.4 Design of T Flip Flop

Aim: To simulate and verify the **T flip flop** with Behavioral model

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity tff is
    Port ( t : in  STD_LOGIC;
          clk,clr : in  STD_LOGIC;
          q : inout STD_LOGIC:= '0'
          qbar: out STD-LOGIC);
end tff;

architecture Behavioral of tff is
begin
    process(clk,t)
    begin
        if(clk'event and clk='1') then
            if(clr='1')then q<='0';qbar<='1';
                elsif(t='0')then q<=q;qbar<=not q;
                else    q<=not q;qbar<=q;
            end if;
        end if;
    end process;
end Behavioral;
```

 Simulation Waveform:**Synthesis Report:**

```

=====
=====
*                               *
Final Report
=====
=====


```

Cell Usage:

```

# BELS : 11
# AND2 : 3
# GND : 1
# INV : 4
# OR2 : 3
# FlipFlops/Latches : 2
# FD : 1
# FDCE : 1
# IO Buffers : 5
# IBUF : 3
# OBUF : 2

```

 RTL Schematic:

Review Questions

1. Define Flip-flop.
2. What is the difference between flip-flop and latch?
3. What is the difference between flip-flop and Register?
4. Define ripple counter.
5. What is the drawback of RS flip flop?
6. What is race around condition?
7. What are the applications of D flip flop?
8. Which flip-flop has XOR logic?
9. Which flip-flop has XNOR logic?
10. Write the characteristic equation of T flip flop.

EXERCISE PROBLEMS

1. To simulate and verify the SR flip-flop with data flow model
2. To simulate and verify the SR flip-flop with behavioral model
3. To simulate and verify the SR flip-flop with structural model
4. To simulate and verify the D flip-flop with data flow model
5. To simulate and verify the D flip-flop with behavioral model
6. To simulate and verify the D flip-flop with structural model
7. To simulate and verify the JK flip-flop with data flow model
8. To simulate and verify the JK flip-flop with behavioral model
9. To simulate and verify the JK flip-flop with structural model
10. To simulate and verify the T flip-flop with data flow model
11. To simulate and verify the T flip-flop with behavioral model
12. To simulate and verify the T flip-flop with structural model
13. To simulate and verify the Master Slave JK flip-flop with data flow model
14. To simulate and verify the Master Slave JK flip-flop with behavioral model
15. To simulate and verify the Master Slave JK flip-flop with structural model
16. To simulate and verify D Latch with data flow model
17. To simulate and verify D Latch with behavioral model

9.1 Design of 4-bit binary counter (synchronous)

Aim: To simulate and verify the **4-bit binary counter (synchronous)**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity synbicount is
    port (clk: in std_logic;
          rst: in std_logic;
          q: inout std_logic_vector (3 downto 0));
end synbicount;

architecture behavioral of synbicount is
    signal count:std_logic_vector(3 downto 0);
    begin
        process (clk, rst)
        begin
            if (clk'event and clk = '1') then
                if (rst = '1') then count <= "0000"; --for down counter count=>"1111"
                else count <= count + 1; -- for down counter count<=count-1;
                end if;
                q<= count;
            end if;
        end process;
    end behavioral;
```

 
Simulation Waveform:**Synthesis Report:**

```
=====
=====
*                               *
Final Report
=====
=====
```

Cell Usage:

```
# BELS : 14
# AND2 : 6
# INV : 5
# XOR2 : 3
# FlipFlops/Latches : 8
# FD : 8
# IO Buffers : 6
# IBUF : 2
# OBUF : 4
```

```
=====
=====
```

 RTL Schematic:

9.2 Design of 4-bit binary counter (asynchronous)

Aim: To simulate and verify the **4-bit binary counter (asynchronous)**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP

Software : Xilinx 9.2i.


Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity asybin1 is
    port (clk: in std_logic;
          rst: in std_logic;
          q: inout std_logic_vector (3 downto 0));
end asybin1;

architecture behavioral of asybin1 is
    signal count:std_logic_vector(3 downto 0);
    begin
        process (clk)
            begin
                if (rst = '1') then count <= "0000"; --for down counter count<="1111"
                else if (clk'event and clk = '1') then
                    count <= count + 1; -- for down counter count<=count-1;
                    q<= count;
                end if;
            end if;
        end process;
    end behavioral;
```


Simulation Waveform:

 

Synthesis Report:

```
=====
=====
*                               *
                        Final Report
*                               *
=====
=====
Cell Usage:
# BELS                               : 8
# AND2                               : 2
# GND                                 : 1
# INV                                 : 2
# XOR2                               : 3
# FlipFlops/Latches                  : 8
# FDC                                : 8
# FDCE                               : 4
# IO Buffers                          : 6
# IBUF                                : 2
# OBUF                                : 4
=====
=====
```

RTL Schematic:

 

9.3 Design of BCD up counter

Aim: To simulate and verify the **BCD up counter**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,

Software : Xilinx 9.2i.

Program:


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity bcdupcount is
    port (clk: in std_logic;
          rst: in std_logic;
          q: inout std_logic_vector (3 downto 0));
end bcdupcount;
```

architecture behavioral of bcdupcount is

signal count:std_logic_vector(3 downto 0);

```
begin
    process (clk)
    begin
        if rst = '0' or count="1010" then count <= "0000"; --for down counter count<="1111"
        else if (clk'event and clk = '1') then
            count <= count + 1; -- for down counter count<=count-1;
            q<= count;
        end if;
    end if;
    end process;
end behavioral;
```

 Simulation Waveform:**Synthesis Report:**

```

=====
*                               *
Final Report
=====
=====


```

Cell Usage:

```

# BELS                               : 15
# AND2                               : 5
# GND                                : 1
# INV                                 : 5
# OR2                                 : 1
# XOR2                               : 3
# FlipFlops/Latches                  : 8
# FDC                                : 4
# FDCE                               : 4
# IO Buffers                          : 6
# IBUF                               : 2
# OBUF                               : 4

```

 RTL Schematic:

9.4 Design of BCD down counter

Aim: To simulate and verify the **BCD down counter**

Apparatus:

Personal Computer:1 No

Operating System : Windows XP,


Software : Xilinx 9.2i.

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity bcddntcount is
    port (clk: in std_logic;
          rst: in std_logic;
          q: inout std_logic_vector (3 downto 0));
end bcddntcount;

architecture behavioral of bcddntcount is
    signal count:std_logic_vector(3 downto 0);
    begin
        process (clk)
        begin
            if rst = '0' or count="1111" then count <= "1001"; --for down counter
count<="1111"
            else if (clk'event and clk = '1') then
                count <= count - 1; -- for down counter count<=count-1;
                q<= count;
            end if;
        end process;
    end behavioral;
```

 Simulation Waveform:**Synthesis Report:**

```
=====
=====
```

```

*                               *
Final Report
*                               *
=====
=====
```


Cell Usage:

```

# BELS                               : 14
# AND4                               : 1
# GND                                : 1
# INV                                : 6
# OR2                                : 3
# XOR2                               : 3
# FlipFlops/Latches                 : 8
# FDC                               : 2
# FDCE                              : 4
# FDP                               : 2
# IO Buffers                        : 6
# IBUF                              : 2
# OBUF                              : 4

```

```
=====
=====
```

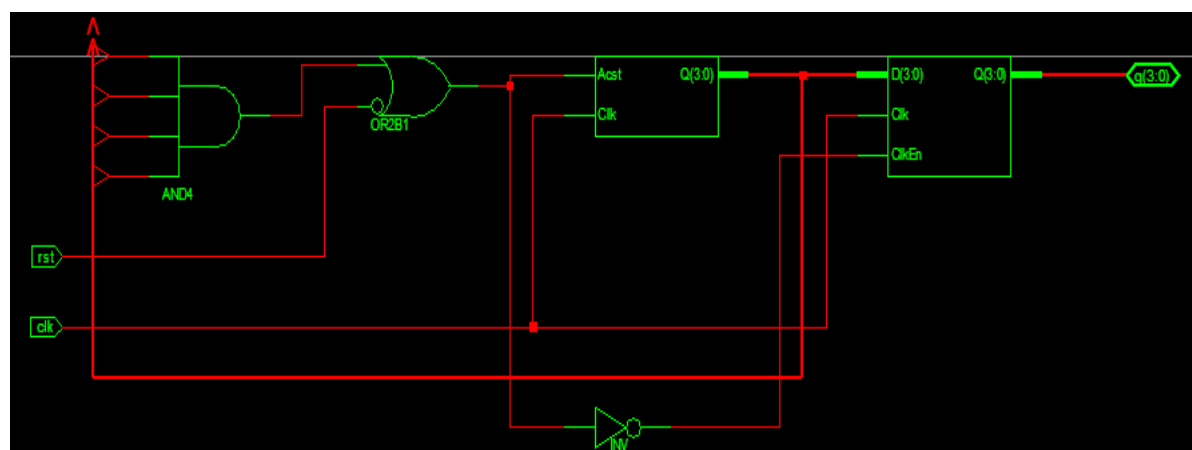RTL Schematic:

Viva Questions

1. Define counter.
2. What is the difference between synchronous counter and asynchronous counter?
3. What is the difference between counter and register?
4. What is the use of Johnson Counter?
5. What is ring counter?
6. What is the other name of Johnson counter?
7. How many flip-flops are required to design mod-6 counter?
8. How many flip-flops are required to design mod-10 counter?
9. What is the difference between combinational and sequential circuits?
10. Definition of sequential circuits.

EXERCISE PROBLEMS

1. To simulate and verify the 2-bit binary counter (synchronous).
2. To simulate and verify the 3-bit binary counter (synchronous).
3. To simulate and verify the 2-bit binary counter (asynchronous).
4. To simulate and verify the 3-bit binary counter (asynchronous).
5. To simulate and verify the 2-bit BCD up counter.
6. To simulate and verify the 3-bit BCD up counter.
7. To simulate and verify the 2-bit BCD down counter.
8. To simulate and verify the 3-bit BCD down counter.
9. To simulate and verify the 2-bit Ring counter.
10. To simulate and verify the 3-bit Ring counter.
11. To simulate and verify the 2-bit Twisted Ring counter.
12. To simulate and verify the 3-bit Twisted Ring counter.
13. To simulate and verify the 4-bit binary counter (synchronous).
14. To simulate and verify the 4-bit binary counter (asynchronous).
15. To simulate and verify the 4-bit BCD up counter
16. To simulate and verify the 4-bit BCD down counter
17. To simulate and verify the 4-bit Ring counter (synchronous).
18. To simulate and verify the 4-bit Ring counter (asynchronous)

10. Finite State Machine Design

Aim: To develop the source code for finite state machine by using HDL and obtain the simulation and synthesis.

Apparatus:


Personal Computer: 1 No

Operating System : Windows XP,

Software : Xilinx 9.2i.


The output of a Moore finite state machine depends only on the machine's current state; transitions are not directly dependent upon input.

 - The use of a Mealy FSM leads often to a reduction of the number of states.



Present State	Next State		Output	
	X = 0	X = 1	X = 0	X = 1
S0	S0	S1	0	0
S1	S0	S3	1	0
S2	S0	S2	1	0
S3	S0	S2	1	0

Block Diagram:

 

Program:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

-- FSM model consists of two concurrent processes
-- state_reg and comb_logic
-- we use case statement to describe the state
-- transistion. All the inputs and signals are
-- put into the process sensitive list.
-----
entity seq_design is
port(   a:           in std_logic;
        clock:       in std_logic;
        reset:       in std_logic;
        x:           out std_logic
);
end seq_design;

architecture FSM of seq_design is
    -- define the states of FSM model
    type state_type is (S0, S1, S2, S3);
    signal next_state, current_state: state_type;

begin
    -- cocurrent process#1: state registers
    state_reg: process(clock, reset)
    begin
        if (reset='1') then
            current_state <= S0;
        elsif (clock'event and clock='1') then
            current_state <= next_state;
        end if;
    end process;

    -- cocurrent process#2: combinational logic
    comb_logic: process(current_state, a)
    begin
        -- use case statement to show the
        -- state transistion

        case current_state is

            when S0 => x <= '0';
                     if a='0' then
                         next_state <= S0;
                     elsif a='1' then
                         next_state <= S1;
                     end if;
        end case;
    end process;
end architecture;
```

```

when S1 => x <= '0';
            if a='0' then
                next_state <= S1;
            elsif a='1' then
                next_state <= S2;
            end if;

when S2 => x <= '0';
            if a='0' then
                next_state <= S2;
            elsif a='1' then
                next_state <= S3;
            end if;

when S3 => x <= '1';
            if a='0' then
                next_state <= S3;
            elsif a='1' then
                next_state <= S0;
            end if;


when others => x <= '0';
                next_state <= S0;

end case;
end process;

end FSM;

```

Simulation Waveform:

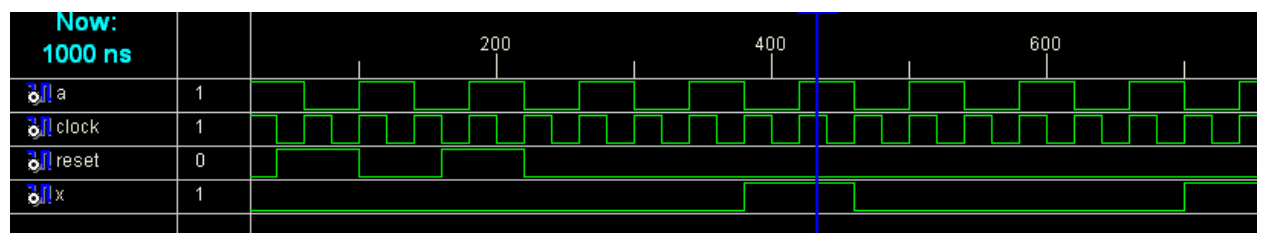

Synthesis Report:

```

=====
=====
*                               *
Final Report
=====
=====

```

Cell Usage:

```


# BELS : 2
# AND2 : 2
# GND : 1
# FlipFlops/Latches : 2
# FTC : 2
# IO Buffers : 4

```

```
# IBUF : 3
# OBUF : 1
```

```
=====
=====
```

RTL Schematic:

 

Result: Thus the program for FSM has been verified and also simulation and synthesis reports have been verified.

Viva Questions

1. What is the function of Mealy machine?
2. What is the difference between blocking and non blocking statement?
3. What is the difference between 'always' and 'initial' statements?
4. What is the difference between 'case x' and 'case z'?
5. What is the function of Moore machine?
6. What are the differences between Moore and Mealy machine?
7. What is meant by simulation?
8. What is meant by synthesis?
9. What are advantages of verilog over high level languages?
10. Define Noise margin.

EXERCISE PROBLEMS

1. To simulate and verify the 4-bit binary counter FSM.
2. To simulate and verify the 4-bit BCD down counter FSM.
3. To simulate and verify the 4-bit BCD up counter FSM.
4. To simulate and verify the 4-bit synchronous counter FSM.
5. To simulate and verify the 4-bit asynchronous counter FSM.
6. To simulate and verify 3-bit binary counter FSM
7. To simulate and verify 3-bit BCD down counter FSM
8. To simulate and verify 3-bit BCD up counter FSM
9. To simulate and verify 3-bit synchronous counter FSM
10. To simulate and verify 3-bit asynchronous counter FSM
11. To simulate and verify 4-bit Ring counter FSM
12. To simulate and verify 3-bit Ring counter FSM
13. To simulate and verify 4-bit Twisted Ring counter FSM
14. To simulate and verify 3-bit Twisted Ring counter FSM
15. To simulate and verify the 4-bit binary counter FSM.(Synchronous)
16. To simulate and verify the 4-bit binary counter FSM. .(Asynchronous)
17. To simulate and verify the 3-bit binary counter FSM.(Synchronous)
18. To simulate and verify the 3-bit binary counter FSM. .(Asynchronous)
19. To simulate and verify the 4-bit ring counter FSM.(Synchronous)
20. To simulate and verify the 4-bit ring counter FSM. .(Asynchronous)